

ECE 10C

Fall 2020

Slide Set 1

Instructor: Galan Moody

TA: Kamyar Parto

When your CS friends talk about their deep learning projects and you remember when you got an arduino LED to blink



Last Week

- Introduction to course

This Week

- KVL/KCL, node methods
- Thevenin
- 1st-order RC/RL circuits

Important Items:

**Homework #1 posted
Due Th, Oct 15 by 5 pm**

**Lab #1 posted
Due Fr, Oct 16**

Piazza Forum for Class Discussions

Piazza is a Q&A platform designed to get you great answers from classmates and instructors fast.

- 1. Edit questions and answers wiki-style.**
- 2. Add a follow-up to comment or ask further questions.**
- 3. Go anonymous.**
- 4. Tag your posts.**
- 5. Format code and equations.**
- 6. View and download class details and resources.**

This Week

Review Chapters 9 and 10 of the textbook to get ready for the course, which really begins week 2



It's important to understand how to do the following:

1. Use KVL, KCL and the node method to formulate the differential equations for analyzing a circuit with energy-storage elements
2. Write Thevenin equivalent circuits to simplify your analysis
3. For first-order RC and RL circuits: Find the homogeneous and particular solutions
4. Use the initial conditions to evaluate the constants in the homogeneous solution

Quiz Time!





Assume capacitors are uncharged at time $t = 0$.

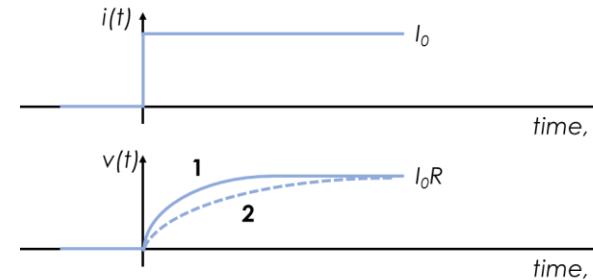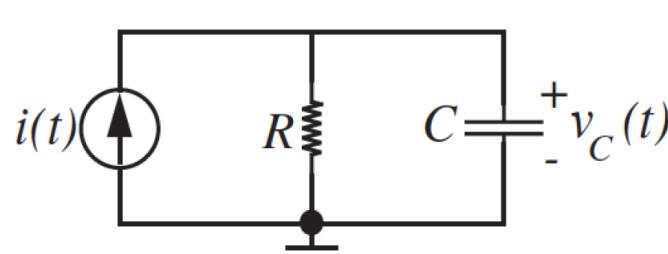Q1 [2 point]. For the parallel RC circuit shown on the left, with a constant-current step source shown on the top right, choose the answer that best describes the circuits for the capacitor voltage shown on the bottom right. Curves 1 and 2 correspond to circuits with R_1, C_1 and R_2, C_2 , but are otherwise identical.




- (a) $R_1C_1 = R_2C_2$ (b) $R_1 > R_2 \text{ & } C_1 < C_2$ (c) $R_1C_1 > R_2C_2$ (d) $C_1 < C_2$

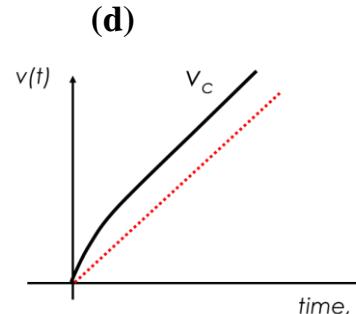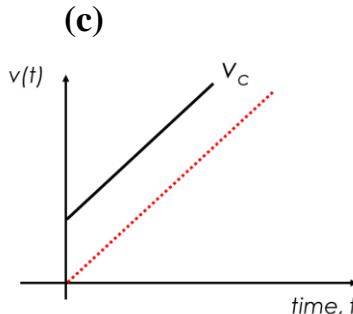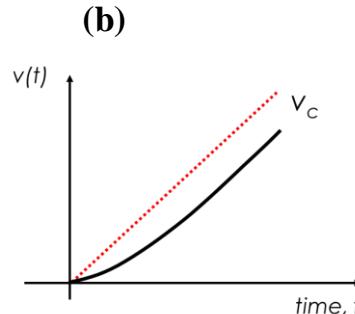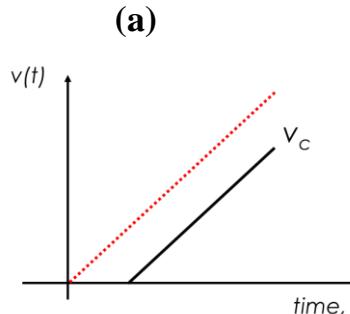Q2 [3 points]. (a) For an RC series circuit with a linear voltage ramp starting at 0V, choose the correct capacitor voltage.



We Need to Pick a Convention

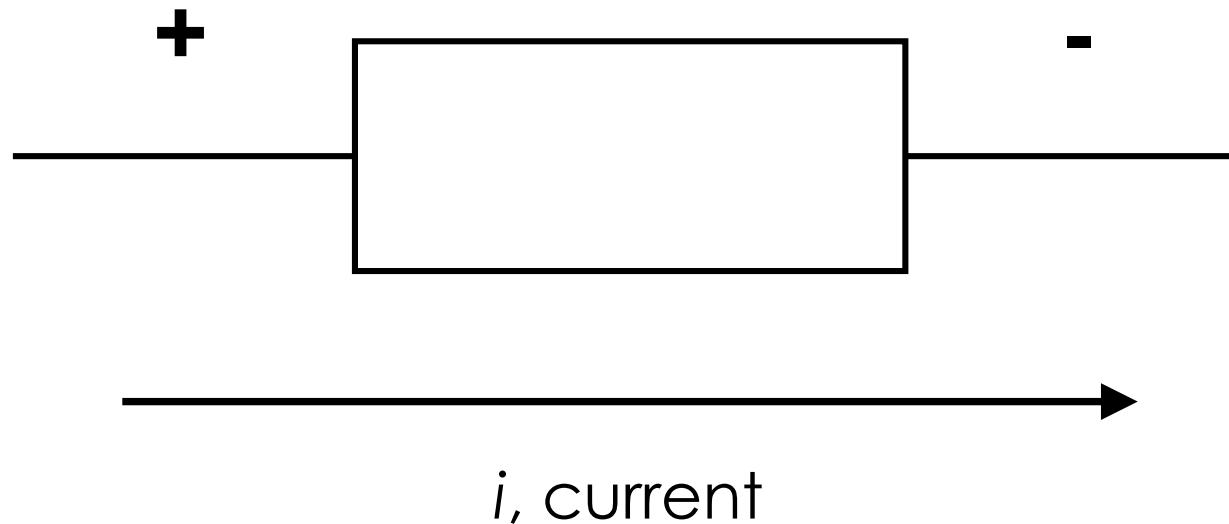
How we define the direction of current and voltage drop is up to us, as long as we are consistent



$$V_+ - V_- > 0$$

Review: KCL


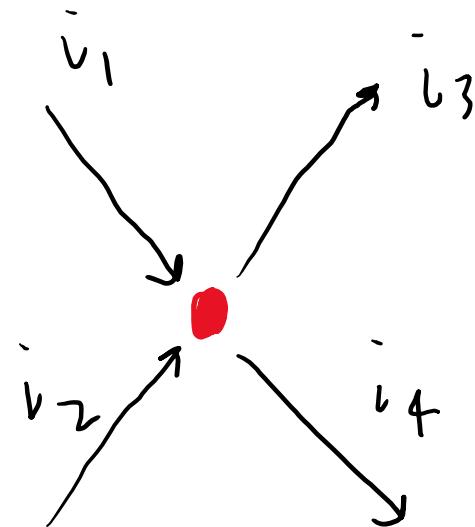
Kirchoff's Current Law: Charge/current can't be created nor destroyed.
Algebraic sum of current has to equal zero at a node



$$i_1 + i_2 - i_3 - i_4 = 0.$$

Review: KCL

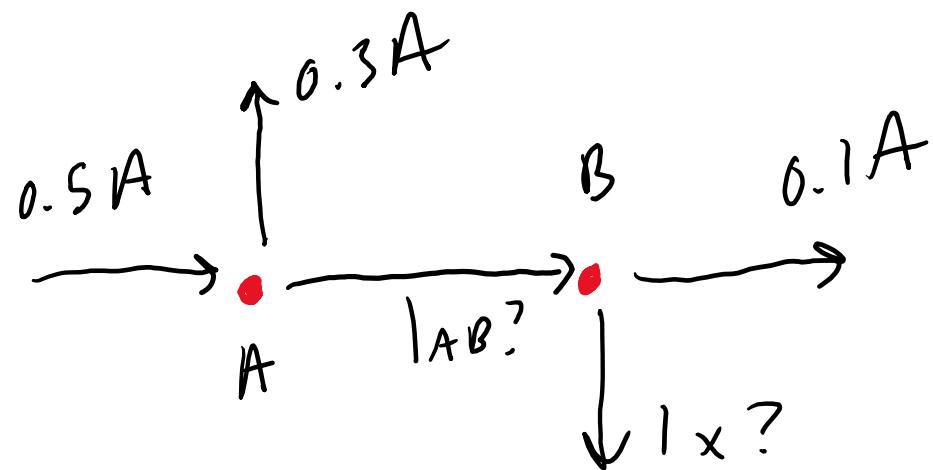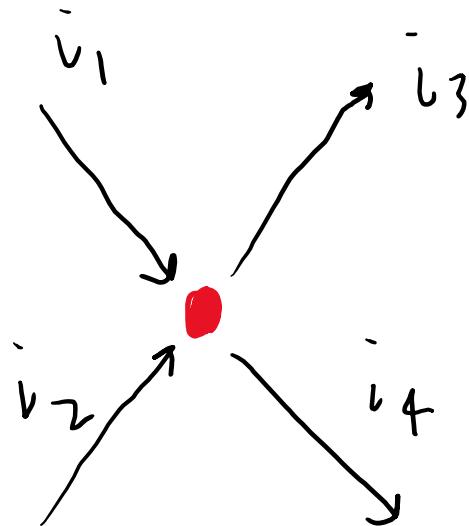Kirchoff's Current Law: Charge/current can't be created nor destroyed.
Algebraic sum of current has to equal zero at a node




$$i_1 + i_2 - i_3 - i_4 = 0$$


$$0.5\text{ A} - 0.3\text{ A} - I_{AB} = 0$$
$$I_{AB} = 0.2\text{ A}$$

Review: KCL

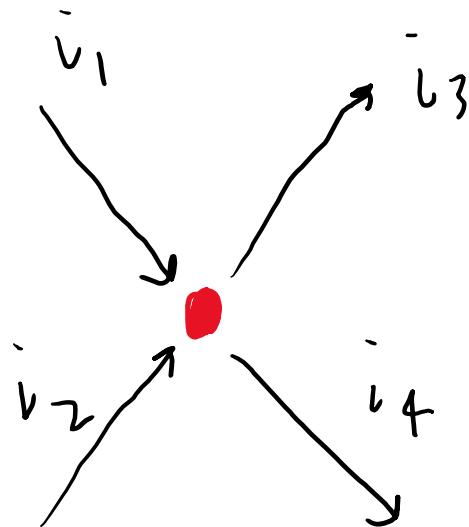Kirchoff's Current Law: Charge/current can't be created nor destroyed.
Algebraic sum of current has to equal zero at a node



$$i_1 + i_2 - i_3 - i_4 = 0$$

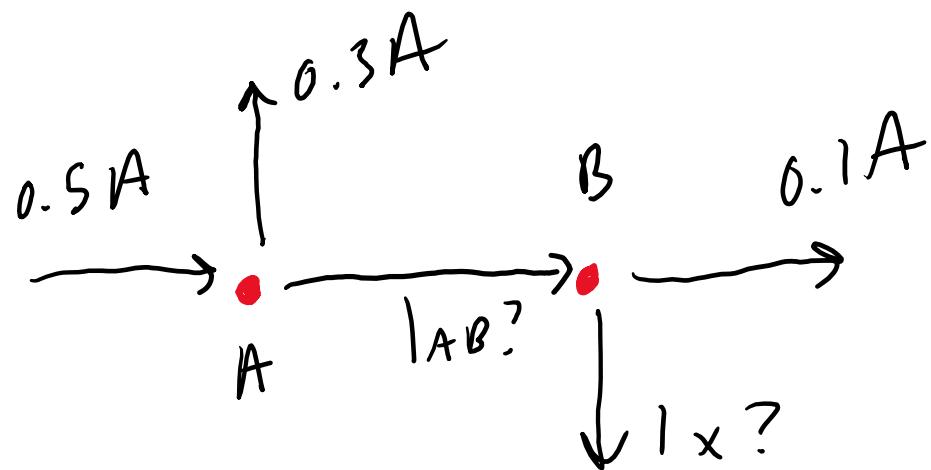


$$0.5\text{ A} - 0.3\text{ A} - I_{AB} = 0$$

$$I_{AB} = 0.2\text{ A}$$

$$0.2\text{ A} - 0.1\text{ A} - I_x = 0 ; I_x = 0.1\text{ A}$$


Review: KVL

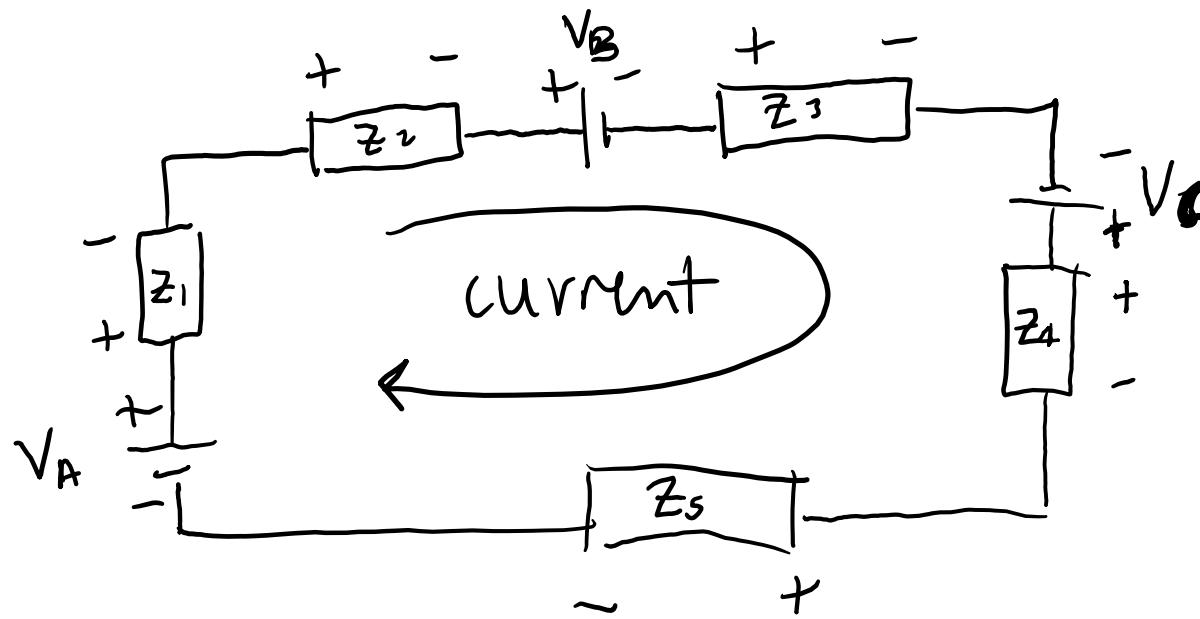Kirchoff's Voltage Law: Algebraic sum of voltage is equal zero around a loop




Review: KVL

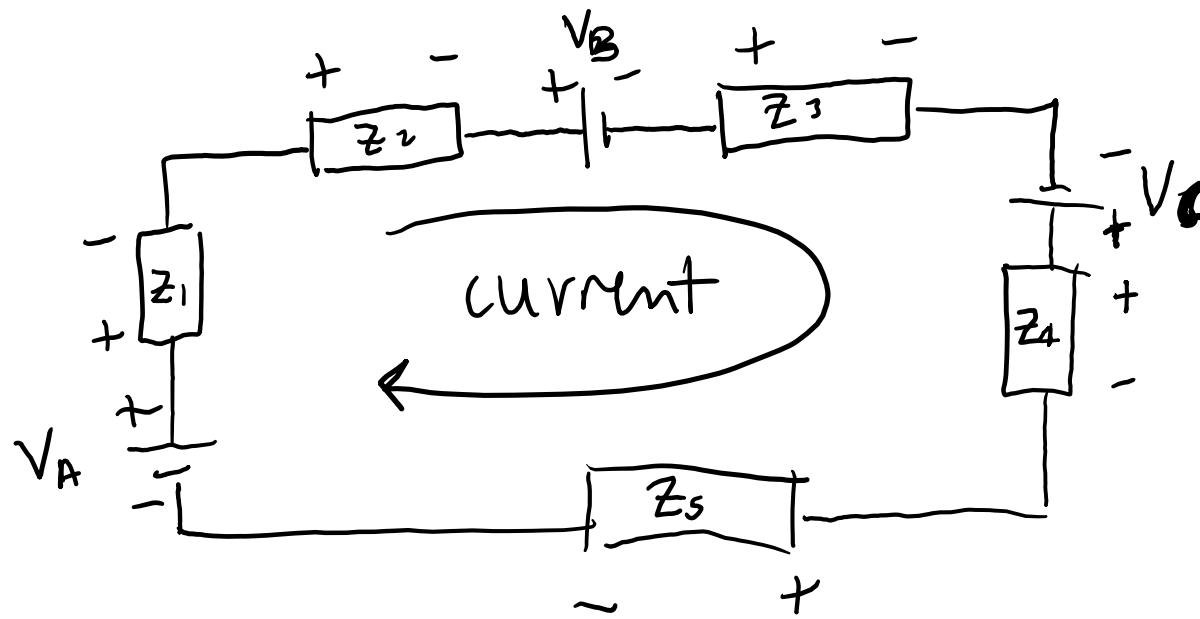Kirchoff's Voltage Law: Algebraic sum of voltage is equal zero around a loop




$$+V_A - V_1 - V_2 - V_B - V_3 + V_C - V_4 - V_S = 0$$

Example of KVL/KCL

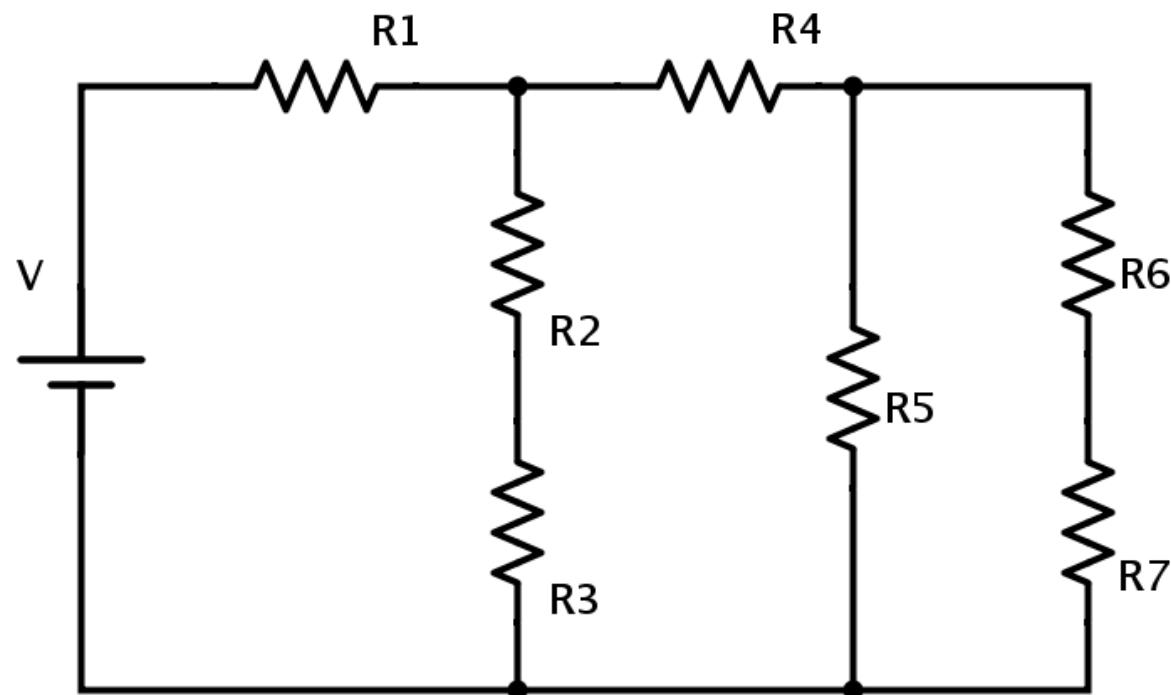

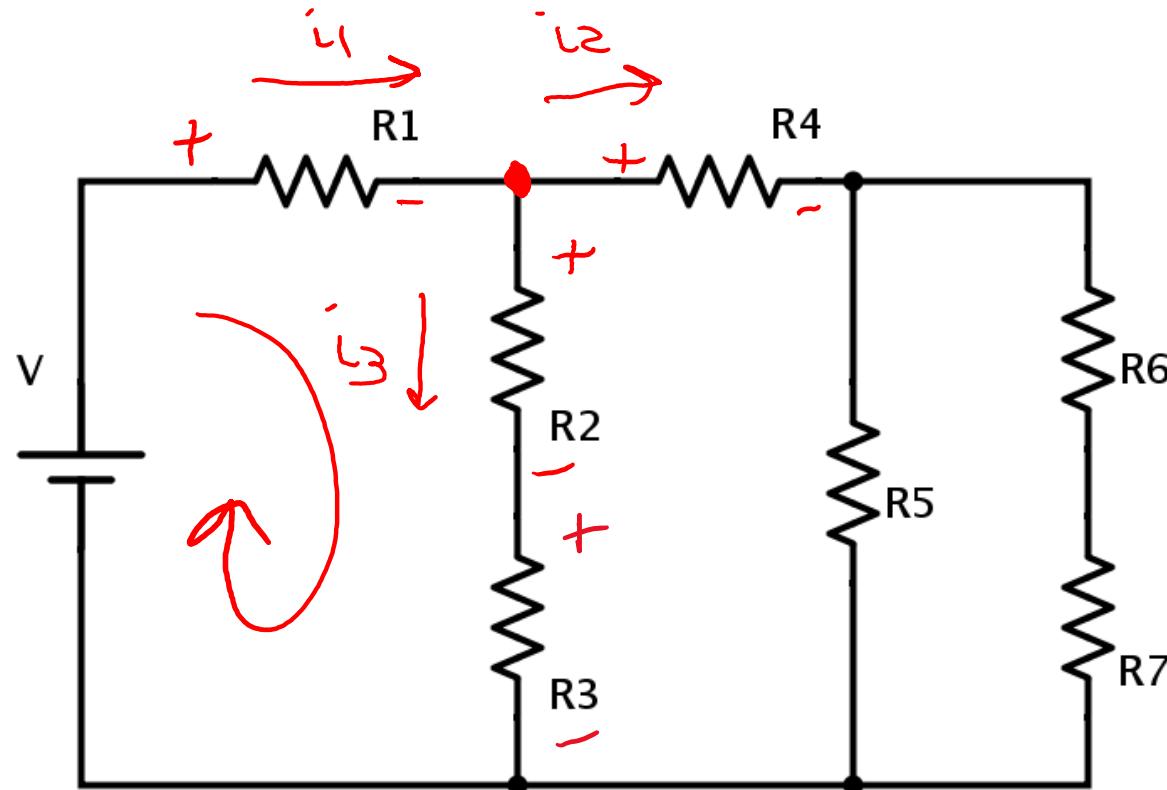Example of KVL/KCL


$$KCL \quad \sum i = \phi \quad i_1 - i_2 - i_3 = 0$$



$$KVL \quad \sum v = \phi \quad V - V_1 - V_2 - V_3 = 0$$


Review: Node Method

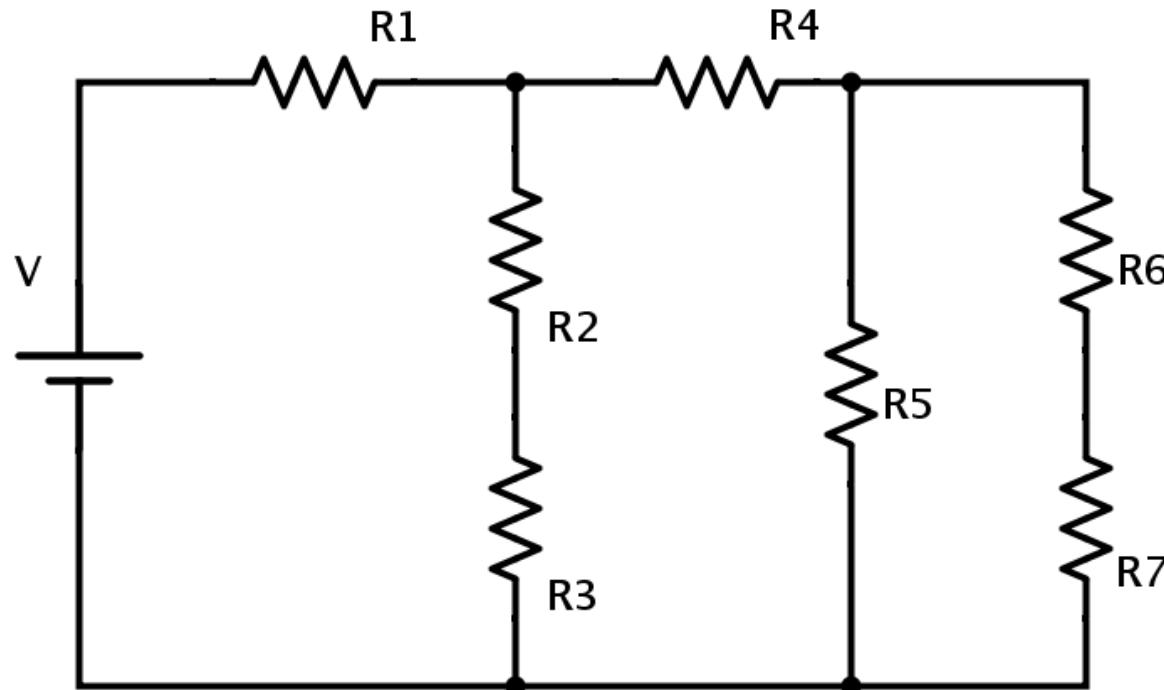Combines KCL/KVL at a given node to write KCL in terms of what we know



Review: Node Method

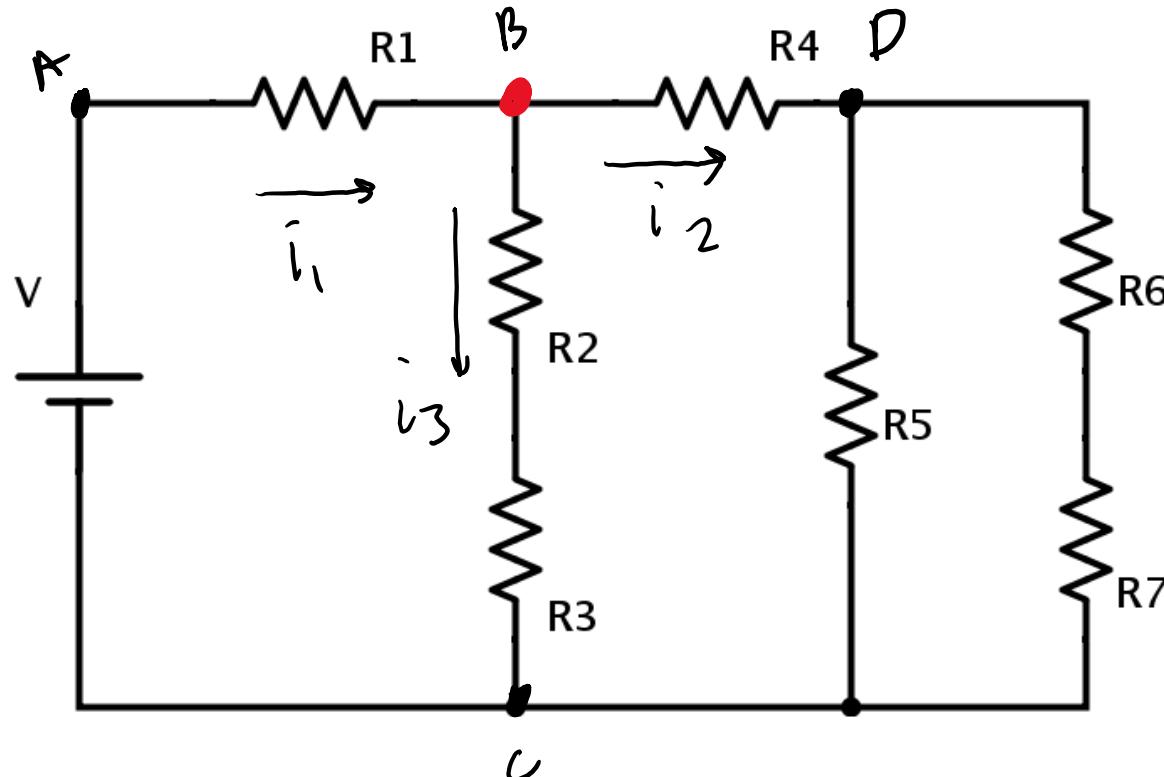Combines KCL/KVL at a given node to write KCL in terms of what we know




$$i_1 = i_2 + i_3$$

$$V = IR$$

Review: Node Method

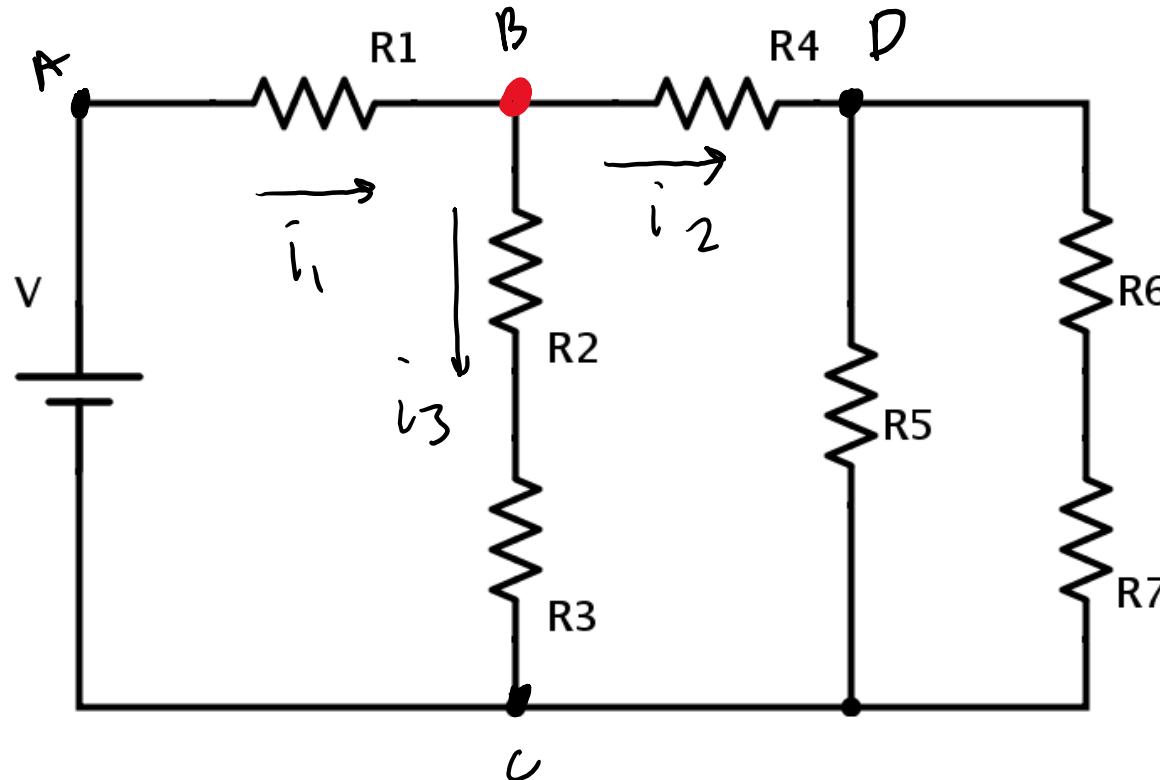Combines KCL/KVL at a given node to write KCL in terms of what we know




$$i_1 = i_2 + i_3$$

$$\frac{V_A - V_B}{R_1} = \frac{V_B - V_D}{R_4} + \frac{V_B - V_C}{R_2 + R_3}$$

$$V = IR$$


Review: Node Method

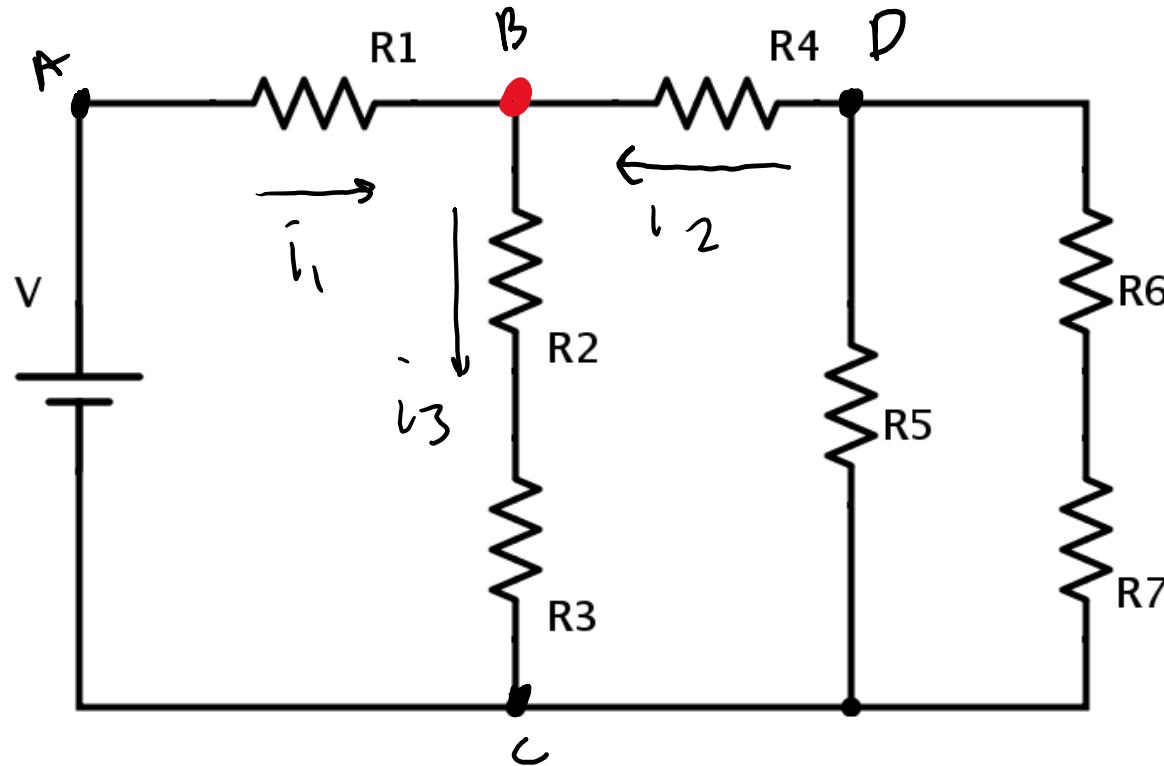Combines KCL/KVL at a given node to write KCL in terms of what we know



Review: Node Method

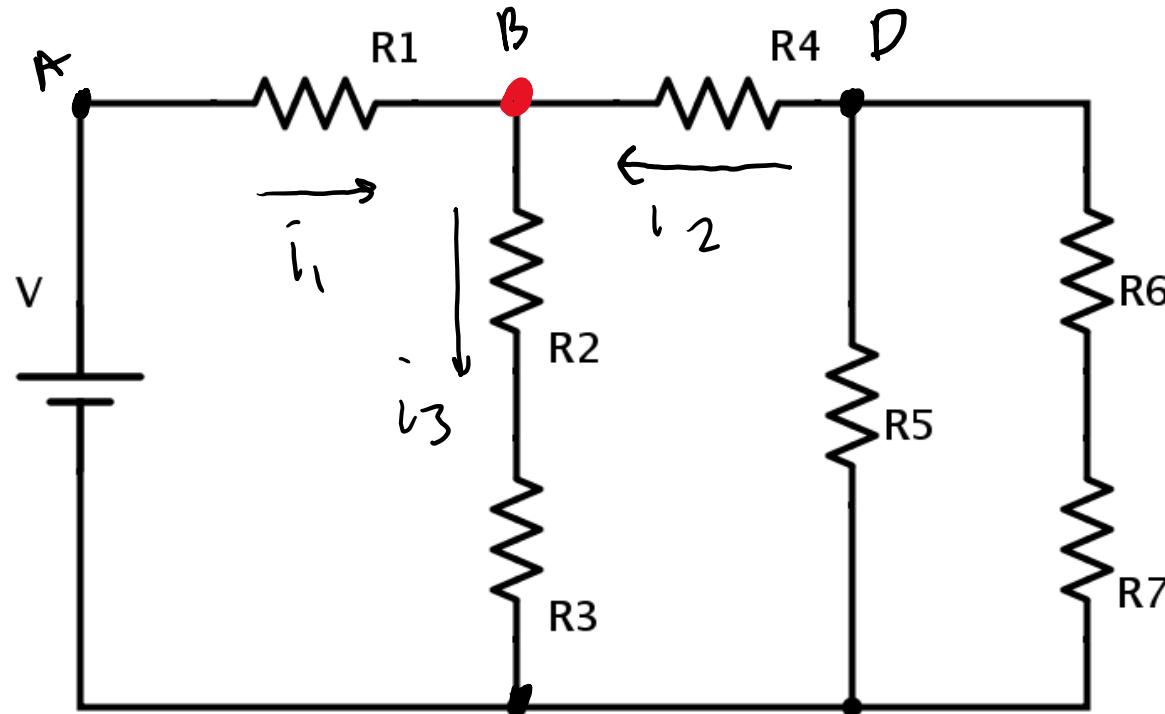Combines KCL/KVL at a given node to write KCL in terms of what we know




$$i_1 + i_2 = i_3$$

$$V = IR$$

Review: Node Method

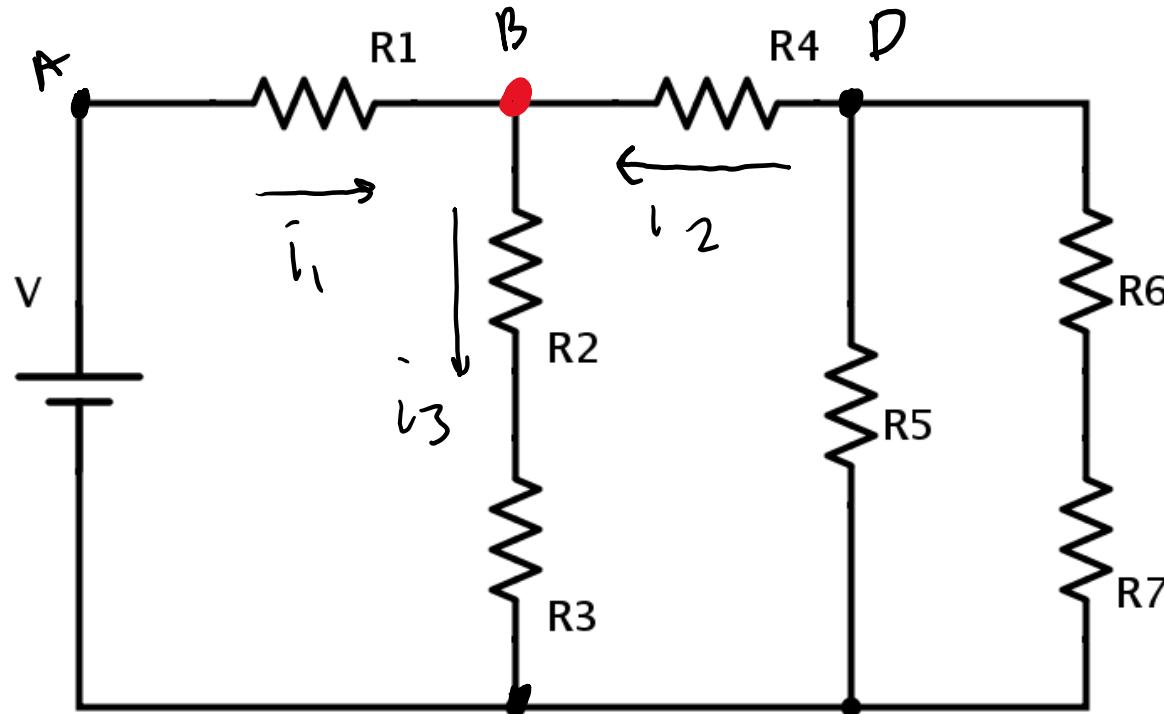Combines KCL/KVL at a given node to write KCL in terms of what we know




$$i_1 + i_2 = i_3$$


$$\frac{V_A - V_B}{R_1} + \frac{V_D - V_B}{R_4} = \frac{V_B - V_C}{R_2 + R_3}$$

$$V = IR$$


Example 1

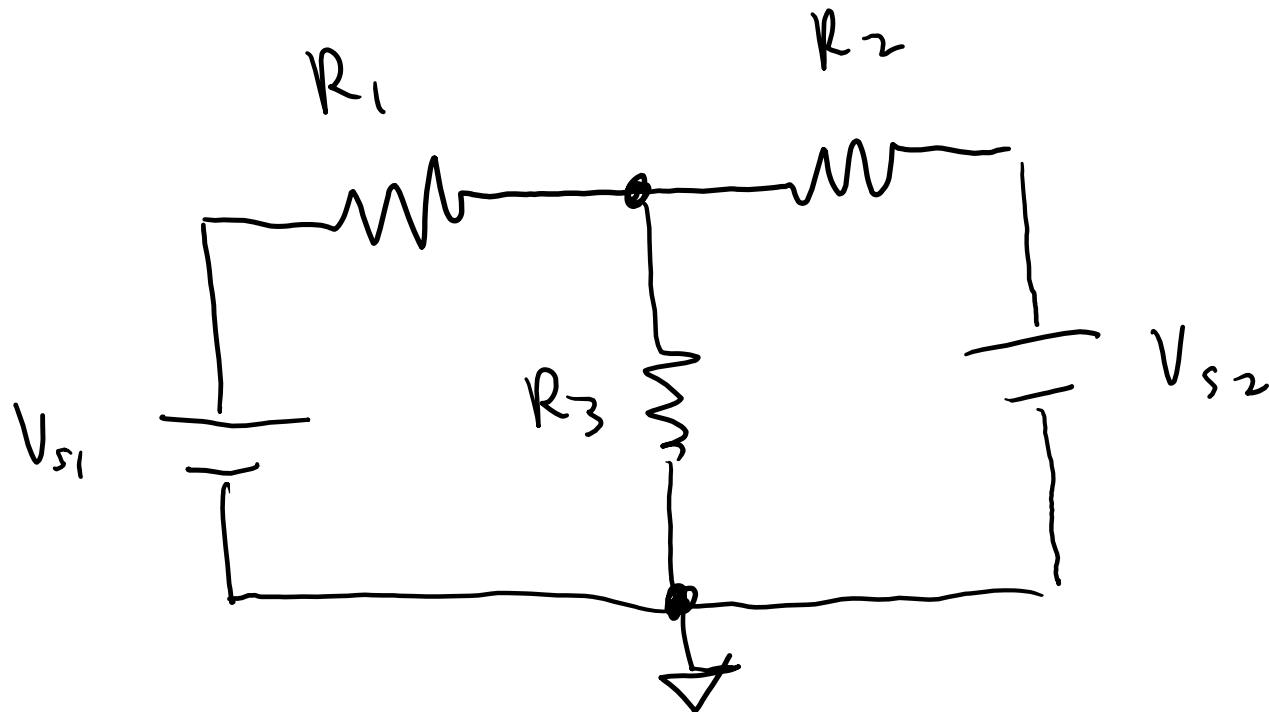

Example 1

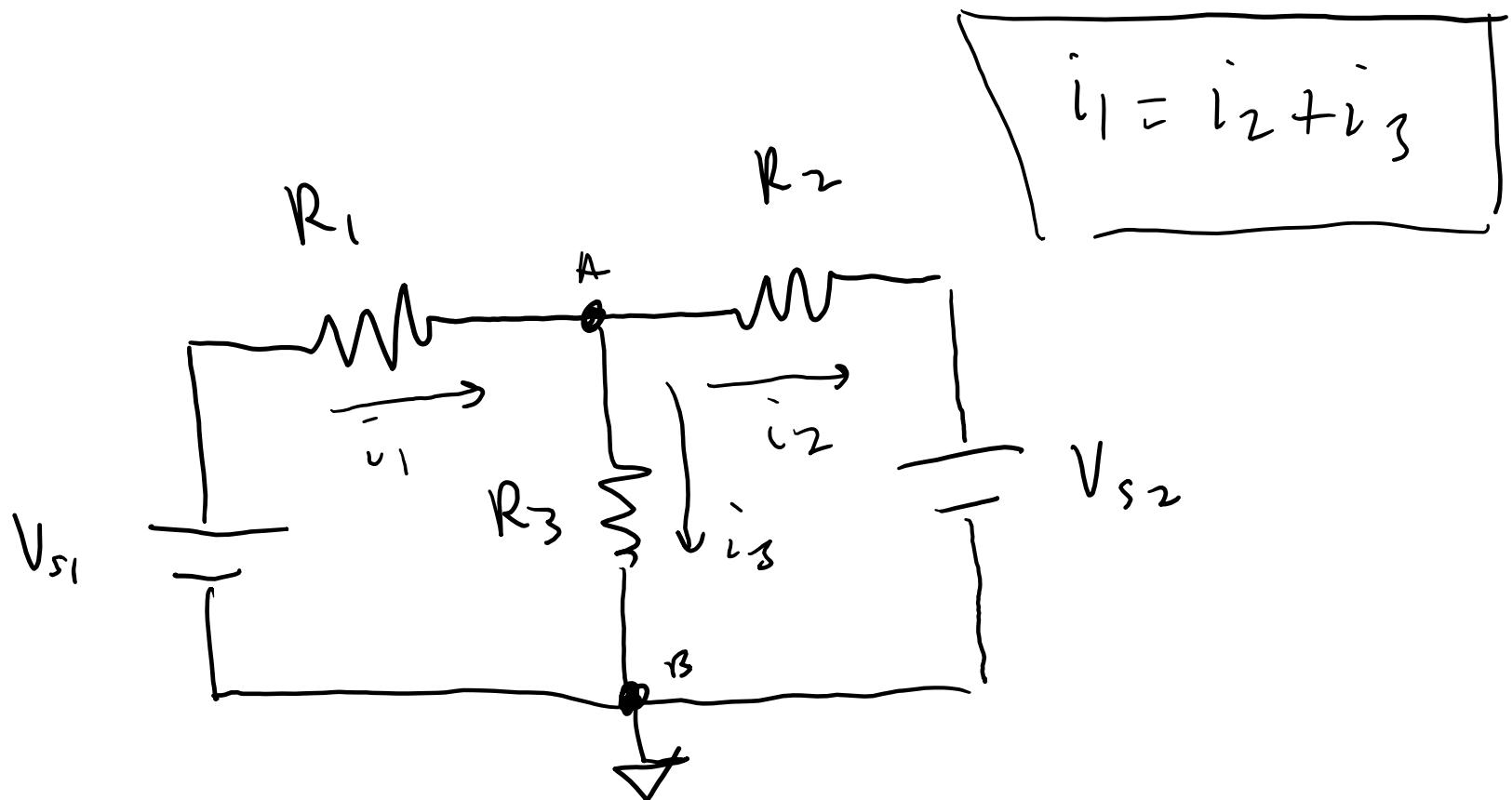


Example 1

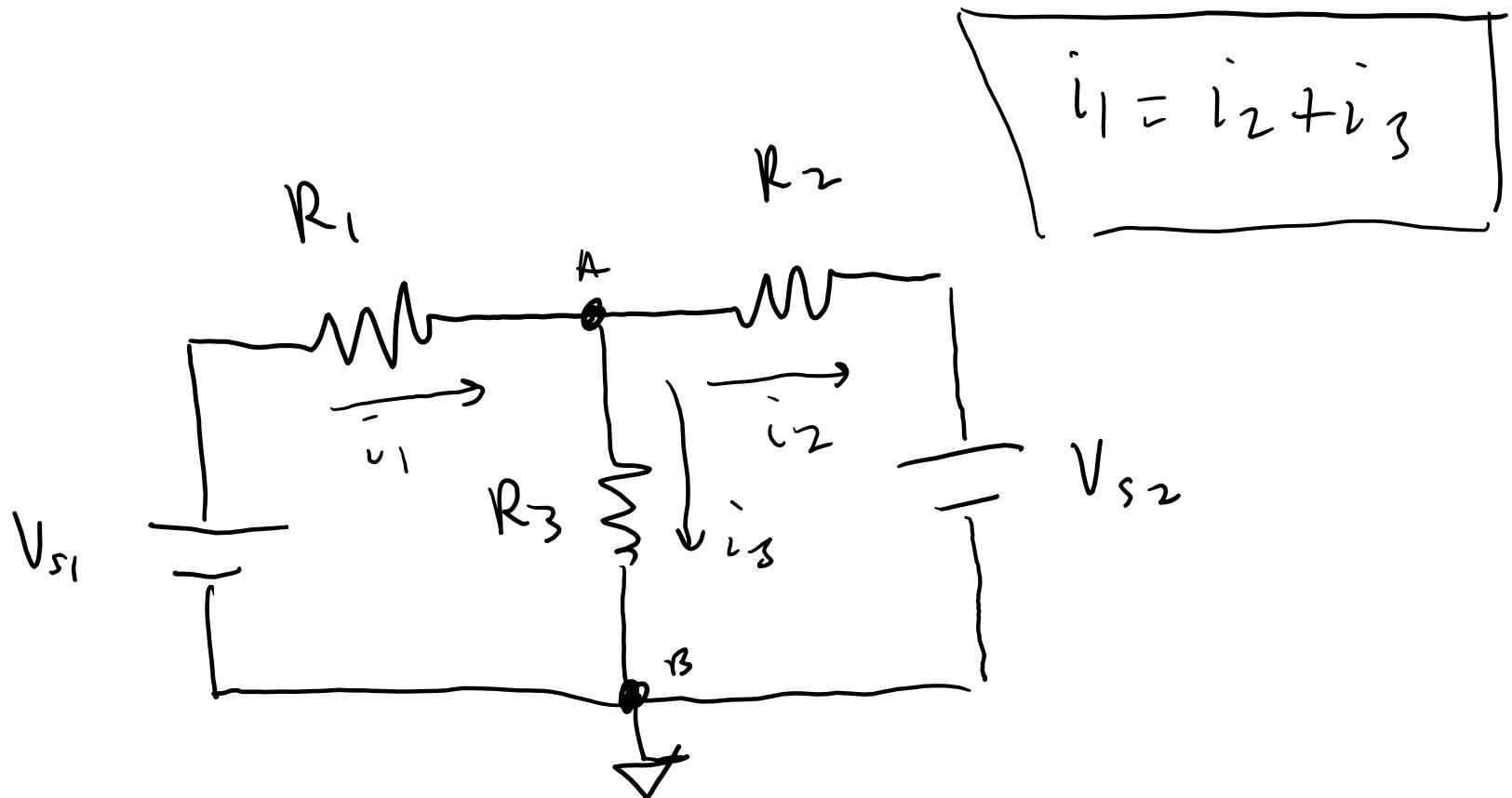


$$\frac{V_{S1} - V_A}{R_1} = \frac{V_A - V_{S2}}{R_2} + \frac{V_A - V_B}{R_3}$$

Example 2

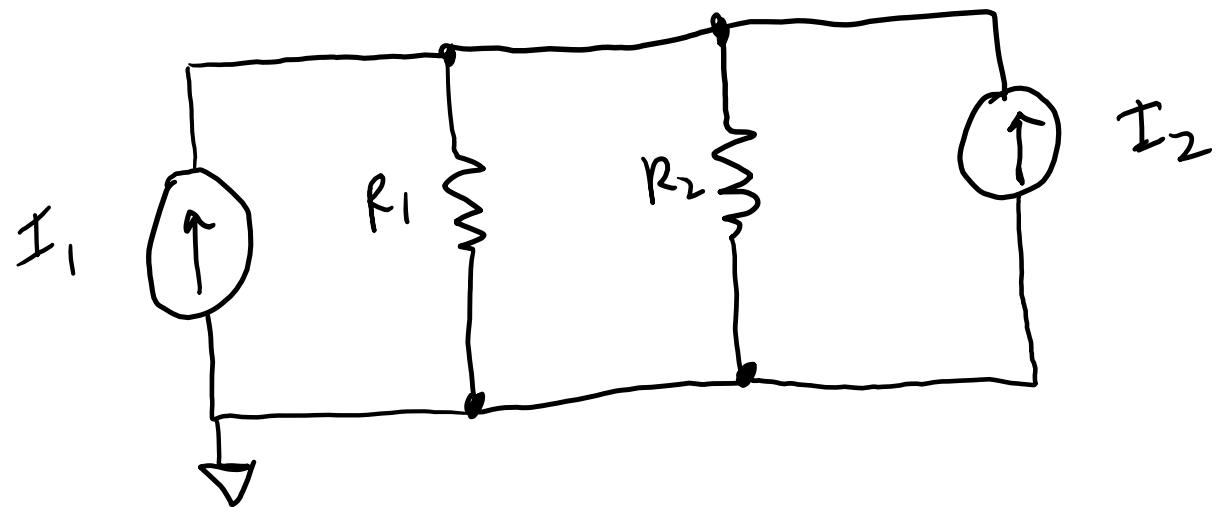


Example 2

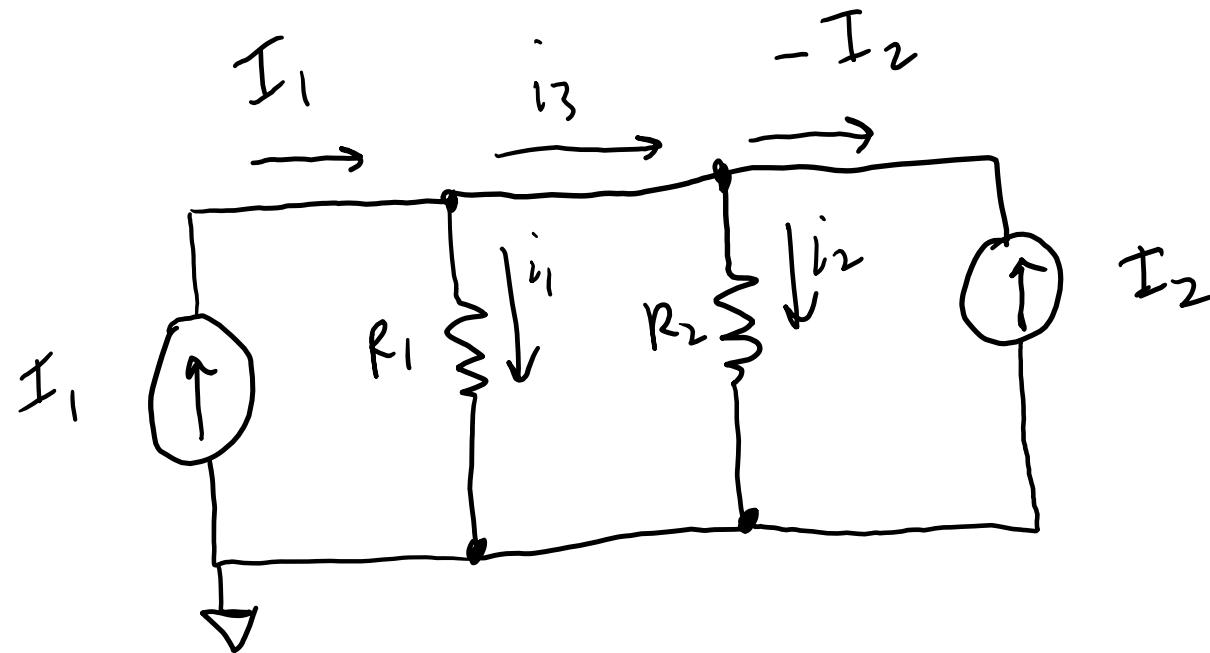

$$I_1 = i_1 + i_3$$

$$i_3 = -I_2 + i_2$$

Example 2

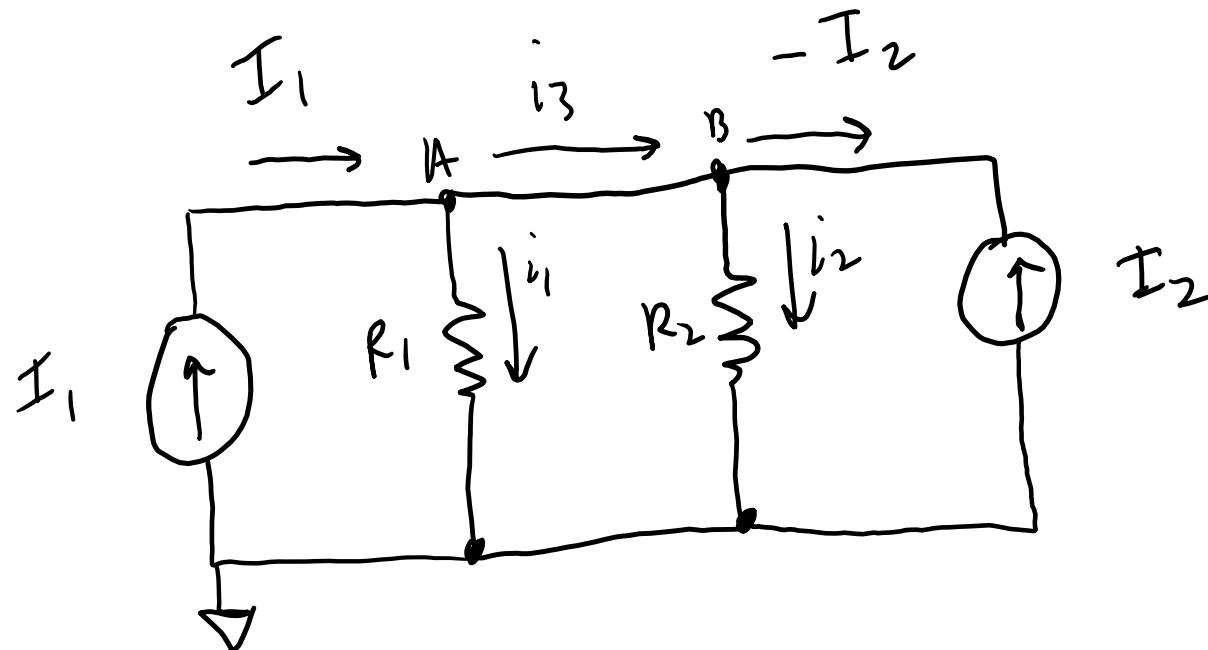

$$I_1 = i_1 + i_3$$


$$i_3 = -I_2 + i_2$$

$$I_1 = \frac{V_A}{R_1} + i_3$$

$$i_3 = -I_2 + \frac{V_B}{R_2}$$


Review: Thevenin Equivalent

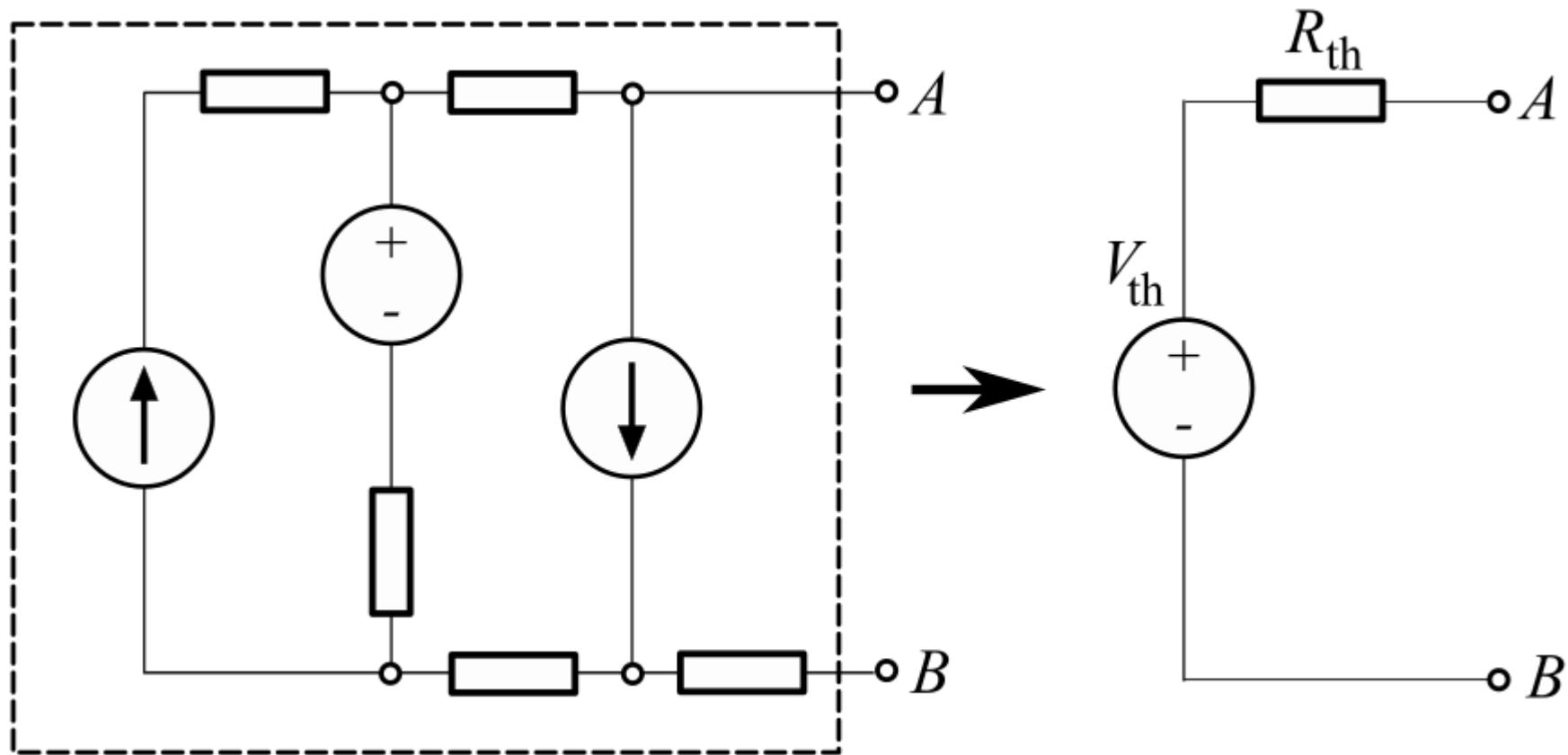Thevenin's Theorem: Any linear electrical network containing only voltage sources, current sources, and resistances can be replaced at terminals A-B by an equivalent combination of a voltage source V_{th} in a series connection with a resistance R_{th} .




Thevenin Equivalent: Rules

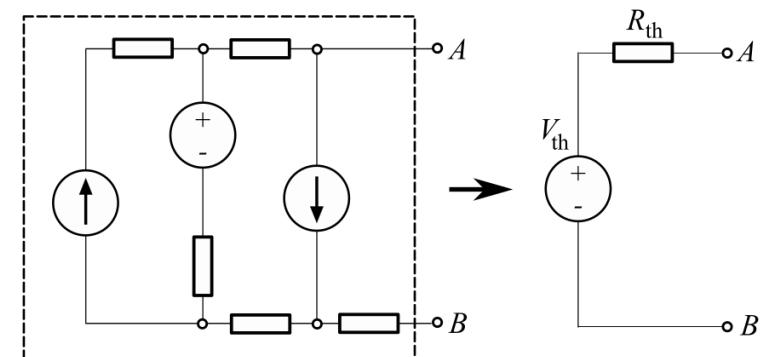
1. The equivalent voltage V_{th} is the voltage you'd get across terminals A-B
2. The equivalent resistance R_{th} is the resistance that the circuit would have across A-B if we replace voltage sources with short circuits and current sources with open circuits
3. If terminals A and B of the Thevenin equivalent circuit are connect to each other, the current flowing would be V_{th}/R_{th}



Thevenin Equivalent: Example 1

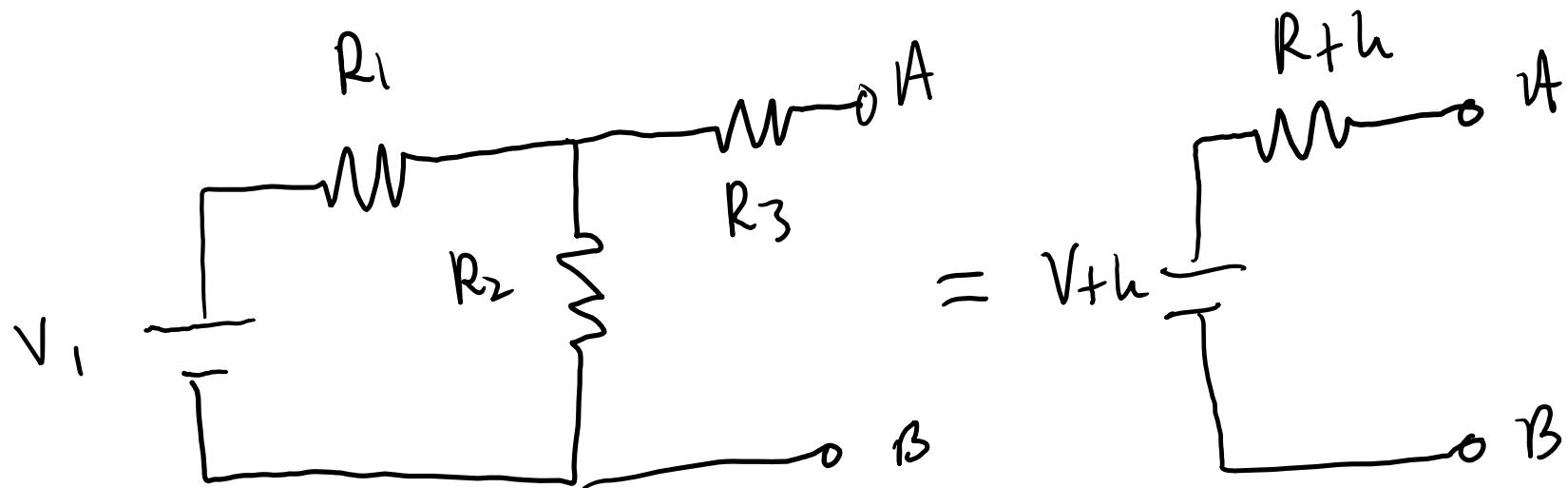


Thevenin Equivalent: Example 1

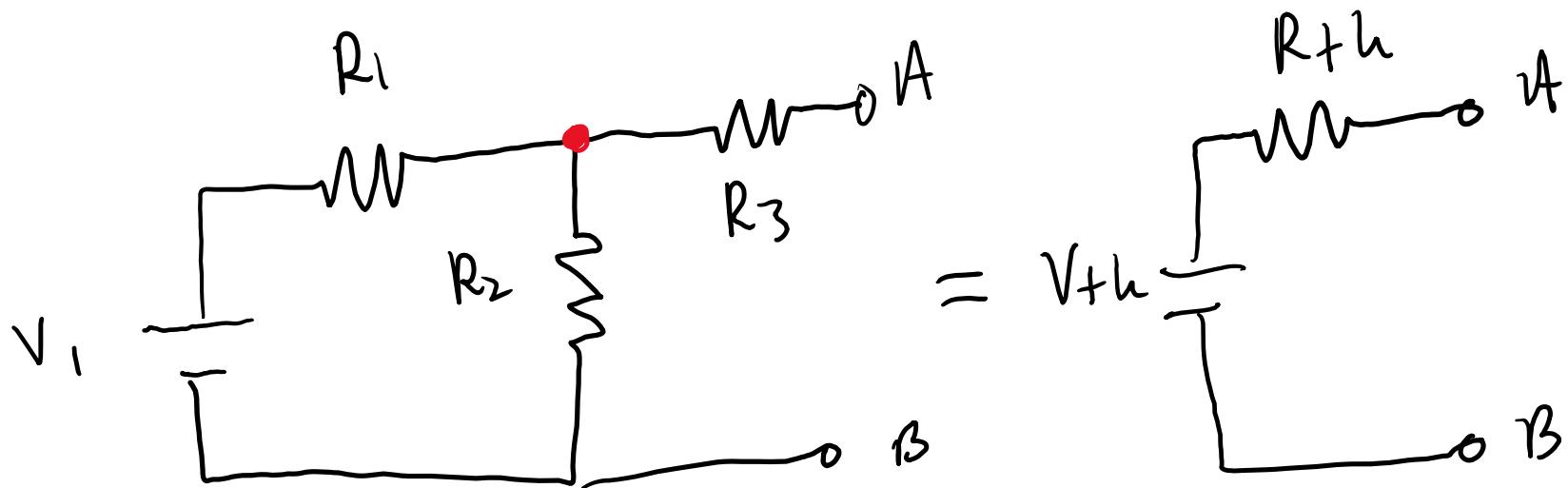

$$\frac{V_1 - V_A}{R_1} = \frac{V_A}{R_2} \rightarrow \frac{V_1}{R_1} = \frac{V_A}{R_2} + \frac{V_A}{R_1}$$


Thevenin Equivalent: Example 1

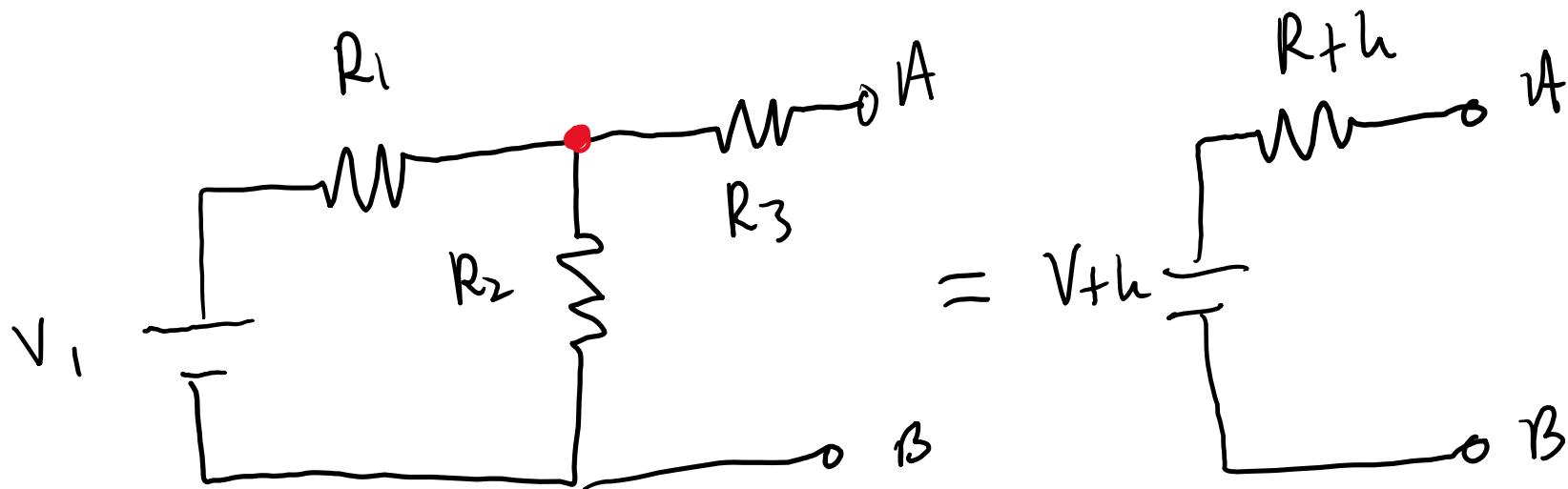


$$\frac{V_1 - V_A}{R_1} = \frac{V_A}{R_2} \rightarrow \frac{V_1}{R_1} = \frac{V_A}{R_2} + \frac{V_A}{R_1}$$

$$\rightarrow \frac{V_1}{R_1} \cdot \left(\frac{R_2 R_1}{R_1 + R_2} \right) = V_A \rightarrow \underline{\underline{V_A = V_{th} = \frac{V_1 R_2}{R_1 + R_2}}}$$

Thevenin Equivalent: Example 1

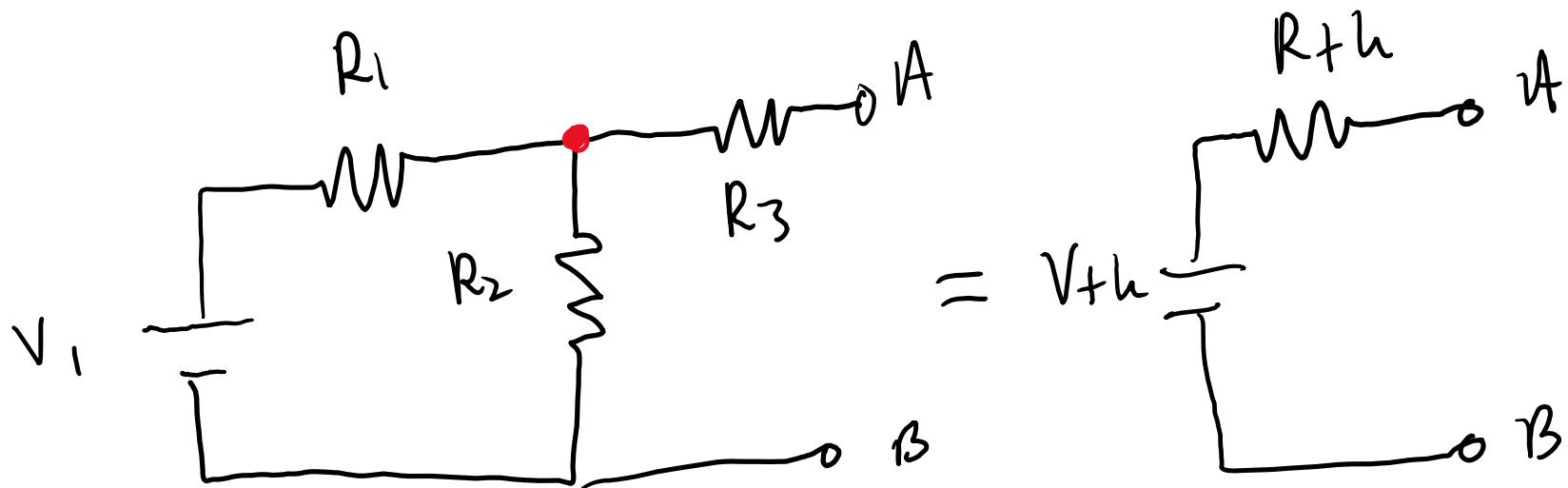


↓ set $V_1 = \text{short}$

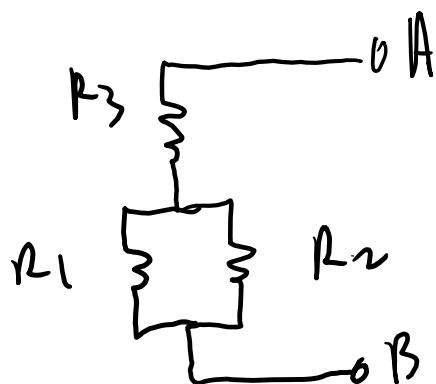


$$R_{Th} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$


Thevenin Equivalent Example 2

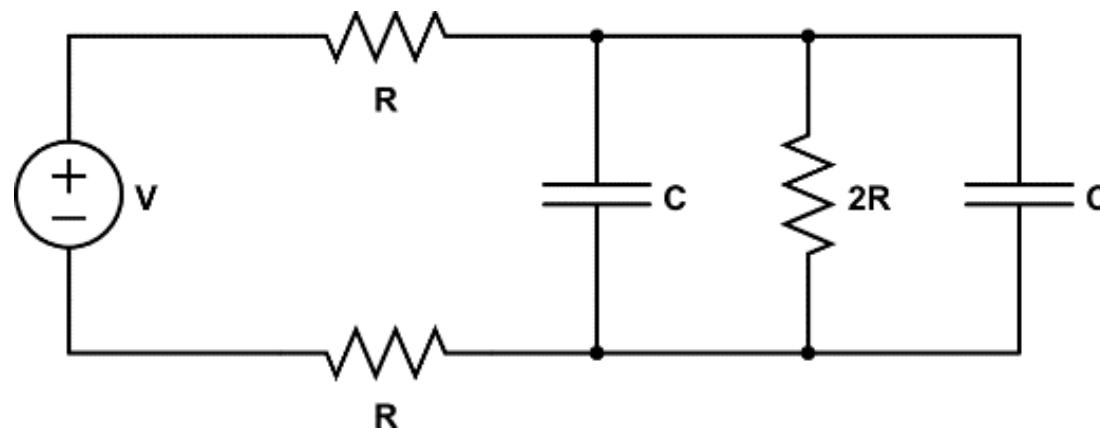


Thevenin Equivalent Example 2

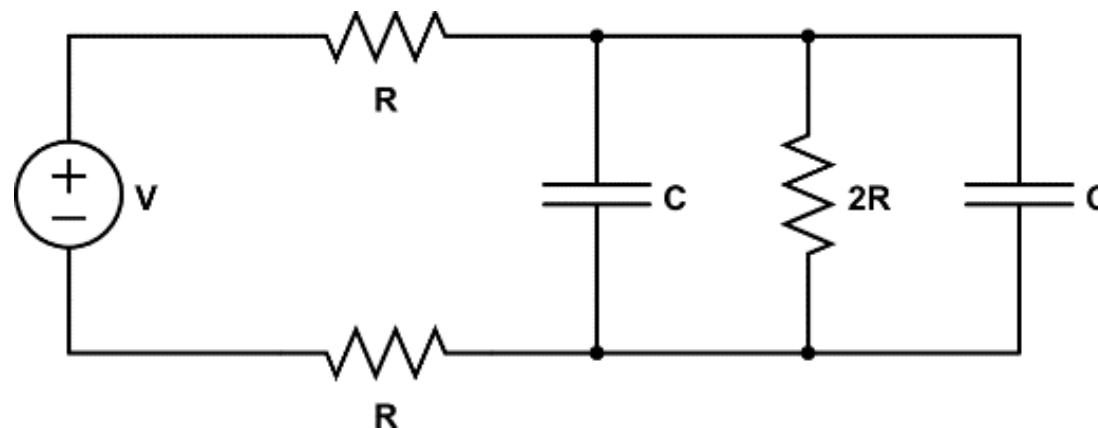


Rewrite:

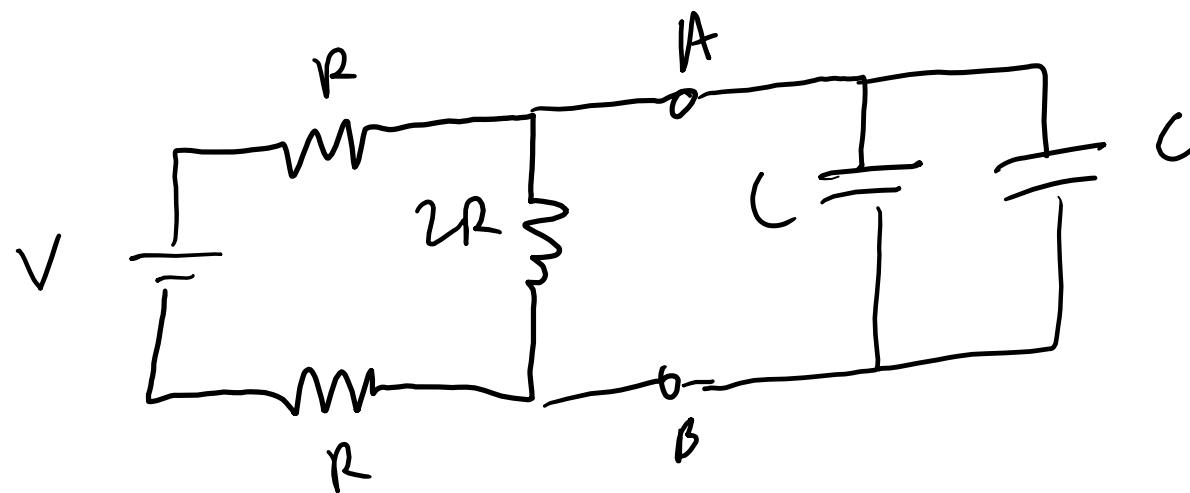

Thevenin Equivalent Example 2

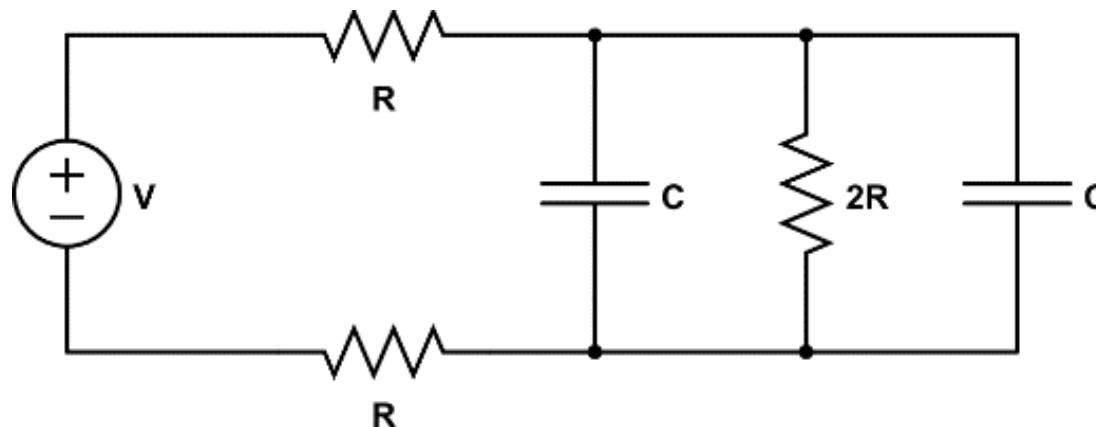


Rewrite:

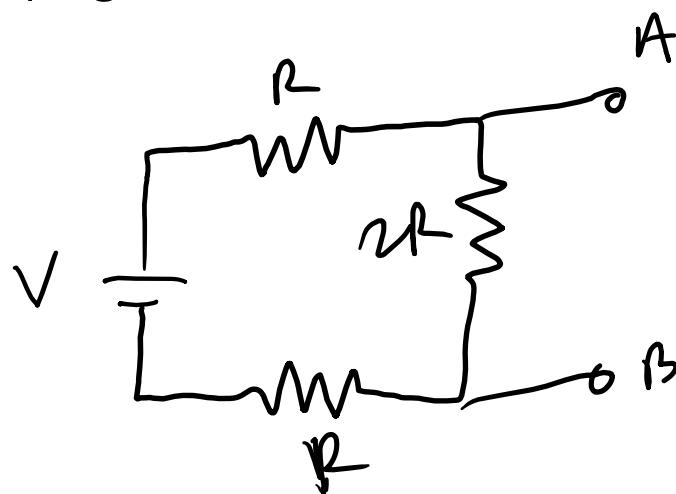

$$V = IR \rightarrow i = \frac{V}{4R}$$


$$\underline{\underline{V_{AB} = V_{Th} = \frac{V}{4R} - 2R = \frac{V}{2}}}$$

Thevenin Equivalent Example 2

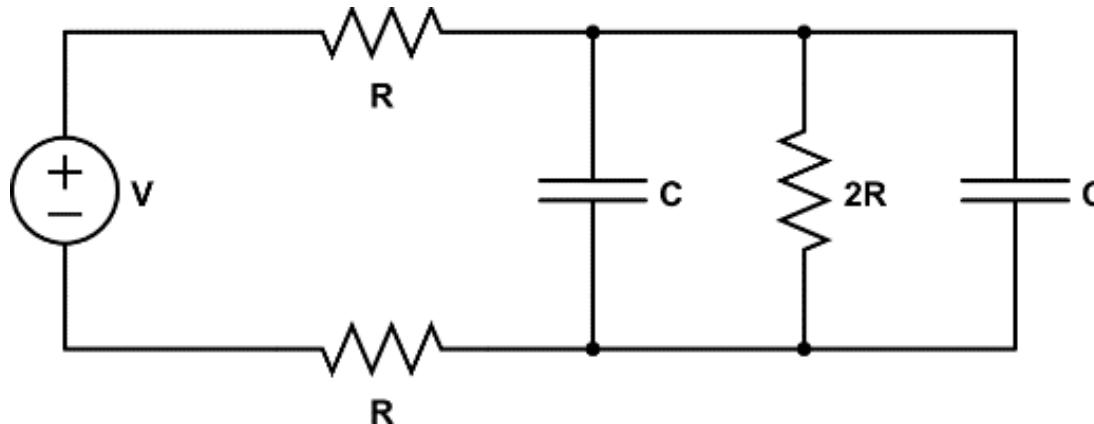

Rewrite -

$$V = IR \rightarrow i = \frac{V}{4R}$$

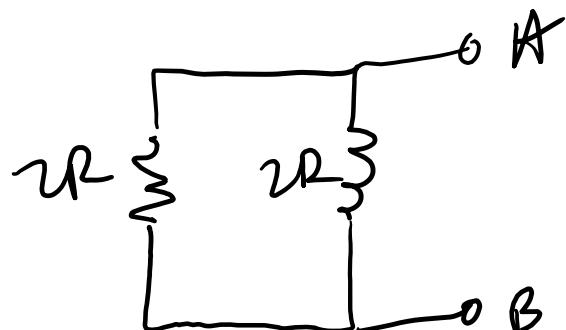

$$V_{AB} = V_{Th} = \frac{V}{4R} - 2R = \frac{V}{2}$$

$$R_{Th} = \frac{2R \cdot 2R}{2R + 2R} = \frac{4R^2}{4R} = R.$$

$$\left(\frac{1}{R_{Th}} = \frac{1}{2R} + \frac{1}{2R} \right)$$


End of the KCL/KVL and Thevenin Review

Review: Storage Elements

Capacitor

Element law: $i(t) = C \frac{dv(t)}{dt}$

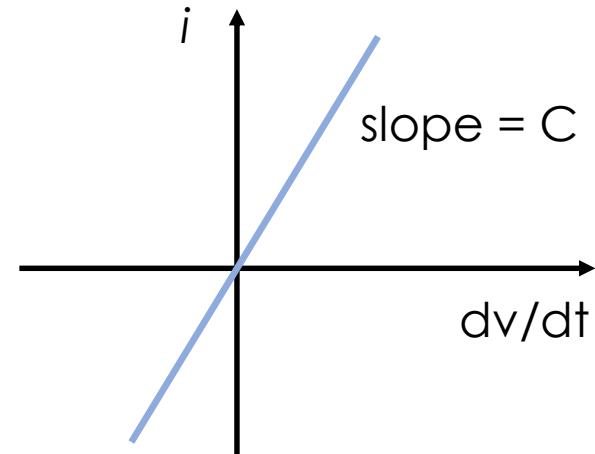
Stored energy: $w_E(t) = \frac{Cv(t)^2}{2}$



Inductor

Element law: $v(t) = L \frac{di(t)}{dt}$

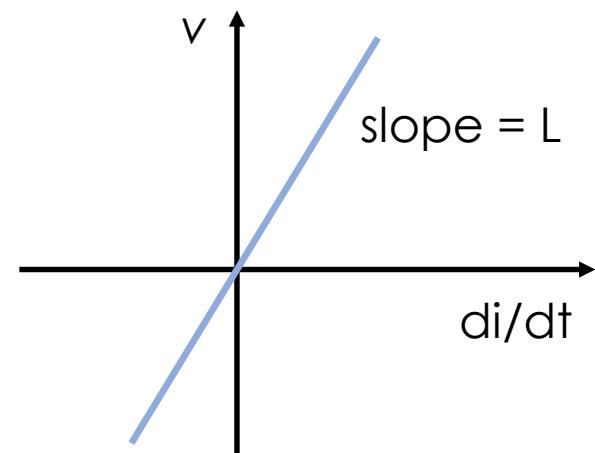
Stored energy: $w_M(t) = \frac{Li(t)^2}{2}$



RULE OF THUMB:

$$\begin{array}{ccc} C & \longleftrightarrow & L \\ v(t) & \longleftrightarrow & i(t) \end{array}$$

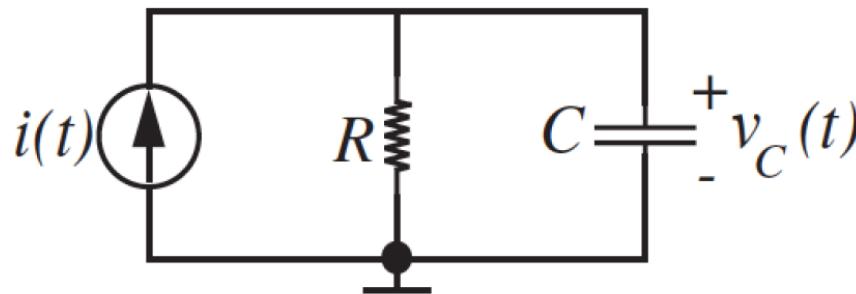Review: Simple RC Circuit – Step Response (I_0)




- Find $v_c(t)$ when the circuit is driven by $i(t) = I_0 f(t) = \begin{cases} 0, t < 0 \\ I_0, t \geq 0 \end{cases}$
- Initial condition: $v_c(t < 0) = 0$ (circuit initially uncharged and at rest)


Solution Steps

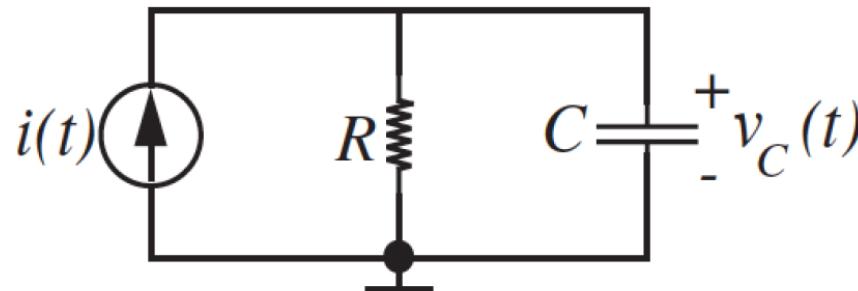1. Use node method to find the differential equation describing v_c
2. Find the homogeneous solution v_{ch} (set the drive to zero)
3. Find the particular solution v_{cp} (educated guess)
4. The total solution is the sum of the homogeneous and particular solutions. Use the initial conditions to solve for the constants.


Review: Simple RC Circuit – Step Response (I_0)



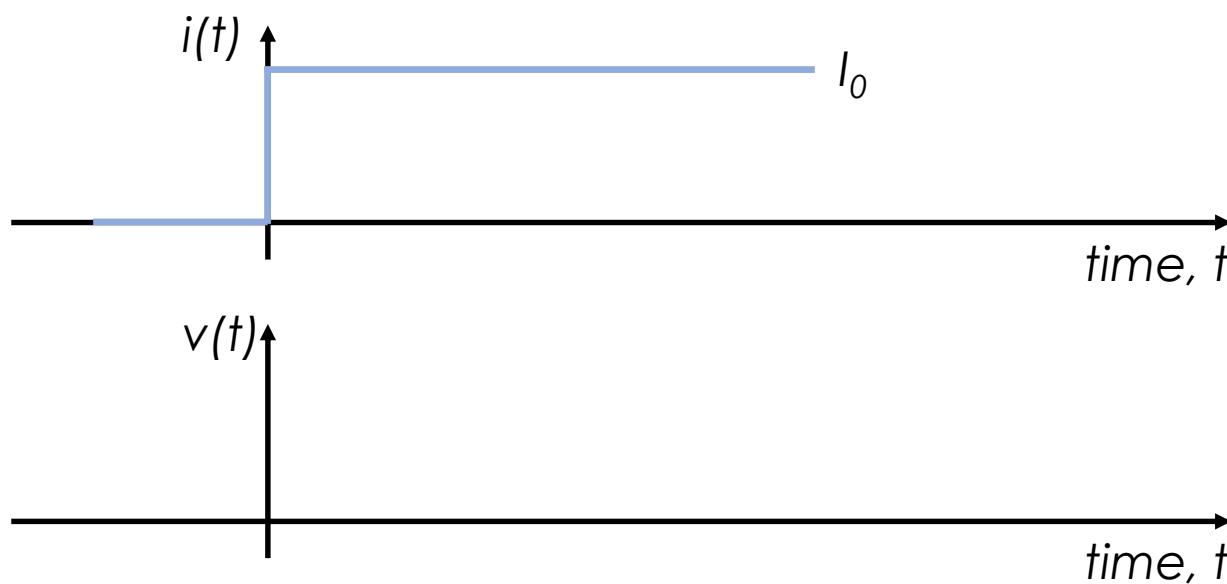
- Find $v_C(t)$ when the circuit is driven by $i(t) = I_0 f(t) = \begin{cases} 0, t < 0 \\ I_0, t \geq 0 \end{cases}$
- Initial condition: $v_C(t < 0) = 0$ (circuit initially uncharged and at rest)



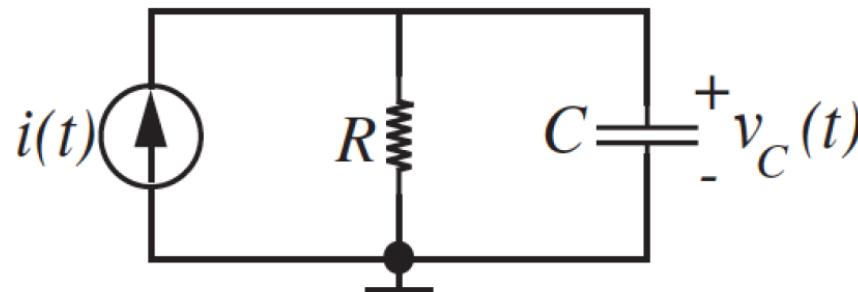
Review: Simple RC Circuit – Step Response (I_0)



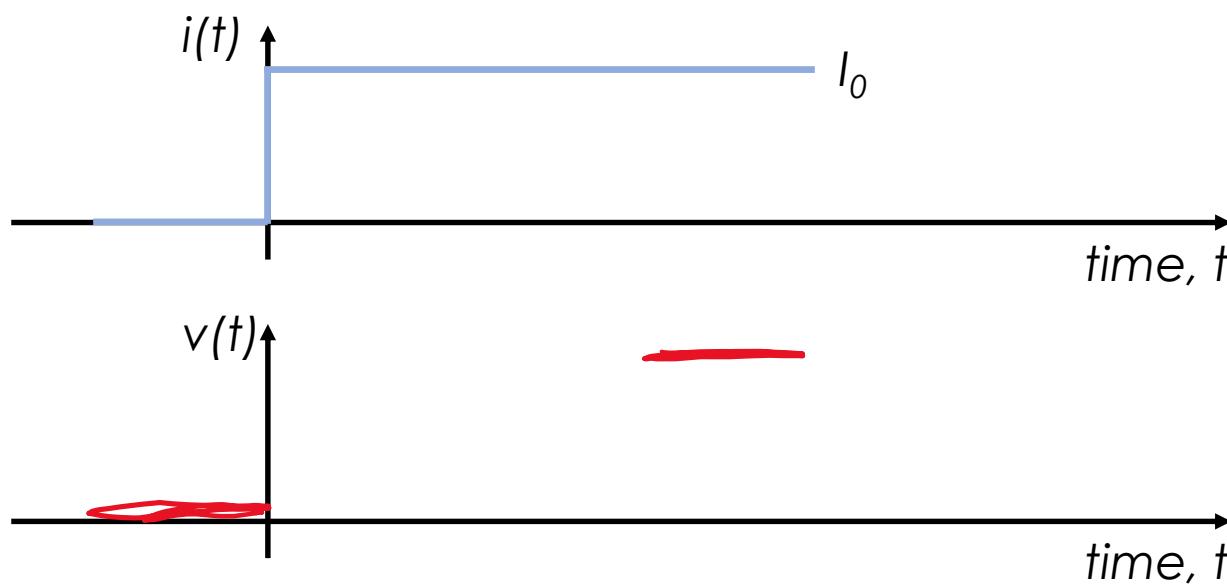
- Find $v_C(t)$ when the circuit is driven by $i(t) = I_0 f(t) = \begin{cases} 0, t < 0 \\ I_0, t \geq 0 \end{cases}$
- Initial condition: $v_C(t < 0) = 0$ (circuit initially uncharged and at rest)



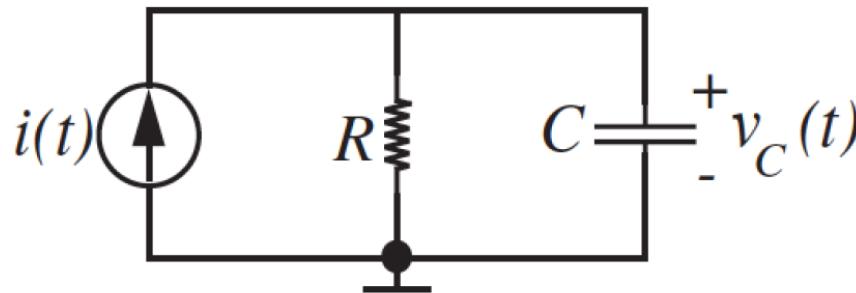
Review: Simple RC Circuit – Step Response (I_0)



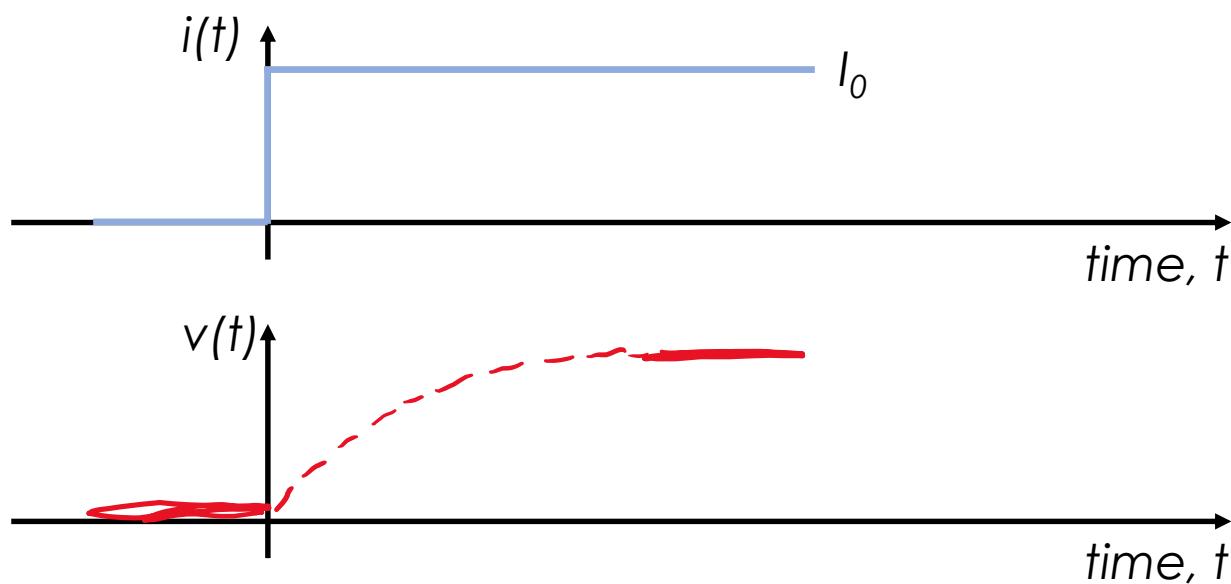- Find $v_C(t)$ when the circuit is driven by $i(t) = I_0 f(t) = \begin{cases} 0, t < 0 \\ I_0, t \geq 0 \end{cases}$
- Initial condition: $v_C(t < 0) = 0$ (circuit initially uncharged and at rest)




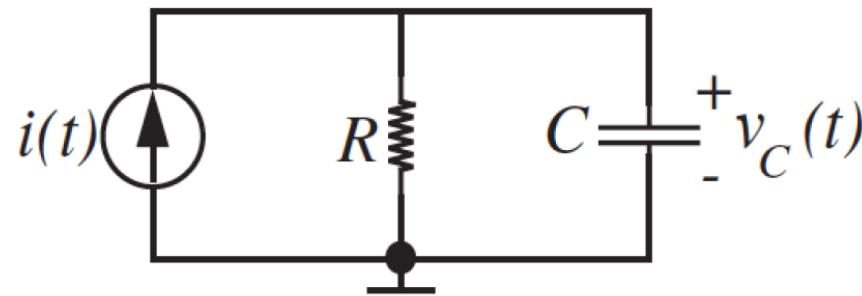Review: Simple RC Circuit – Step Response (I_0)



Review: Simple RC Circuit – Step Response (I_0)

$$\dot{i}_1 = \dot{i}_2 + \dot{i}_3$$

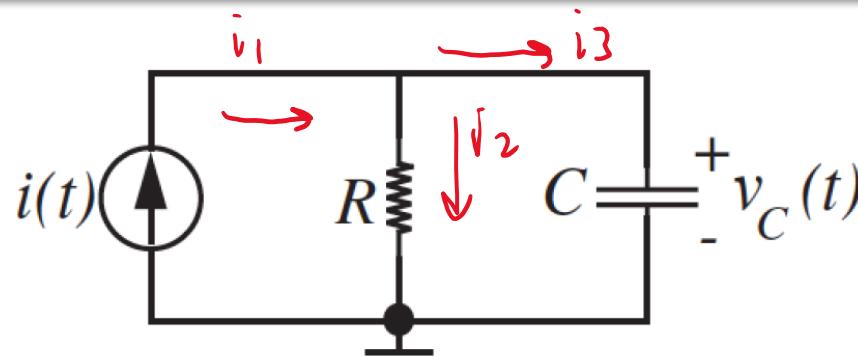


$$\dot{i}_c = C \frac{dV_c}{dt}$$

$$\dot{i}_2 = \frac{V_c}{R}$$

Review: Simple RC Circuit – Step Response (I_0)

$$\dot{i}_1 = \dot{i}_2 + \dot{i}_3$$

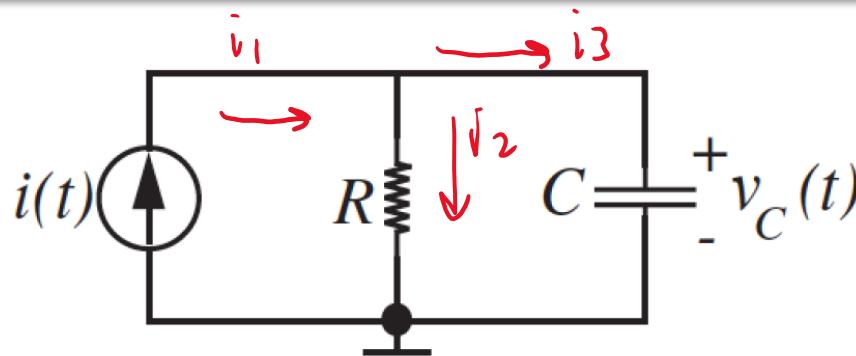

$$\dot{i}_c = C \frac{dV_c}{dt}$$


$$i_2 = \frac{V_c}{R}$$

- From node method/KCL:

$$\dot{i}(+) = \frac{V_c}{R} + C \frac{dV_c}{dt} \quad (1^{\text{st}} \text{ order ODE})$$

Review: Simple RC Circuit – Step Response (I_0)

$$\dot{i}_1 = i_2 + i_3$$

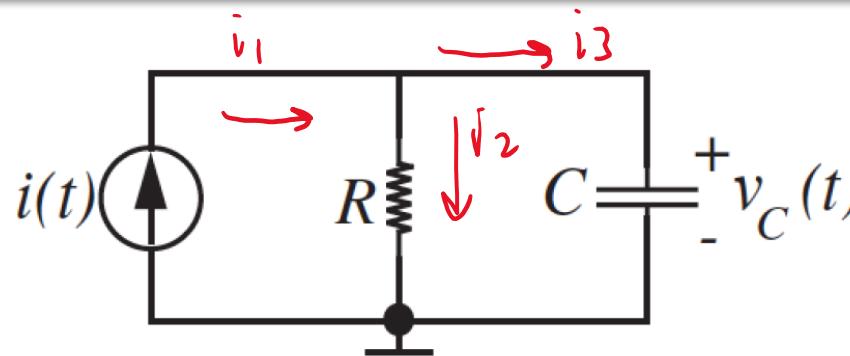

$$\dot{i}_c = C \frac{dV_c}{dt}$$

$$i_2 = \frac{V_c}{R}$$

- From node method/KCL:

$$\dot{i}(+) = \frac{V_c}{R} + C \frac{dV_c}{dt} \quad (1^{\text{st}} \text{ order ODE})$$

- To find the homogeneous solution, set the drive $i(t) = 0$

$$\dot{v} = \frac{V_c}{R} + C \frac{dV_c}{dt}$$

The homogeneous solution to any constant coefficient ODE is a superposition of functions of the form Ae^{st} (with a caveat*)

* unless the characteristic equation has repeated roots

Review: Simple RC Circuit – Step Response (I_0)

- Plug $v_{ch} = Ae^{st}$ into the differential equation $0 = \frac{v_{ch}}{R} + C \frac{dv_{ch}}{dt}$
- **Characteristic equation:** $\cancel{0} = \frac{Ae^{st}}{R} + CS A e^{st} \Rightarrow s = -\frac{1}{RC}$

The characteristic equation of an n^{th} degree differential equation is a polynomial of n^{th} degree. We know that an n^{th} degree polynomial will have n roots (including repeated roots or complex roots)


Review: Simple RC Circuit – Step Response (I_0)

- Plug $v_{ch} = Ae^{st}$ into the differential equation $0 = \frac{v_{ch}}{R} + C \frac{dv_{ch}}{dt}$
- **Characteristic equation:** $\cancel{0} = \frac{Ae^{st}}{R} + CS A e^{st} \Rightarrow s = -\frac{1}{RC}$

The characteristic equation of an n^{th} degree differential equation is a polynomial of n^{th} degree. We know that an n^{th} degree polynomial will have n roots (including repeated roots or complex roots)

- $s \equiv$ root of characteristic equation, also = “natural frequency” (Chpt 12)
- **Homogeneous Solution:** $V_{ch}(t) = Ae^{-t/RC}$
- Natural response of the circuit (only depends on internal components)
- **RC dimensions = time and is called the time constant of the circuit**
- We’ll find A after solving for the particular solution

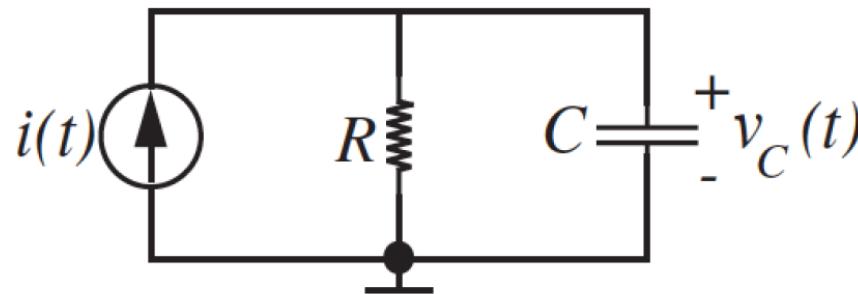
Review: Simple RC Circuit – Step Response (I_0)



- The particular solution satisfies the original equation but doesn't need to satisfy the initial conditions:

$$I_0 = \frac{v_{cp}}{R} + C \frac{dv_{cp}}{dt}$$

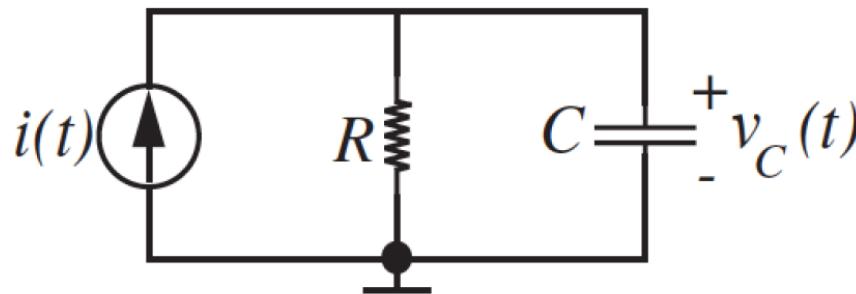Review: Simple RC Circuit – Step Response (I_0)




- The particular solution satisfies the original equation but doesn't need to satisfy the initial conditions:

$$I_0 = \frac{v_{cp}}{R} + C \frac{dv_{cp}}{dt}$$

$$K = I_0 R$$

- Since source is constant for $t > 0$, one acceptable solution: $v_{cp} = K$

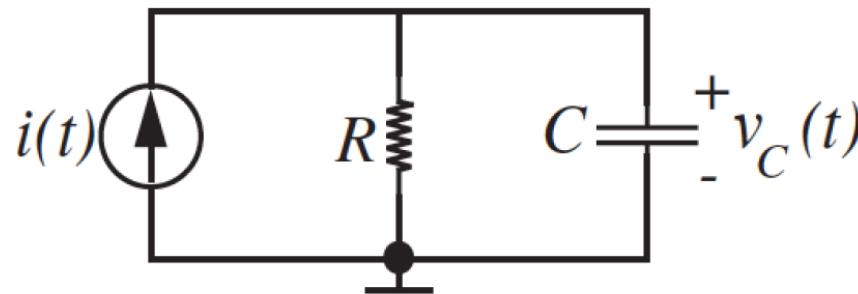Review: Simple RC Circuit – Step Response (I_0)




- The particular solution satisfies the original equation but doesn't need to satisfy the initial conditions:

$$I_0 = \frac{v_{cp}}{R} + C \frac{dv_{cp}}{dt} \quad K = I_0 R$$


- Since source is constant for $t > 0$, one acceptable solution: $v_{cp} = K$
- Total solution? $v_{ch} + v_{cp}$ $v(t) = I_0 R + A e^{-t/RC}$
- Initial condition $v_c = 0$ for $t = 0$ allows us to find unknown constant A

$$A = -I_0 R \Rightarrow v(t) = I_0 R - I_0 R e^{-t/RC}$$

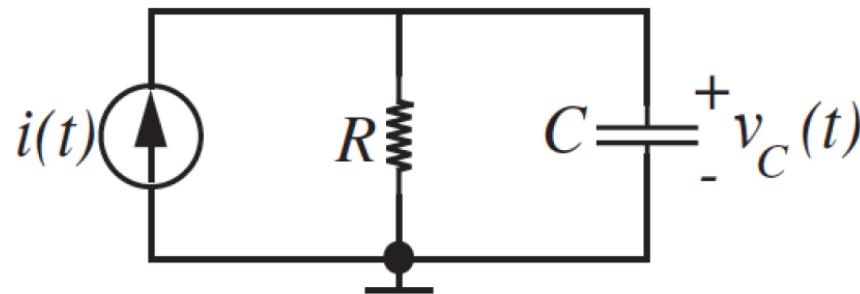
Review: Simple RC Circuit – Step Response (I_0)



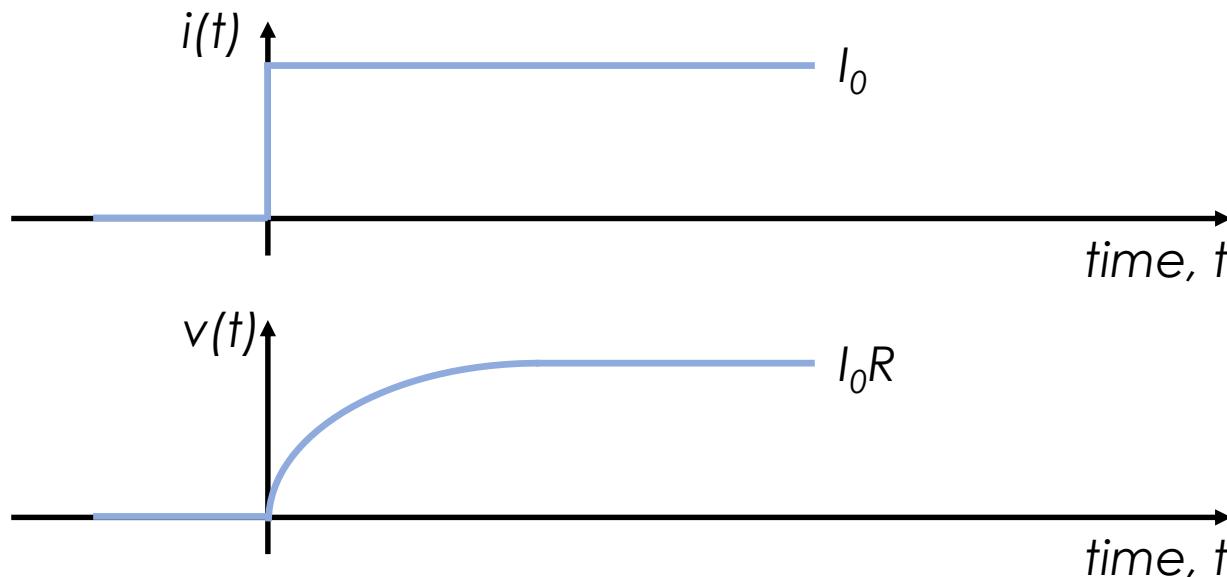
$$v_c(t) = -I_0 R e^{-\frac{t}{RC}} + I_0 R$$



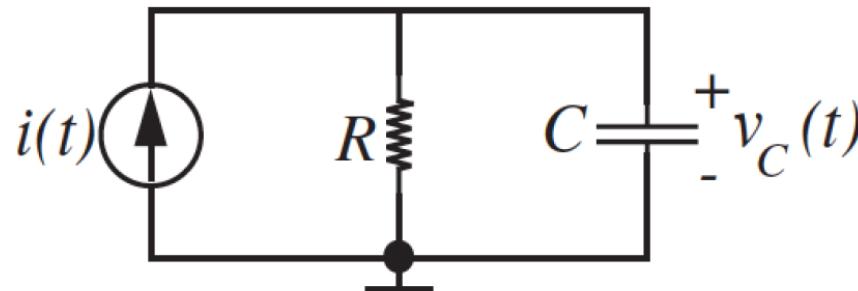
Review: Simple RC Circuit – Discharge Transient



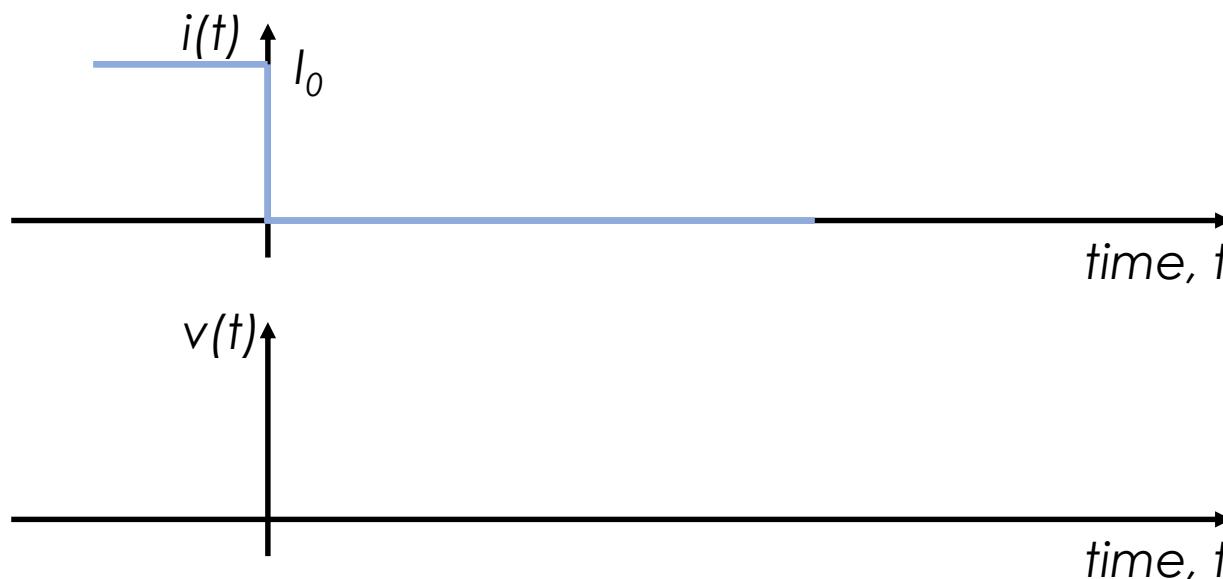
- Find $v_c(t)$ when the circuit is driven by $i(t) = I_0 f(t) = \begin{cases} I_0, t < 0 \\ 0, t \geq 0 \end{cases}$
- Initial condition: $v_c(t < 0) = I_0 R$ (capacitor initially charged)



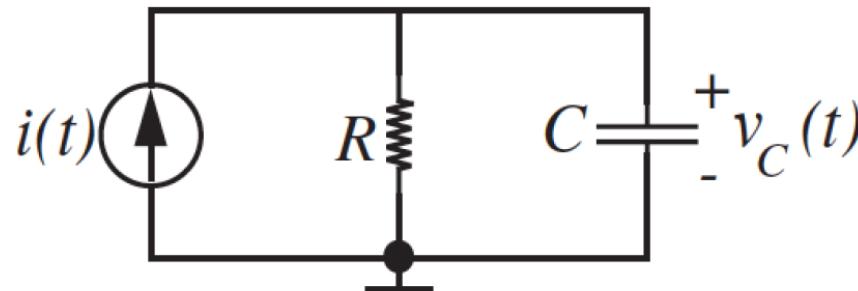
Review: Simple RC Circuit – Discharge Transient



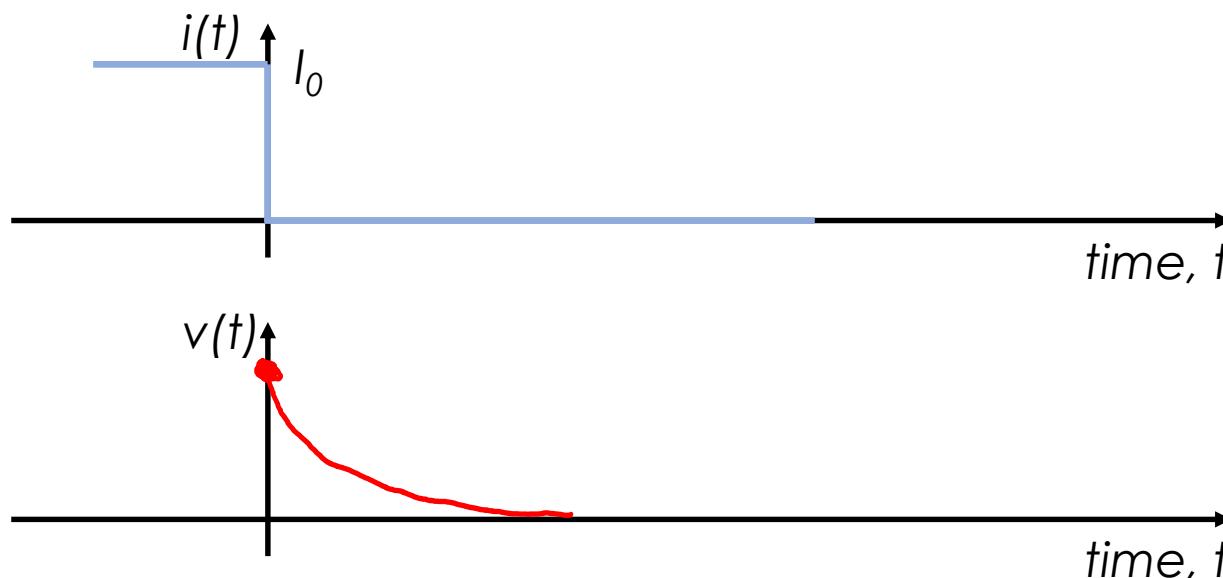- Find $v_c(t)$ when the circuit is driven by $i(t) = I_0 f(t) = \begin{cases} I_0, t < 0 \\ 0, t \geq 0 \end{cases}$
- Initial condition: $v_c(t < 0) = I_0 R$ (capacitor initially charged)



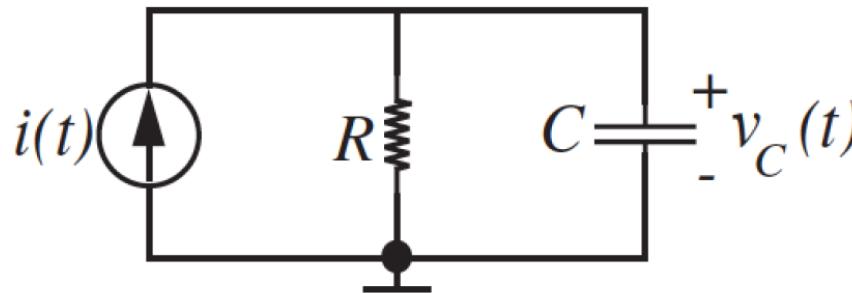Review: Simple RC Circuit – Discharge Transient



- Find $v_c(t)$ when the circuit is driven by $i(t) = I_0 f(t) = \begin{cases} I_0, t < 0 \\ 0, t \geq 0 \end{cases}$
- Initial condition: $v_c(t < 0) = I_0 R$ (capacitor initially charged)

$$i(t) = \frac{v_c}{R} + C \frac{dv_c}{dt}$$

Homogeneous solution same as before.

Without source, no particular solution.


Thus $v_{ch} = v_c$.

$$v_{ch} = Ae^{-t/RC} = v_c$$


$$I_0 R = Ae^{-0/RC}$$

Using initial condition, determine A to get: $v_c = I_0 Re^{-t/RC}$

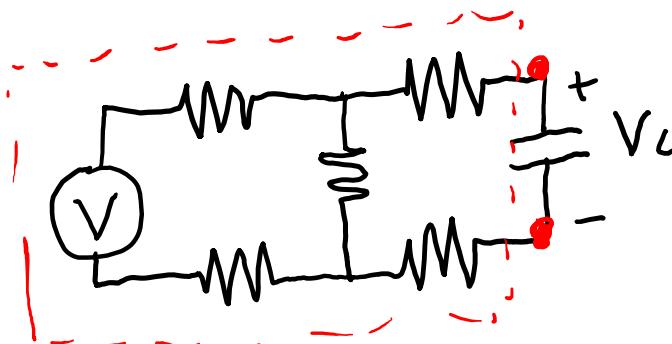Review: Let's Add Some Resistors to our RC Circuit




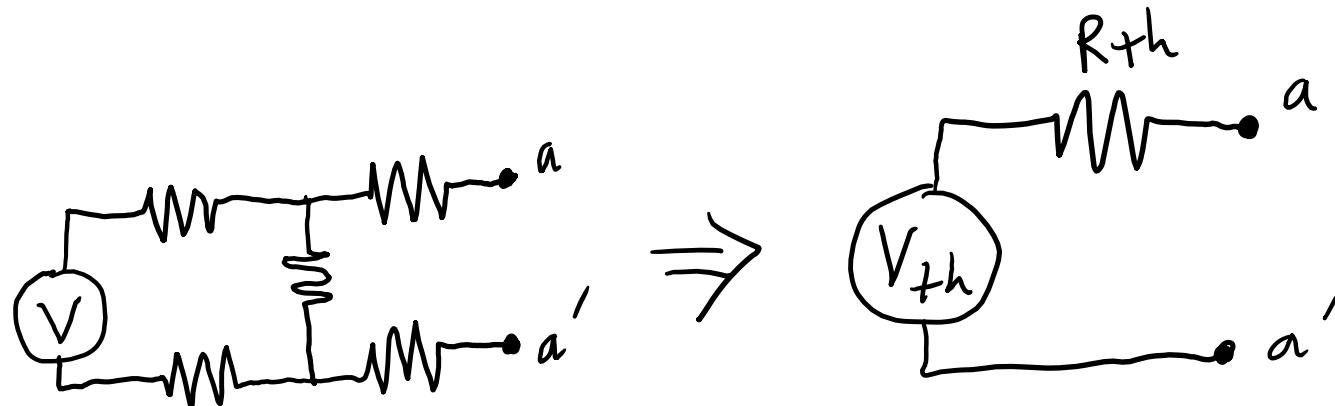How do we determine the transient behavior?




Determine the Thevenin equivalent circuit

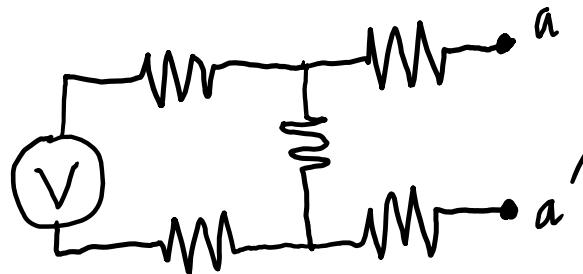Review: Let's Add Some Resistors to our RC Circuit



Determine the Thevenin equivalent circuit

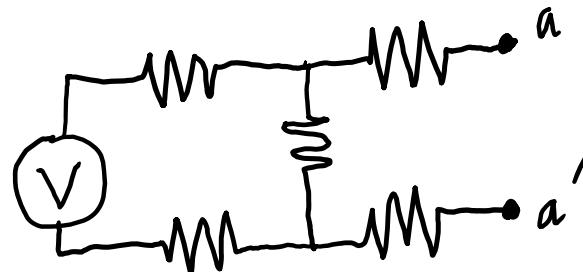Review: Let's Add Some Resistors to our RC Circuit




Determine the Thevenin equivalent circuit

$$V_{th} = \frac{V}{3}$$


from inspection

$$2R//R + R + R \\ = R_{th}$$

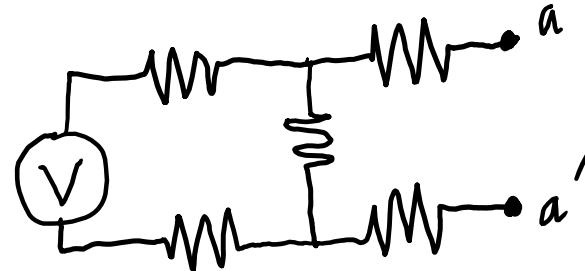Review: Let's Add Some Resistors to our RC Circuit



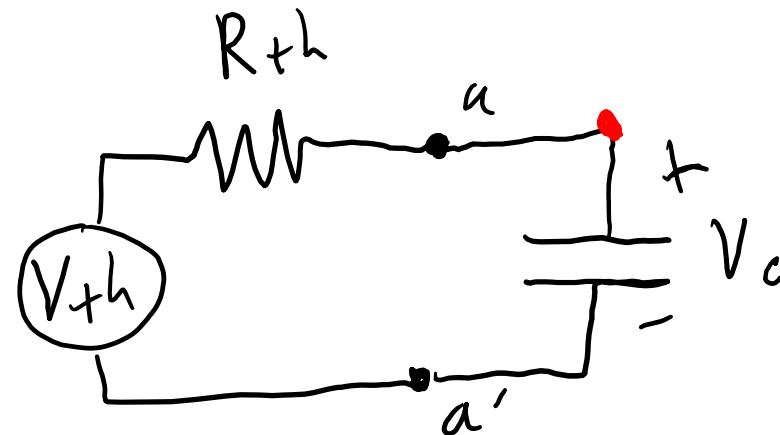Determine the Thevenin equivalent circuit



$$V_{th} = \frac{V}{3}$$

$$R_{th} = 2R // R + 2R$$

ECE 10C
Fall 2020
Slide Set 1
Instructor: Galan Moody
TA: Kamyar Parto

REMEMBER: WITH GREAT
POWER COMES GREAT
CURRENT SQUARED
TIMES RESISTANCE.



OHM NEVER FORGOT HIS
DYING UNCLE'S ADVICE.

Last Week

- Introduction to course

This Week

- KVL/KCL, node methods
- Thevenin
- 1st-order RC/RL circuits

Important Items:



Homework #1 posted
Due Th, Oct 15 by 5 pm

Lab #1 posted
Due Fr, Oct 16

Quiz Time!





Assume capacitors are uncharged at time $t = 0$.

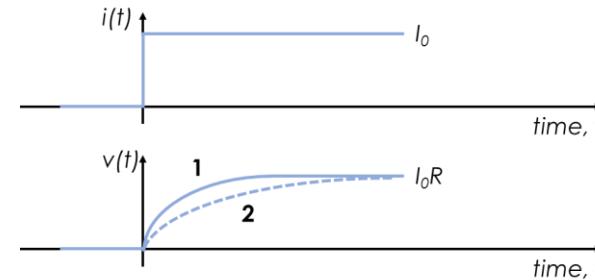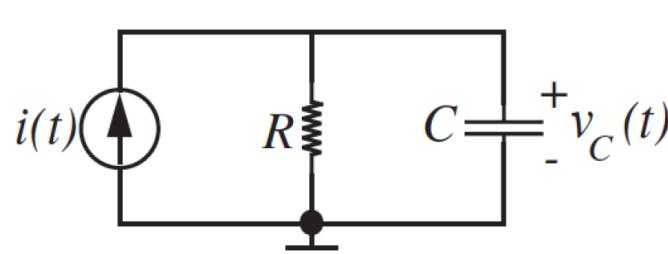Q1 [2 point]. For the parallel RC circuit shown on the left, with a constant-current step source shown on the top right, choose the answer that best describes the circuits for the capacitor voltage shown on the bottom right. Curves 1 and 2 correspond to circuits with R_1, C_1 and R_2, C_2 , but are otherwise identical.



- (a) $R_1C_1 = R_2C_2$ (b) $R_1 > R_2 \text{ & } C_1 < C_2$ (c) $R_1C_1 > R_2C_2$ (d) $C_1 < C_2$

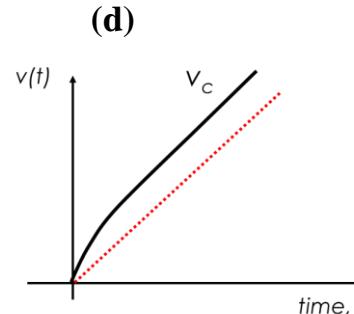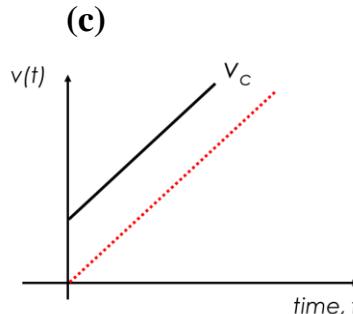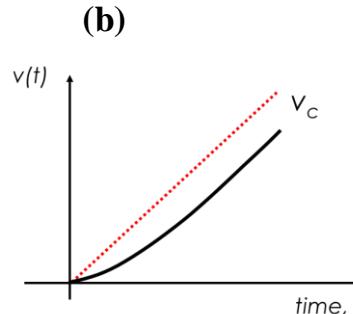
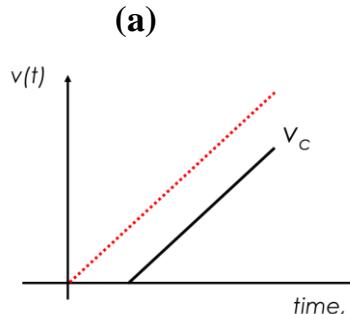
Q2 [3 points]. (a) For an RC series circuit with a linear voltage ramp starting at 0V, choose the correct capacitor voltage.



Quiz Time!


Assume capacitors are uncharged at time $t = 0$.

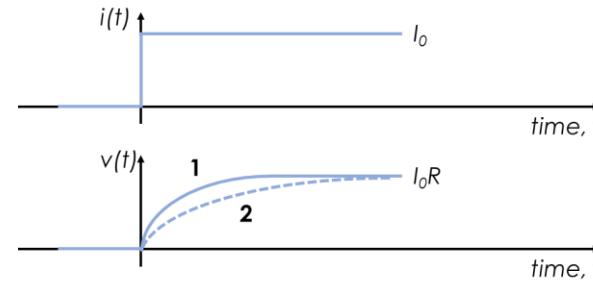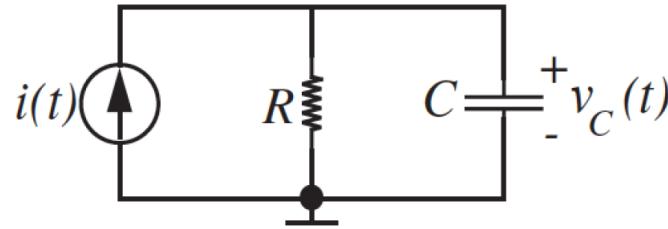Q1 [2 point]. For the parallel RC circuit shown on the left, with a constant-current step source shown on the top right, choose the answer that best describes the circuits for the capacitor voltage shown on the bottom right. Curves 1 and 2 correspond to circuits with R_1, C_1 and R_2, C_2 , but are otherwise identical.



- (a) $R_1C_1 = R_2C_2$ (b) $R_1 > R_2 \text{ & } C_1 < C_2$ (c) $R_1C_1 > R_2C_2$ (d) $C_1 < C_2$

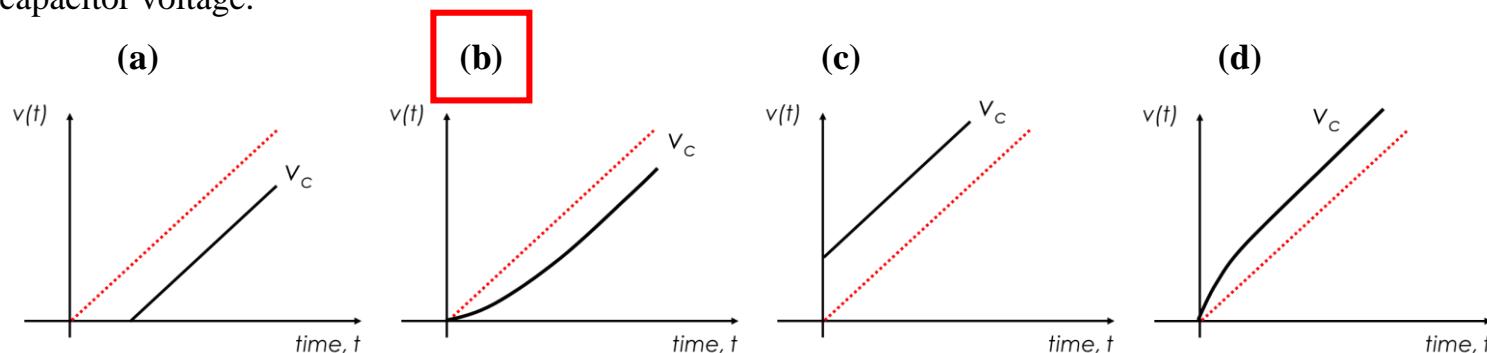
Q2 [3 points]. (a) For an RC series circuit with a linear voltage ramp starting at 0V, choose the correct capacitor voltage.



Quiz Time!


Q1 [1 point]. True or False? An inductor stores energy in its magnetic field and reacts to the change in current.

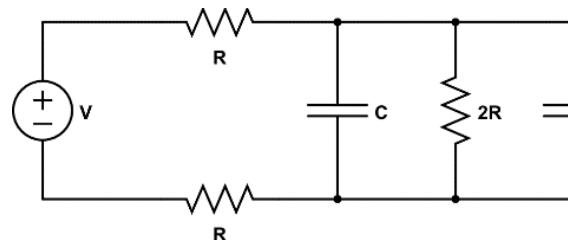Q2 [2 point]. Pick the correct Thevenin voltage and resistance as would be seen across the two capacitors.



- (a) $V_{th} = V/2$, $R_{th} = 2R$
- (b) $V_{th} = V$, $R_{th} = R$
- (c) $V_{th} = V/2$, $R_{th} = R$

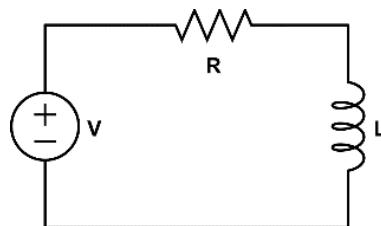Q3 [2 points]. For a step voltage response from $V = 0$ to $V = V_0$, choose the correct statements for the RL circuit below. Assume the system had been at “rest” for a long time.




At the instance $V = V_0$:

- (a) The current through L is zero.
- (b) The current through L is not zero.

At long times (steady-state):

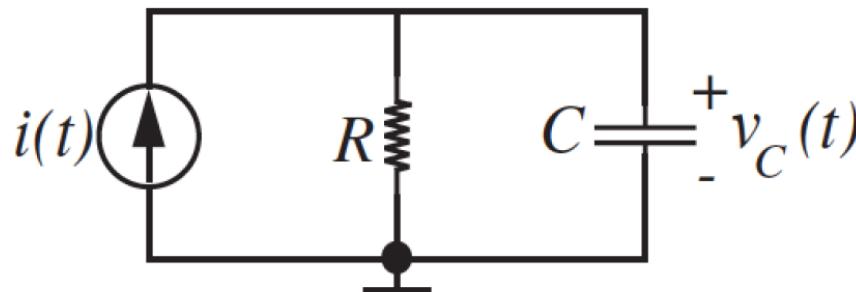- (a) The voltage across L is not zero.
- (b) The voltage across L is zero.

Review: Simple RC Circuit – Step Response (I_0)




- Find $v_c(t)$ when the circuit is driven by $i(t) = I_0 f(t) = \begin{cases} 0, t < 0 \\ I_0, t \geq 0 \end{cases}$
- Initial condition: $v_c(t < 0) = 0$ (circuit initially uncharged and at rest)

Solution Steps

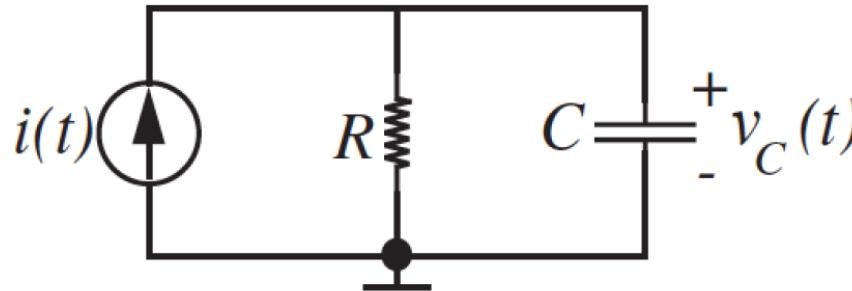1. Use node method to find the differential equation describing v_c
2. Find the homogeneous solution v_{ch} (set the drive to zero)
3. Find the particular solution v_{cp} (educated guess)
4. The total solution is the sum of the homogeneous and particular solutions. Use the initial conditions to solve for the constants.

Review: Simple RC Circuit – Discharge Transient



- Find $v_c(t)$ when the circuit is driven by $i(t) = I_0 f(t) = \begin{cases} I_0, t < 0 \\ 0, t \geq 0 \end{cases}$
- Initial condition: $v_c(t < 0) = I_0 R$ (capacitor initially charged)

$$i(t) = \frac{v_c}{R} + C \frac{dv_c}{dt}$$

Homogeneous solution same as before.

Without source, no particular solution.


Thus $v_{ch} = v_c$.

$$v_{ch} = A e^{-t/RC} = v_c$$


$$I_0 R = A e^{-0/RC}$$

Using initial condition, determine A to get: $v_c = I_0 R e^{-t/RC}$

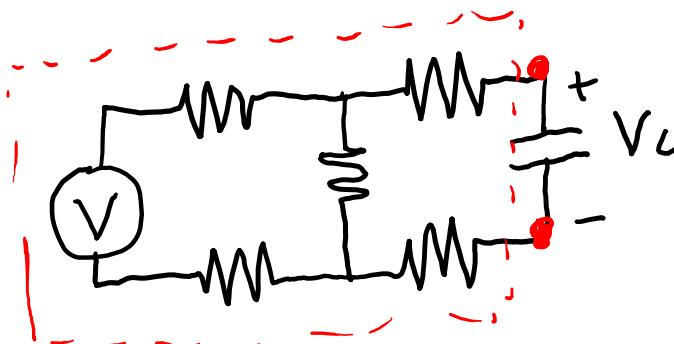Review: Let's Add Some Resistors to our RC Circuit




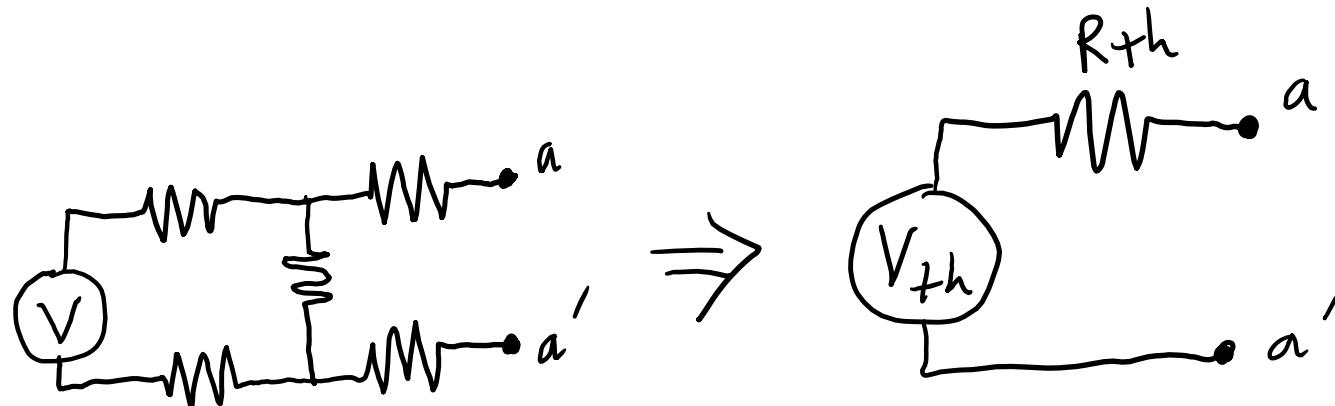How do we determine the transient behavior?




Determine the Thevenin equivalent circuit

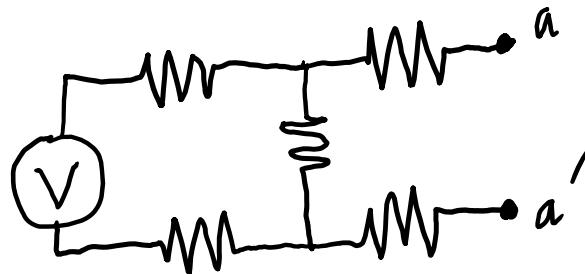Review: Let's Add Some Resistors to our RC Circuit



Determine the Thevenin equivalent circuit

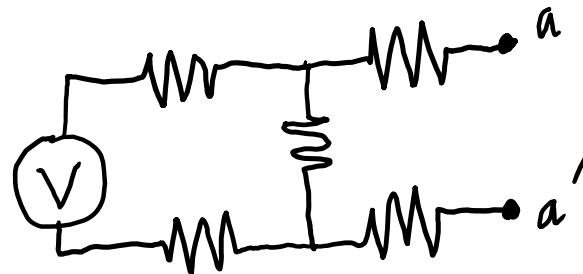Review: Let's Add Some Resistors to our RC Circuit




Determine the Thevenin equivalent circuit

$$V_{th} = \frac{V}{3}$$


from inspection

$$2R//R + R + R \\ = R_{th}$$

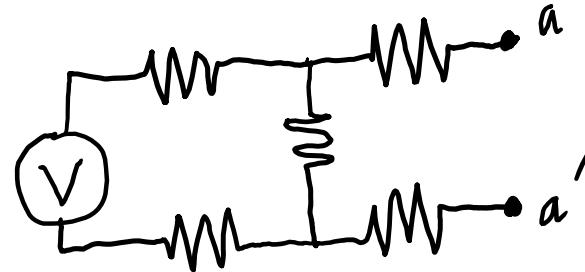Review: Let's Add Some Resistors to our RC Circuit



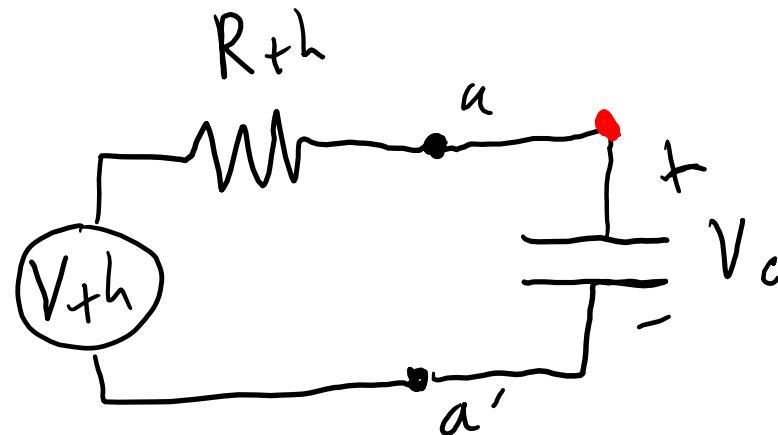
Determine the Thevenin equivalent circuit



$$V_{th} = \frac{V}{3}$$

$$R_{th} = 2R // R + 2R$$

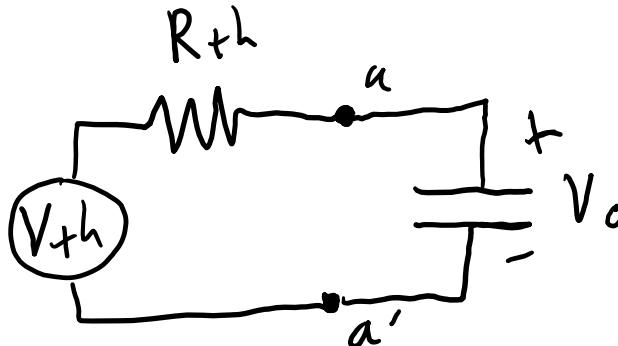Review: Let's Add Some Resistors to our RC Circuit







- Find $v_c(t)$ when the circuit is driven by $v(t) = V_0 f(t) = \begin{cases} V_0, t > 0 \\ 0, t = 0 \end{cases}$
- Initial condition: $v_c(t < 0) = 0$ (capacitor initially charged)
- Use node method: $\frac{v_{th} - v_c}{R} - C \frac{dv_c}{dt} = 0$ $v_{th} = v_c + RC \frac{dv_c}{dt}$

Recall current step response for parallel RC circuit: $I_0 = \frac{v_{cp}}{R} + C \frac{dv_{cp}}{dt}$

We have a similar expression: $v_c(t) = V_0 - V_0 e^{-\frac{t}{RC}}$

Review: RC versus RL Circuit Transient Response

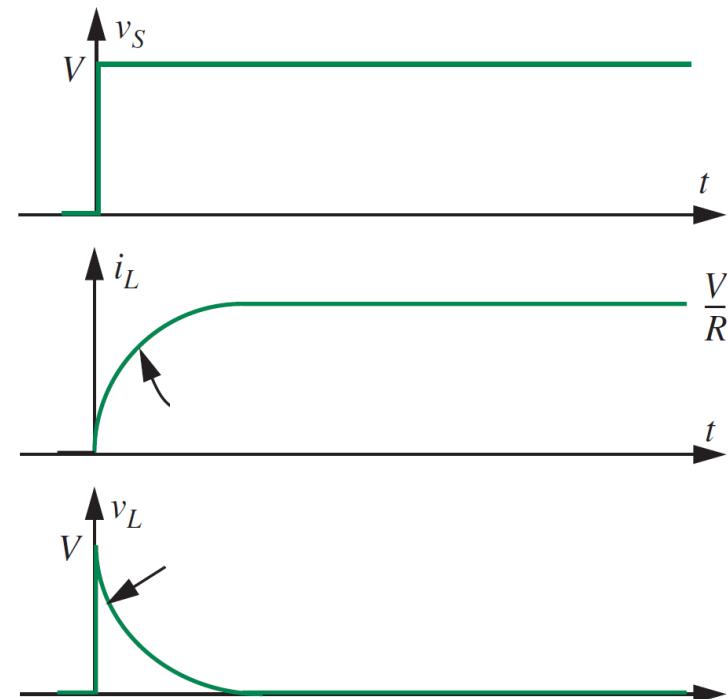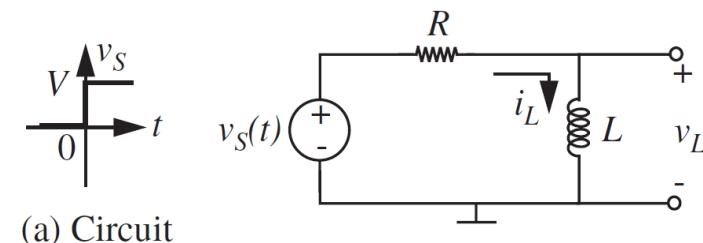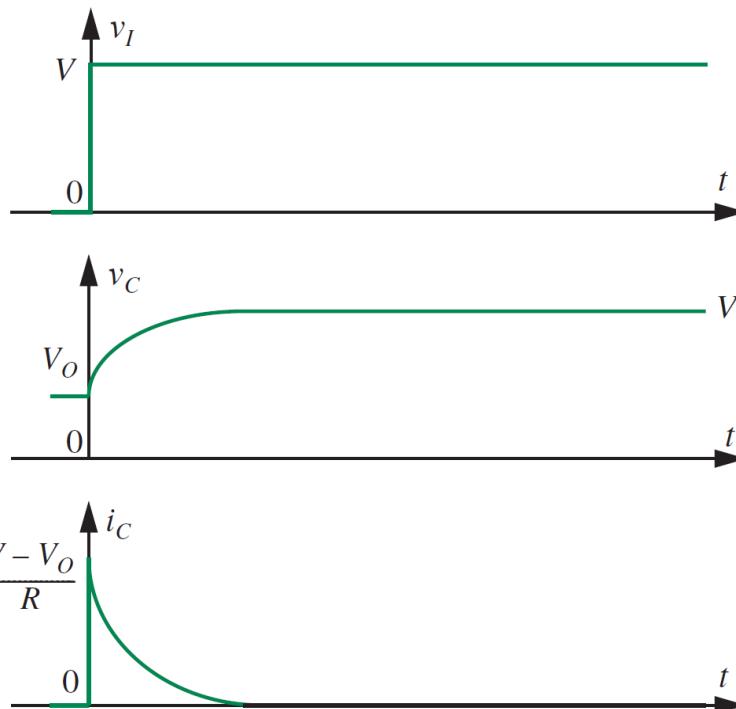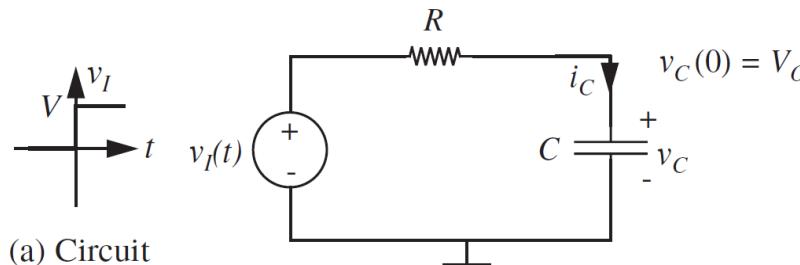The transient behavior of an inductor can be understood in a similar way to the capacitor, replacing $C \rightarrow L$ and $v \rightarrow i$



Review: RC versus RL Circuit Transient Response

Often the initial conditions aren't given. Instead, we're told that the circuit has reached a steady state before being disturbed.

Principle #1: Initial response of C and L

A capacitor acts like a short circuit and an inductor like an open circuit when they are "at rest"


Principle #2: Steady-state of C and L

A capacitor acts like an open circuit and an inductor like a short circuit when they are in their steady state

Principle #3: Continuity

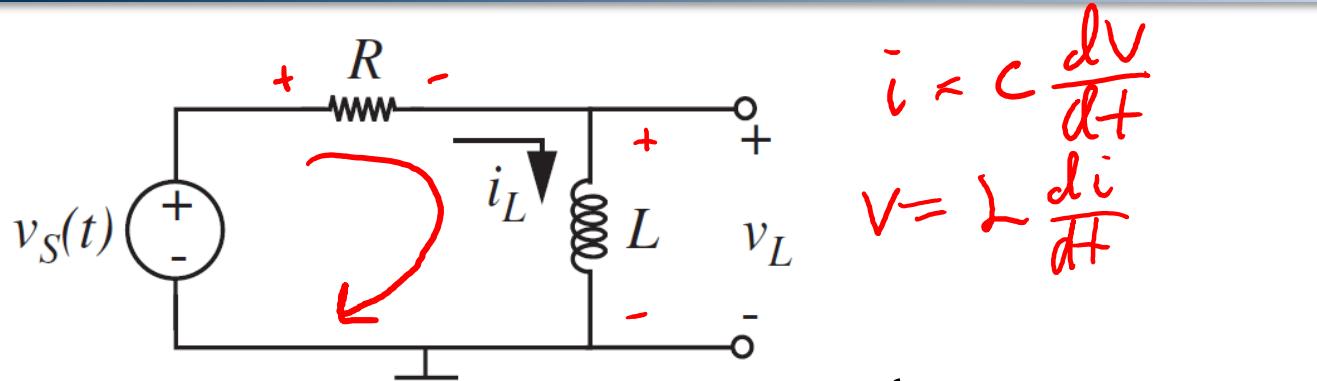
1. Voltage across C is continuous (unless an impulse current)
2. Current through L is continuous (unless impulse voltage)

Review: Simple RL Circuit – Step Response (V_0)




- Find $i_L(t)$ when the circuit is driven by $v(t) = V_0 f(t) = \begin{cases} 0, t < 0 \\ V_0, t \geq 0 \end{cases}$
- Initial condition: $i_L(t < 0) = 0$ (circuit initially uncharged and at rest)
- From KVL**: $v_S - i_L R - L \frac{di}{dt} = 0 \quad | \quad v_S = i_L R + L \frac{di}{dt}$
- Homogeneous solution: $i_L(t) = Ae^{st} \quad | \quad 0 = Ae^{st}R + LsAe^{st}$
- Characteristic equation: $s = -\frac{R}{L}$
- Homogeneous solution: $i_L(t) = Ae^{-R/L t} \quad t_c = \frac{L}{R}$

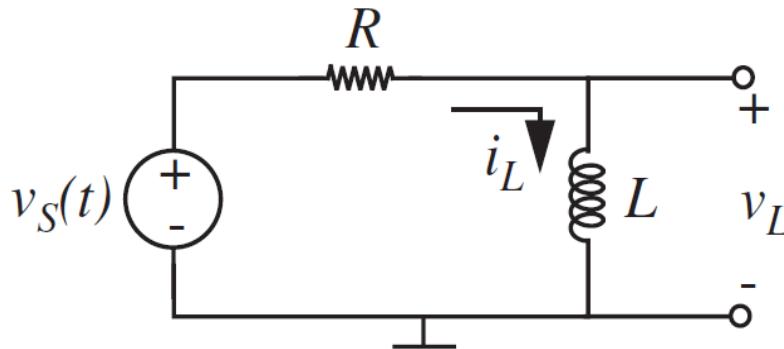Review: Simple RL Circuit – Step Response (V_0)



- Find $i_L(t)$ when the circuit is driven by $v(t) = V_0 f(t) = \begin{cases} 0, t < 0 \\ V_0, t \geq 0 \end{cases}$
- Initial condition: $i_L(t < 0) = 0$ (circuit initially uncharged and at rest)
- Particular equation: $i_L R + L \frac{di_L}{dt} = v_s$
- Because source is step response, try: $i_{L,p} = K \quad | \quad kR = V_0 \Rightarrow k = \frac{V_0}{R}$
- Total solution: $i_L(t) = Ae^{-t/t_c} + \frac{V_0}{R}$
- Initial conditions: $i_L(t) = -\frac{V_0}{R} e^{-t/t_c} + \frac{V_0}{R}$

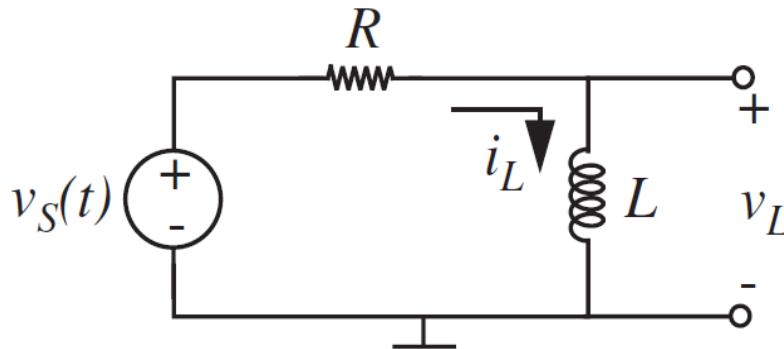Review: Simple RL Circuit – Step Response (V_0)




Current response:


$$i_L = -\frac{V}{R} e^{-\frac{Rt}{L}} + \frac{V}{R}$$

Voltage response:



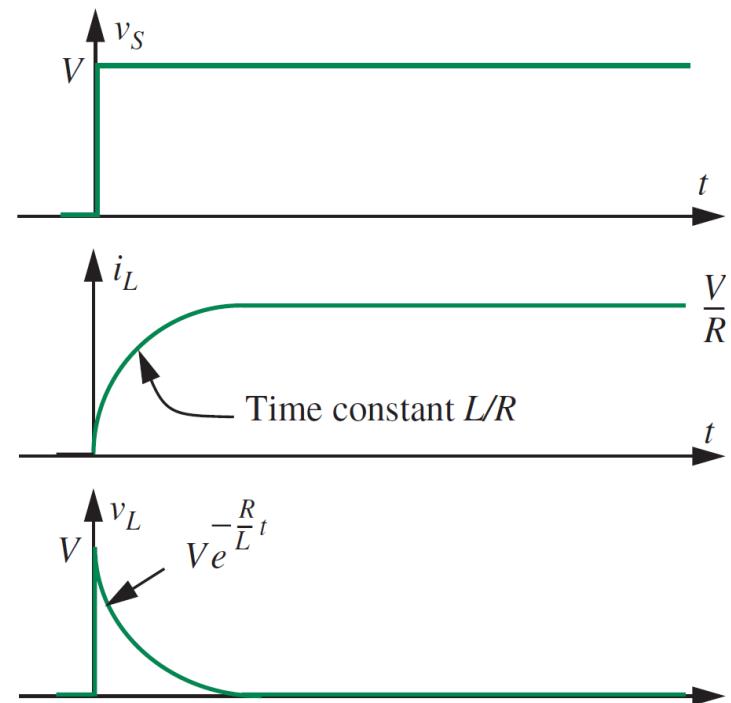
$$v_L = L \frac{di_L}{dt} = V e^{-\frac{Rt}{L}}$$



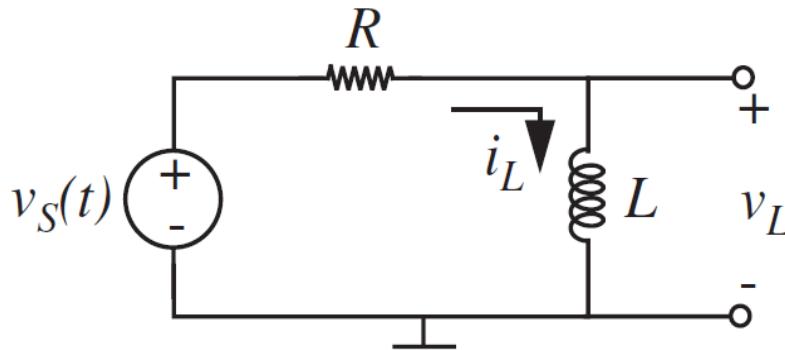
Review: Simple RL Circuit – Pulsed Response (V_0)



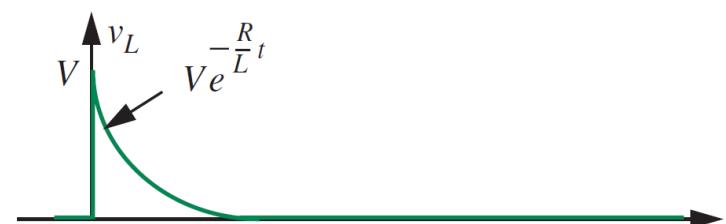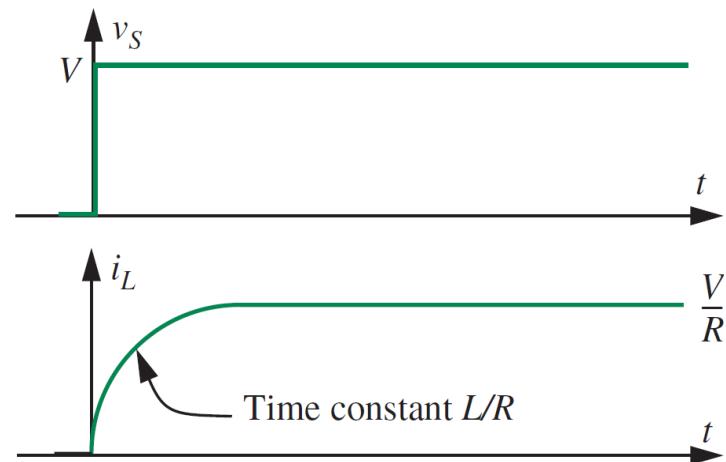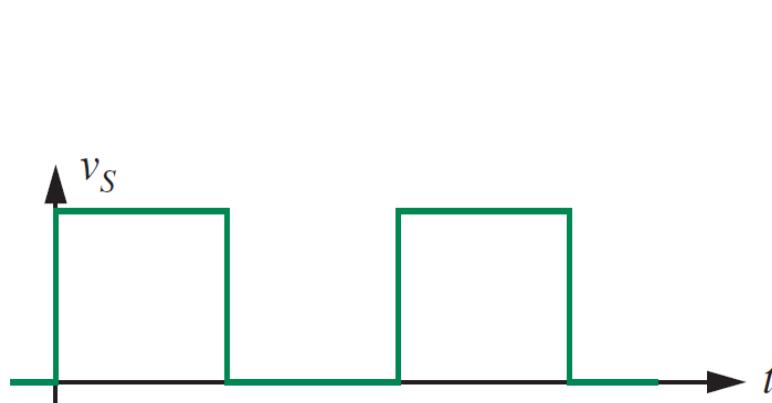
What happens when we use a square wave voltage source?



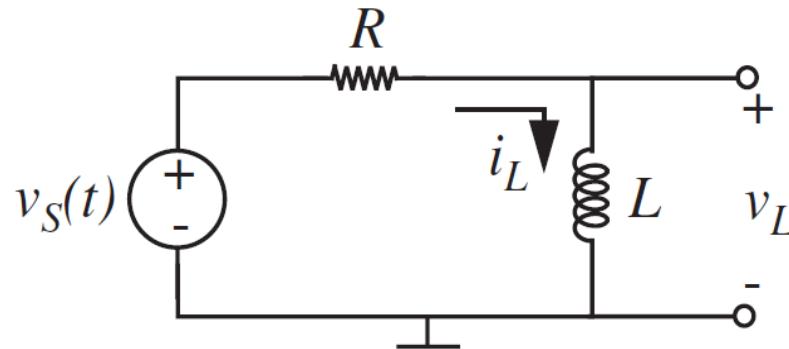
Review: Simple RL Circuit – Pulsed Response (V_0)



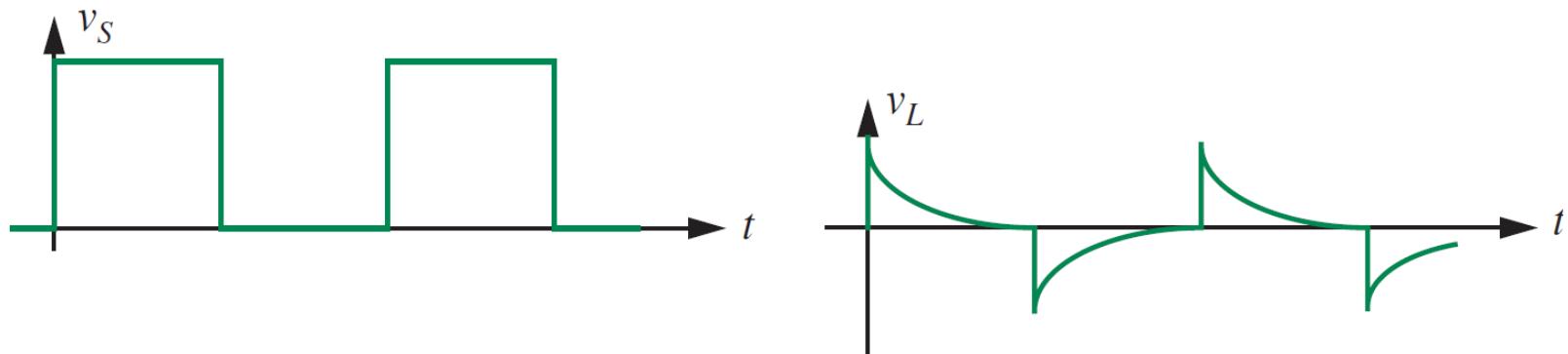What happens when we use a square wave voltage source?



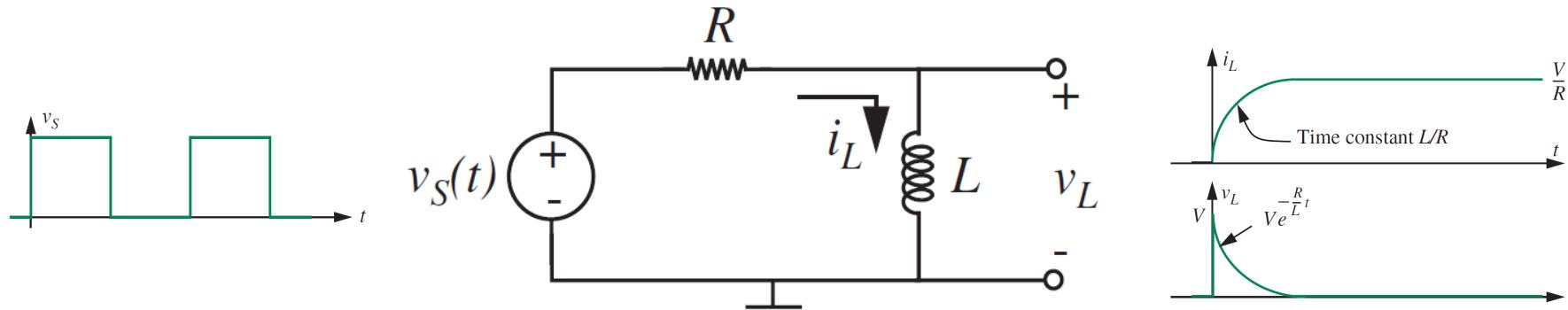Review: Simple RL Circuit – Pulsed Response (V_0)



- Initial condition: $i_L(t = 0) = V/R$

- Homogeneous equation: $i_L R + L \frac{di_L}{dt} = 0$


- Solution: $i_L(t) = A e^{-t/t_c}$

- Initial conditions: $i_L(0) = \frac{V}{R}$


$$i_L(t) = \frac{V}{R} e^{-t/t_c} \quad \left| \quad v = L \frac{di}{dt} \right.$$

$$v(t) = L \cdot \frac{V}{R} e^{-t/t_c} \cdot -\frac{R}{L} = -V e^{-t/t_c}$$

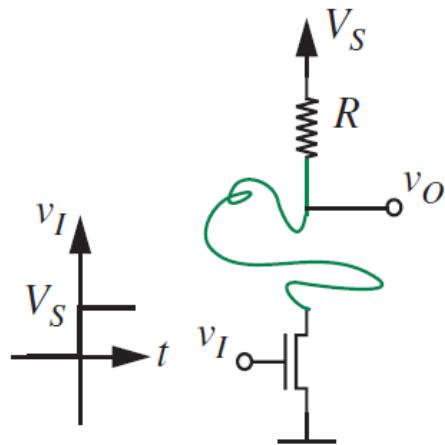
Bigger Picture: Inductance in Digital Circuits



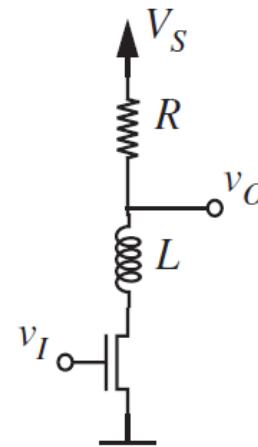
(a) Inverter with a long wire connecting the output and the MOSFET drain



(b) Circuit model

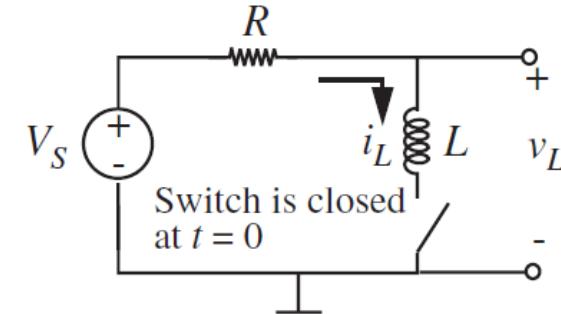

(c) Circuit for step input at v_I

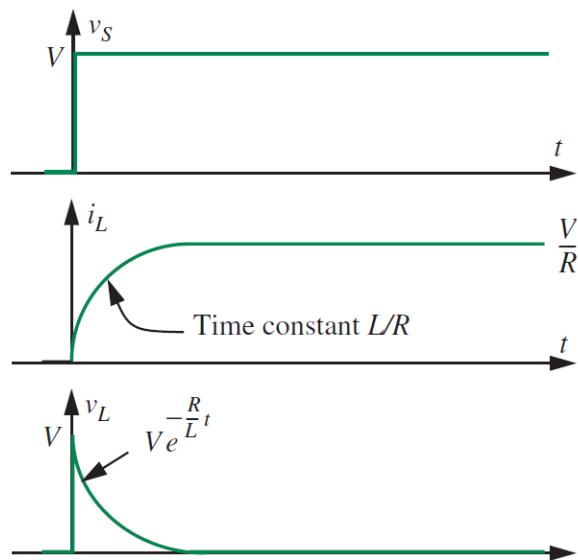

Unwanted inductance introduces a delayed response = unexpected behavior, slower response times of logic circuits

Summary: Capacitor and Inductor 1st Order ODEs

In general, the response of a 1st-order circuit (RC or RL) will be of the form:

$$y(t) = \text{final value} + (\text{initial value} - \text{final value})e^{-t/t_c}$$

$$v_c(t) = v_c(\infty) + (v_c(0) - v_c(\infty))e^{-t/RC}$$

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty))e^{-Rt/L}$$

****applies to branch variables such as C or L current, resistor V, etc.****

Capacitor


- Behaves as instantaneous **short** circuit when inputs make abrupt changes
- Behaves as **open** circuit at long times when driven by DC voltage source
- If initially charged, behaves like a **voltage source** for abrupt transitions

Inductor

- Behaves as instantaneous **open** circuit when inputs make abrupt changes
- Behaves as **short** circuit at long times when driven by DC current source
- If current is non-zero, behaves like a **current source** for abrupt transitions

Power and Energy

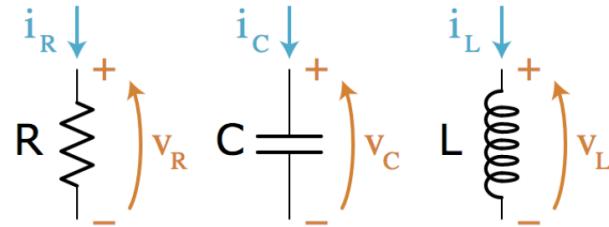Power = rate of change of energy per unit time



Power and Energy Relation in a Two-Terminal Element

Power: $P(t) = i(t)v(t) = \frac{v(t)^2}{R} = i(t)^2R$ [J/s or W]

where $i(t)$ is defined to be positive if it enters at the positive terminal.

Energy: $w(t) = \int_0^T p(t)dt$

circuit elements can consume or release power/energy if $p(t) > 0$ or $p(t) < 0$

Power and Energy

- Battery storage is limited...we want to optimize (reduce) the energy consumption of an IC, while preserving the functionality
- High power consumption = excessive heat = adverse effects
- Where does the consumed power go?
 - Resistors = dissipated as heat
 - Capacitors and inductors = stored

$$w_C(t) = \frac{Cv(t)^2}{2} \qquad w_L(t) = \frac{Li(t)^2}{2}$$

- Where does the consumed power come from? The source


Power and Energy in Circuit Elements

Delivered power:

$$V_{DD}I_{DD}(t)$$

Delivered Energy:

$$\int V_{DD}I_{DD}dt$$

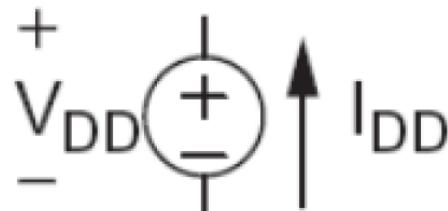

Dissipated power:

$$V_R(t)IR(t)$$

Delivered Energy:

$$\int V_R(t)IR(t)dt$$



Instantaneous power:

$$CV_C \frac{dV_C}{dt}$$

Stored energy at t :

$$\frac{1}{2}CV_C^2$$

$$+\frac{V_C}{C} \downarrow C \downarrow I_C = C \frac{dV}{dt}$$

ECE 10C
Fall 2020
Slide Set 1
Instructor: Galan Moody
TA: Kamyar Parto

REMEMBER: WITH GREAT
POWER COMES GREAT
CURRENT SQUARED
TIMES RESISTANCE.



OHM NEVER FORGOT HIS
DYING UNCLE'S ADVICE.

Last Week

- Introduction to course

This Week

- KVL/KCL, node methods
- Thevenin
- 1st-order RC/RL circuits

Important Items:


Homework #1 posted
Due Th, Oct 15 by 5 pm

Lab #1 posted
Due Fr, Oct 16

Last Quiz


Q1 [1 point]. True or False? An inductor stores energy in its magnetic field and reacts to the change in current.

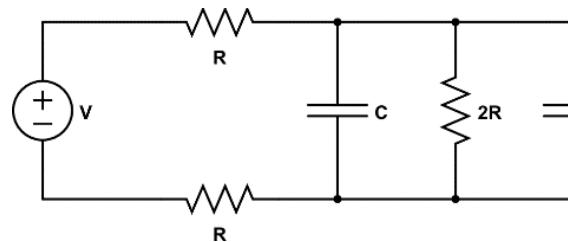Q2 [2 point]. Pick the correct Thevenin voltage and resistance as would be seen across the two capacitors.



- (a) $V_{th} = V/2$, $R_{th} = 2R$
- (b) $V_{th} = V$, $R_{th} = R$
- (c) $V_{th} = V/2$, $R_{th} = R$

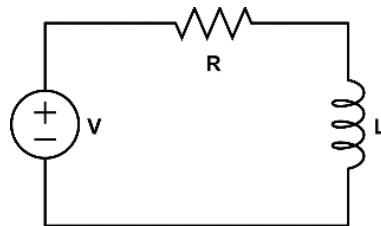Q3 [2 points]. For a step voltage response from $V = 0$ to $V = V_0$, choose the correct statements for the RL circuit below. Assume the system had been at “rest” for a long time.



At the instance $V = V_0$:

- (a) The current through L is zero.
- (b) The current through L is not zero.


At long times (steady-state):

- (a) The voltage across L is not zero.
- (b) The voltage across L is zero.


Last Quiz

Q1 [1 point]. True or False? An inductor stores energy in its magnetic field and reacts to the change in current.

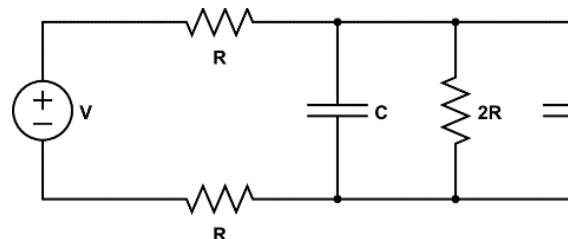
Q2 [2 point]. Pick the correct Thevenin voltage and resistance as would be seen across the two capacitors.



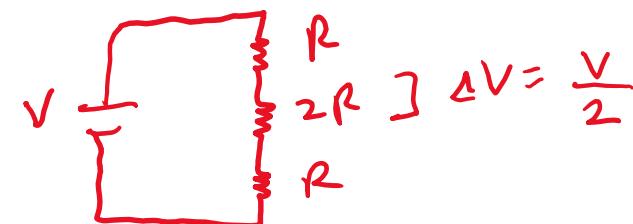- (a) $V_{th} = V/2$, $R_{th} = 2R$
- (b) $V_{th} = V$, $R_{th} = R$
- (c) $V_{th} = V/2$, $R_{th} = R$**



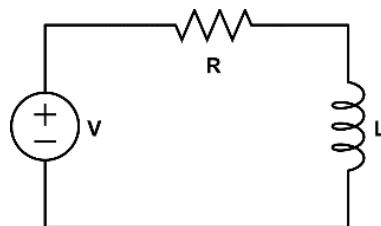Q3 [2 points]. For a step voltage response from $V = 0$ to $V = V_0$, choose the correct statements for the RL circuit below. Assume the system had been at “rest” for a long time.



At the instance $V = V_0$:

- (a) The current through L is zero.**
- (b) The current through L is not zero.

At long times (steady-state):

- (a) The voltage across L is not zero.
- (b) The voltage across L is zero.**


$$i_L(0^-) = i_L(0^+)$$

at steady state, L=short.
Thus no ΔV across L.

Quiz Time


Q1 [1 point]. True or False? An inductor stores energy in its magnetic field and reacts to the change in current.

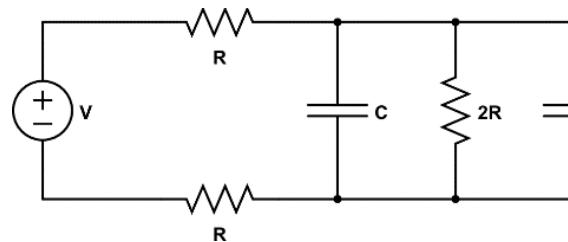Q2 [2 point]. Pick the correct Thevenin voltage and resistance as would be seen across the two capacitors.



- (a) $V_{th} = V/2$, $R_{th} = 2R$
- (b) $V_{th} = V$, $R_{th} = R$
- (c) $V_{th} = V/2$, $R_{th} = R$

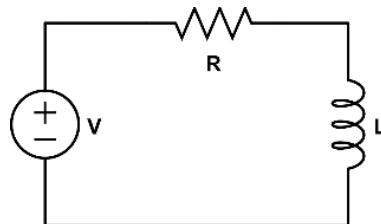Q3 [2 points]. For a step voltage response from $V = 0$ to $V = V_0$, choose the correct statements for the RL circuit below. Assume the system had been at “rest” for a long time.



At the instance $V = V_0$:


- (a) The current through L is zero.
- (b) The current through L is not zero.

At long times (steady-state):

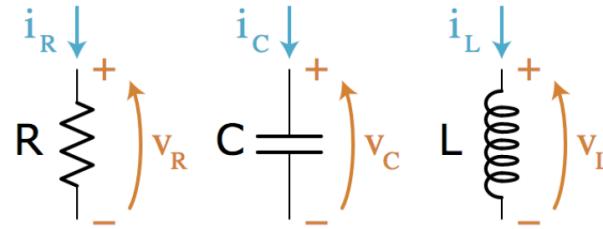- (a) The voltage across L is not zero.
- (b) The voltage across L is zero.

Power and Energy

Power = rate of change of energy per unit time



Power and Energy Relation in a Two-Terminal Element

Power: $P(t) = i(t)v(t) = \frac{v(t)^2}{R} = i(t)^2R$ [J/s or W]

where $i(t)$ is defined to be positive if it enters at the positive terminal.

Energy: $w(t) = \int_0^T p(t)dt$

circuit elements can consume or release power/energy if $p(t) > 0$ or $p(t) < 0$

Note About Time Before/After Switches Open/Close

Time right **before** a switch changes position usually denoted as $t = 0^-$

Time right **after** a switch changes position usually denoted as $t = 0^+$

Capacitor

Element law: $i(t) = C \frac{dv(t)}{dt}$

Stored energy: $w_E(t) = \frac{Cv(t)^2}{2}$

Inductor


Element law: $v(t) = L \frac{di(t)}{dt}$

Stored energy: $w_M(t) = \frac{Li(t)^2}{2}$

For a capacitor, voltage $v_c(0^-) = v_c(0^+)$ [$V = Q/C$ --> charge stored in capacitor is same right before and after a switch opens/closes]


For an inductor, current $i_L(0^-) = i_L(0^+)$ [$I = \text{Flux}/L$ --> magnetic flux in inductor is same right before and after a switch opens/closes]

Power and Energy in Simple RC Circuit

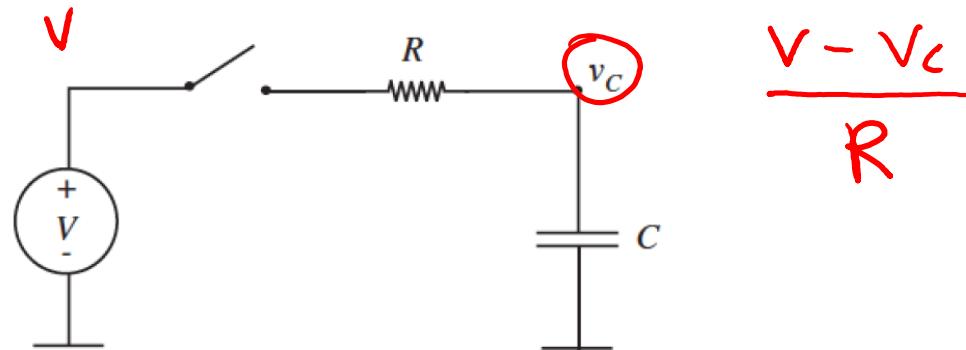

- Assume $v_c(0^-) = 0$ (zero state)
- Let's find the instantaneous power drawn from the voltage source when we close the switch at $t = 0$
- We know: $p(t) = i(t)V$
where $i(t) = [V - v_c(t)]/R$
- We need to find $v_c(t)$ when $v_c(0^-) = 0$

Power and Energy in Simple RC Circuit

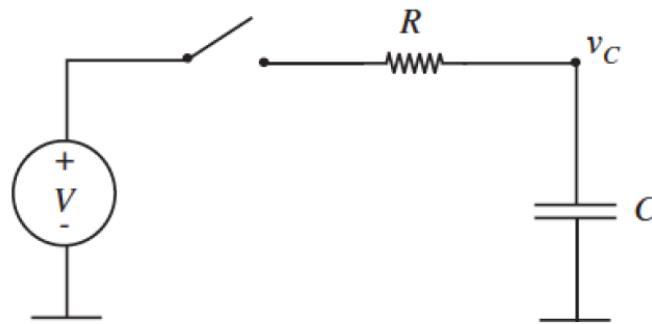


We can find the zero-state response of $v_c(t)$ to the step input $V_0 f(t)$ following the same steps as the parallel RC circuit using the generic expression:

$$v_c(t) = V_0 - V_0 e^{-\frac{t}{RC}}$$

$\left. \begin{aligned} v(+)= & \underbrace{V(\infty)}_{V_0} + \underbrace{\left[V(0) - V(\infty) \right]}_{0} e^{-\frac{t}{\tau_c}} \\ & \underbrace{V_0}_{RC} \end{aligned} \right\}$

Power and Energy in Simple RC Circuit

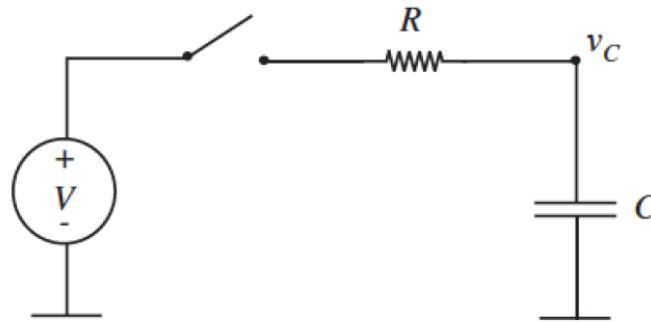


Thus, the instantaneous power **drawn** from the source:

$$p(t) = i(t)V = \frac{V_0 - v_c(t)}{R} \times V_0 = \frac{V_0 e^{-\frac{t}{RC}}}{R} \times V_0 = \frac{V_0^2 e^{-\frac{t}{RC}}}{R}$$

Energy consumption by an element

Energy: $w(t) = \int_0^T p(t)dt$

Power and Energy in Simple RC Circuit

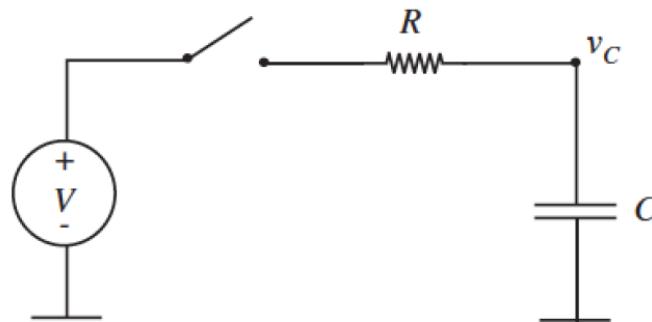

$$p(t) = \frac{V_0^2 e^{-\frac{t}{RC}}}{R}$$


- Total energy **supplied by the voltage source**:

$$w = \int_0^\infty \frac{V_0^2 e^{-\frac{t}{RC}}}{R} dt = -\frac{V_0^2 R C e^{-\frac{t}{RC}}}{R} \Big|_0^\infty = C V_0^2$$

- Energy **stored in the capacitor**:

$$w = C V_0^2 / 2$$

Power and Energy in Simple RC Circuit

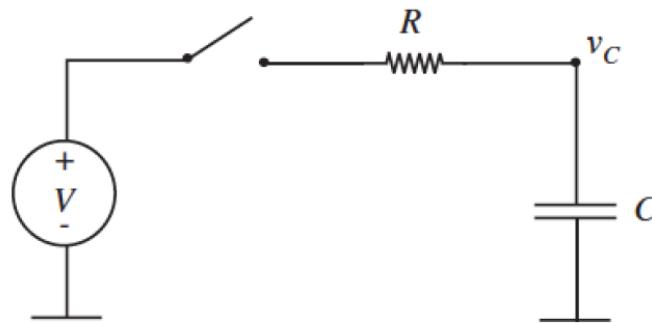

$$p(t) = \frac{V_0^2 e^{-\frac{t}{RC}}}{R}$$

- Total energy **supplied by the voltage source**:

$$w = \int_0^\infty \frac{V_0^2 e^{-\frac{t}{RC}}}{R} dt = -\frac{V_0^2 R C e^{-\frac{t}{RC}}}{R} \Big|_0^\infty = C V_0^2$$


- Energy **stored in the capacitor**:

$w = CV_0^2/2$ **Doesn't equal energy supplied by source.**
Why???


In Class Exercise

The switch in the circuit is opened at $t = 0$ after being closed for a long time.

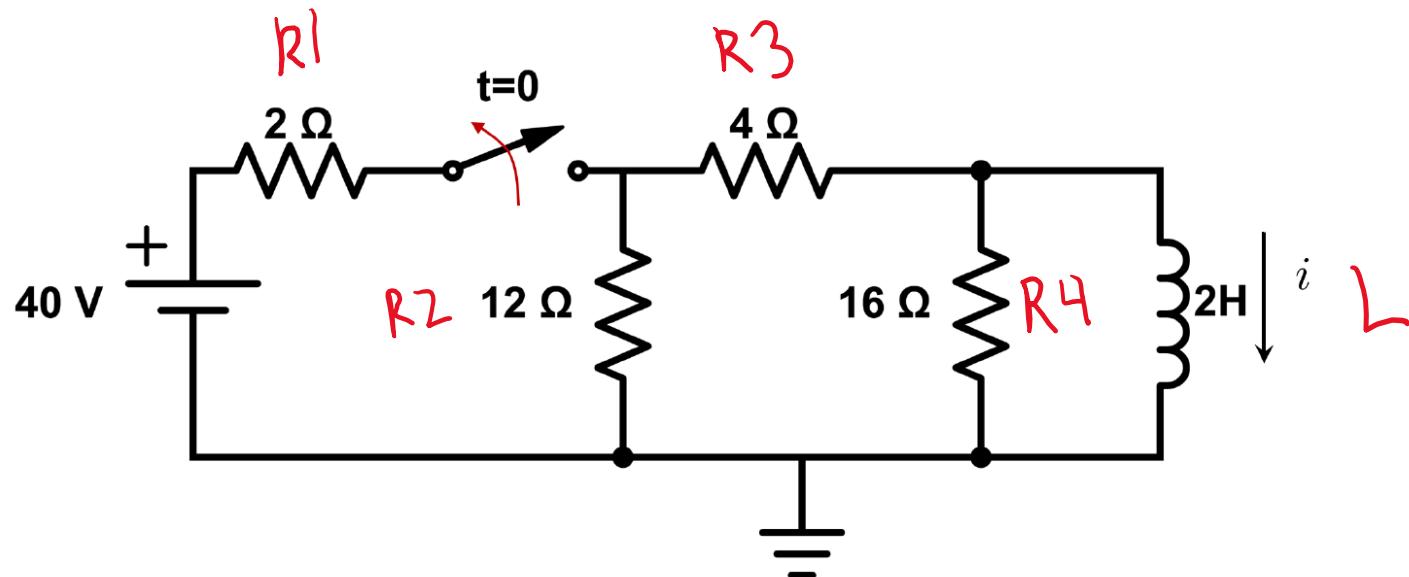1. Find $i(0)$
2. Find $i(t)$ for $t > 0$
3. Find the total energy dissipated by the circuit after $t > 0$



In Class Exercise

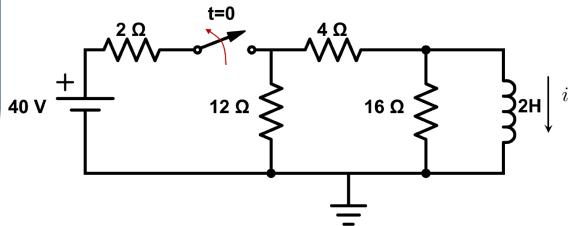


Find $i(0)$.

Switch has been closed for a long time.

What's the voltage across L?

What's the current through R4 ($16\ \Omega$ resistor)?

In Class Exercise

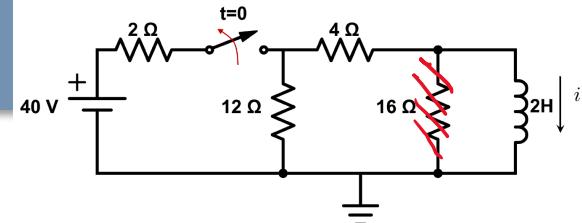


Find $i(0)$.

Switch has been closed for a long time.

What's the voltage across L?

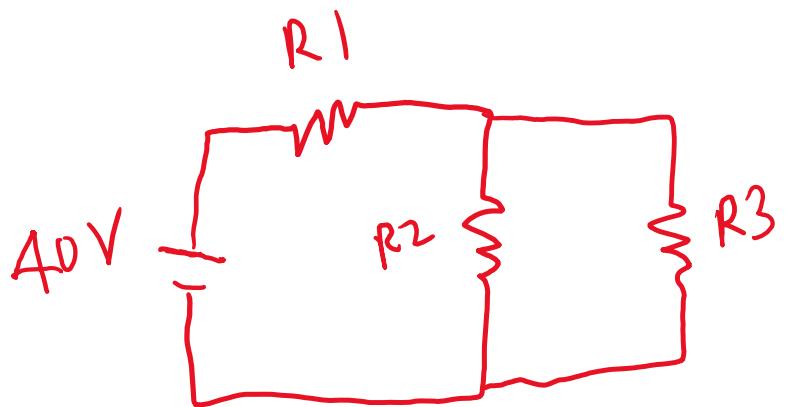
What's the current through R4 (16 Ω resistor)?



let's find current drawn from V_s ,

$$R = R_1 + R_2 // R_3 = 2 + \frac{12 \cdot 4}{11} = 5 \Omega$$

In Class Exercise

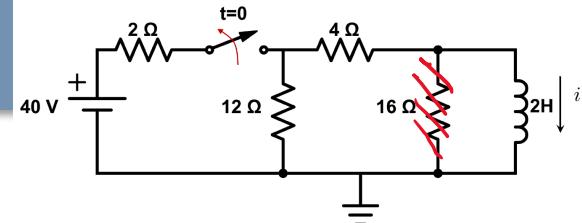


Find $i(0)$.

Switch has been closed for a long time.


What's the voltage across L?

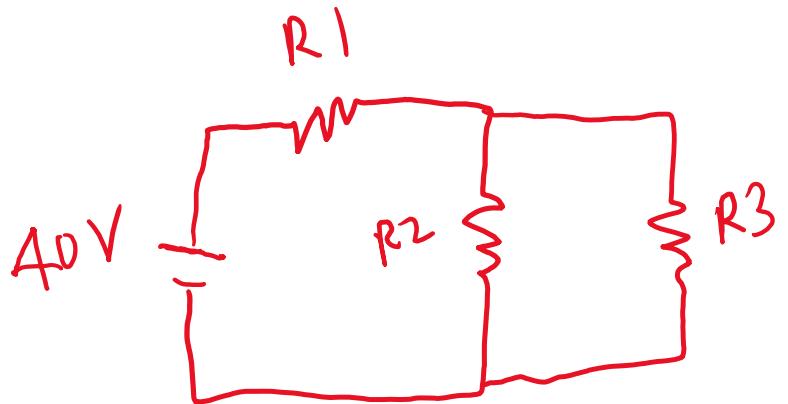What's the current through R4 (16 Ω resistor)?



let's find current drawn from V_s ,
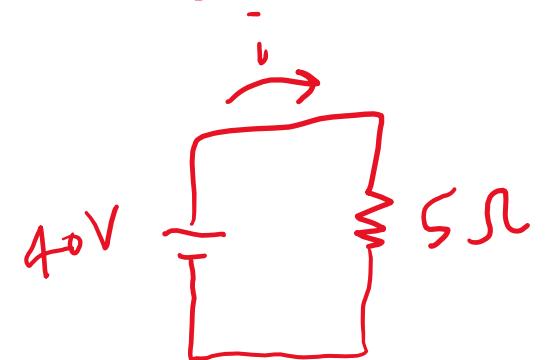
$$R = R_1 + R_2 // R_3 = 2 + \frac{12 \cdot 4}{12+4} = 5 \Omega$$




$$i = \frac{40V}{5\Omega} = 8A. \text{ How much through } R_3?$$

$$\text{Same V across } R_2 \text{ and } R_3. \frac{R_3}{R_2+R_3} = \frac{1}{4}$$

Thus $\frac{3}{4} i$ through $R_3 \rightarrow$



$$6A = i(0)$$

In Class Exercise

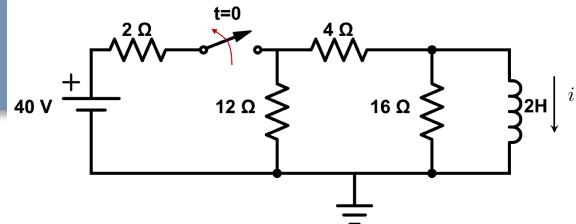


Switch opens. Find $i(t)$.

$$i_L(0^-) = i_L(0^+) = 6 \text{ A.}$$

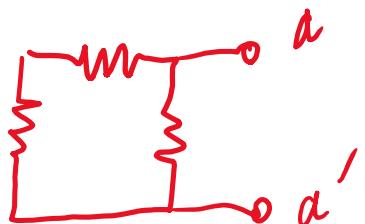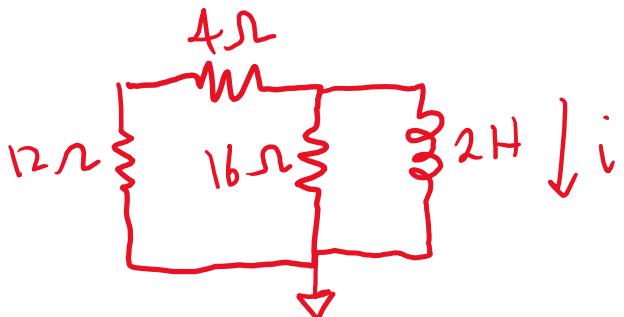


$$\rightarrow R_{eq} = 16 \parallel 16 = 8 \Omega$$

In Class Exercise

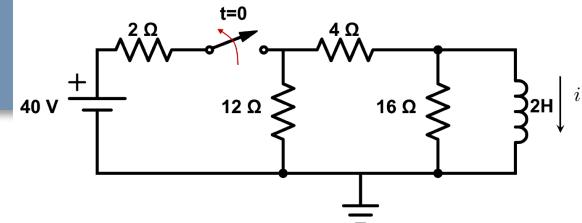

Switch opens. Find $i(t)$.

$$i_L(0^-) = i_L(0^+) = 6 \text{ A.}$$

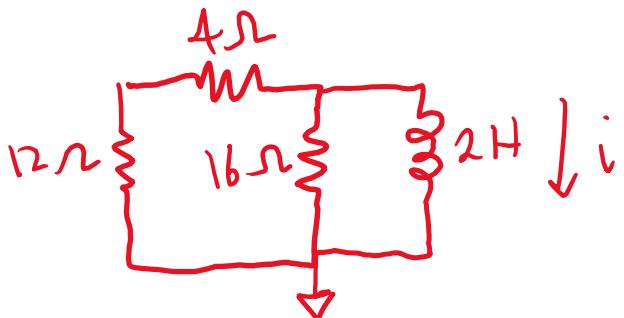

A red-drawn circuit diagram of the parallel branch. It shows the 12Ω and 16Ω resistors in series, with terminals a and a' indicated. The equation $R_{\text{eq}} = 12 \parallel 16 = 8 \Omega$ is written next to it.


$$R_{\text{eq}} = 12 \parallel 16 = 8 \Omega$$

A red-drawn circuit diagram of the inductor branch. It shows the 2H inductor in parallel with an 8Ω resistor. The current i flows through the inductor.

$$t_c = \frac{L}{R} = 0.25 \text{ sec.}$$


$$i_L(t) = i(\infty) + (i(0) - i(\infty)) e^{-t/t_c} = 6 \text{ A} e^{-t/0.25}$$

In Class Exercise

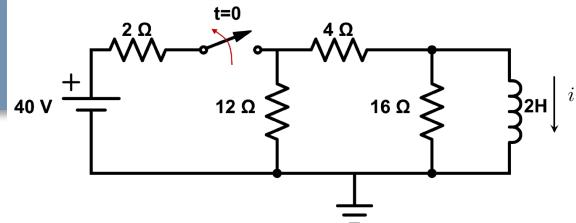

Determine power and energy dissipated.

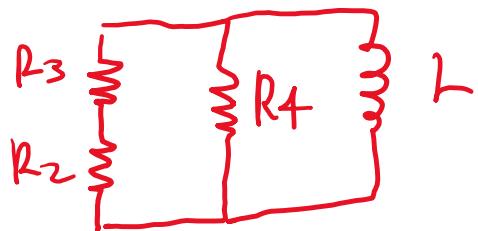
$$p(t) = i(t) V(t) = \frac{V(t)^2}{R} \quad i(t) = 6 e^{-4t} \text{ A}$$



$$V_L = V_{\text{across } R_2 + R_3} = V_{\text{across } R_4}$$


$$V_L = L \frac{di}{dt} = 2 \cdot 6 \cdot -4 e^{-4t} = -48 e^{-4t} \text{ V}$$

In Class Exercise

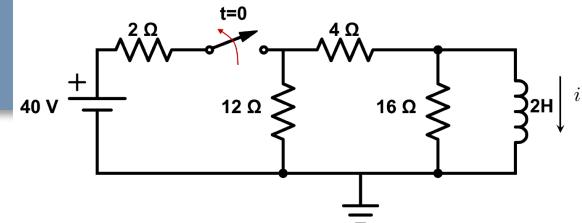

Determine power and energy dissipated.
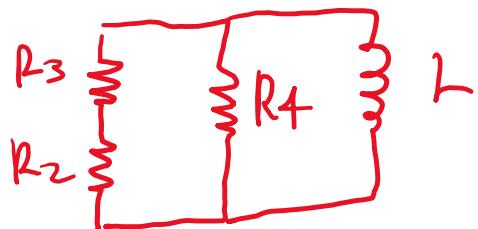
$$p(t) = i(t) V(t) = \frac{V(t)^2}{R} \quad i(t) = 6 e^{-4t} \text{ A}$$




$$V_L = V_{\text{across } R_2 + R_3} = V_{\text{across } R_4}$$

$$V_L = L \frac{di}{dt} = 2 - 6 \cdot -4 e^{-4t} = -48 e^{-4t} \text{ V.}$$


$$p(t) = \frac{(-48 e^{-4t})^2}{16 \Omega} = \frac{(-48 e^{-4t})^2}{16 \Omega} \cdot 2 = 288 e^{-8t}$$

In Class Exercise

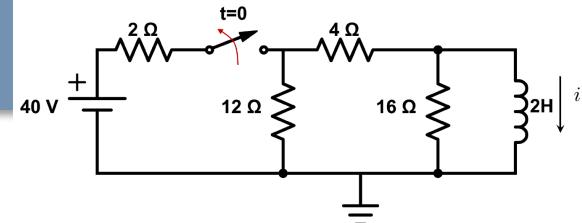

Determine power and energy dissipated.
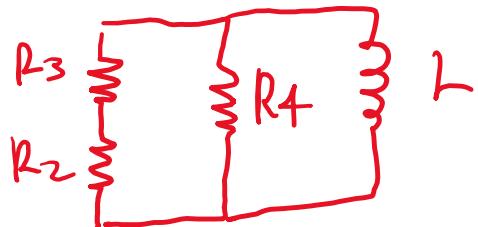
$$p(t) = i(t) V(t) = \frac{V(t)^2}{R} \quad i(t) = 6 e^{-4t} \text{ A}$$




$$V_L = V_{\text{across } R_2 + R_3} = V_{\text{across } R_4}$$

$$V_L = L \frac{di}{dt} = 2 - 6 \cdot -4 e^{-4t} = -48 e^{-4t} \text{ V.}$$

$$p(t) = \frac{(-48 e^{-4t})^2}{R} = \frac{(-48 e^{-4t})^2}{16 \Omega} \cdot 2 = 288 e^{-8t}$$


$$W = \int_0^\infty p(t) dt = \int_0^\infty 288 e^{-8t} dt = \frac{288}{-8} e^{-8t} \Big|_0^\infty = 36 \text{ J.}$$

In Class Exercise

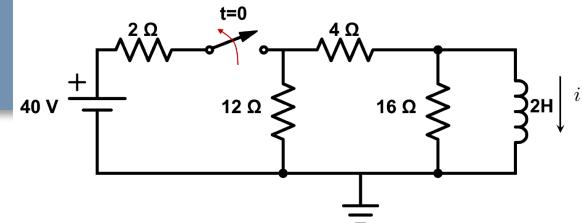

Determine power and energy dissipated.
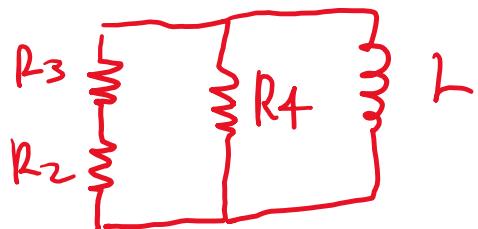
$$p(t) = i(t) V(t) = \frac{V(t)^2}{R} \quad i(t) = 6 e^{-4t} \text{ A}$$



$$V_L = V_{\text{across } R_2 + R_3} = V_{\text{across } R_4}$$


$$V_L = L \frac{di}{dt} = 2 \cdot 6 \cdot -4 e^{-4t} = -48 e^{-4t} \text{ V.}$$

$$p(t) = \frac{(-48 e^{-4t})^2}{R} = \frac{(-48 e^{-4t})^2}{16 \Omega} \cdot 2 = 288 e^{-8t}$$

$$W = \int_0^\infty p(t) dt = \int_0^\infty 288 e^{-8t} dt = \frac{288}{-8} e^{-8t} \Big|_0^\infty = 36 \text{ J.}$$


Energy stored in inductor?

In Class Exercise

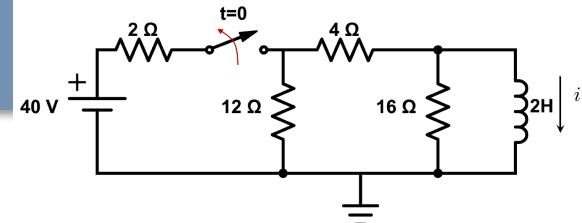

Determine power and energy dissipated.
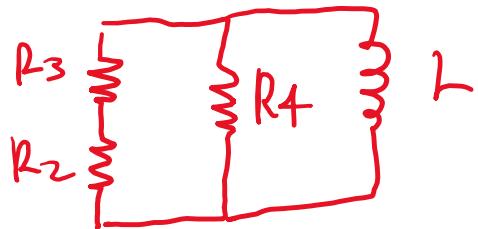
$$p(t) = i(t) V(t) = \frac{V(t)^2}{R} \quad i(t) = 6 e^{-4t} \text{ A}$$



$$V_L = V_{\text{across } R_2 + R_3} = V_{\text{across } R_4}$$

$$V_L = L \frac{di}{dt} = 2 - 6 \cdot -4 e^{-4t} = -48 e^{-4t} \text{ V.}$$

$$p(t) = \frac{(-48 e^{-4t})^2}{R} = \frac{(-48 e^{-4t})^2}{16 \Omega} \cdot 2 = 288 e^{-8t}$$

$$W = \int_0^\infty p(t) dt = \int_0^\infty 288 e^{-8t} dt = \frac{288}{-8} e^{-8t} \Big|_0^\infty = 36 \text{ J.}$$

Energy stored in inductor? $W = \frac{1}{2} L I_0^2 = \frac{1}{2} \cdot 2 \cdot 6^2 = 36 \text{ J}$

Good!

Summary: Capacitor and Inductor 1st Order ODEs

$$y(t) = \text{final value} + (\text{initial value} - \text{final value})e^{-t/t_c}$$

$$v_c(t) = v_c(\infty) + (v_c(0) - v_c(\infty))e^{-t/RC}$$

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty))e^{-Rt/L}$$

****applies to branch variables such as C or L current, resistor V, etc.****

Capacitor

- Behaves as instantaneous **short** circuit when inputs make abrupt changes
- Behaves as **open** circuit at long times when driven by DC voltage source

Inductor

- Behaves as instantaneous **open** circuit when inputs make abrupt changes
- Behaves as **short** circuit at long times when driven by DC current source

Power and Energy Relation in a Two-Terminal Element

Power:

$$P(t) = i(t)v(t) = \frac{v(t)^2}{R}$$

Energy:

$$w(t) = \int_0^T p(t)dt$$