

**ECE 10C
Fall 2020**

Slide Set 11

**Instructor: Galan Moody
TA: Kamyar Parto**



1st correct answer in chat = +1 quiz point:

What is this, and what happened to it today? What's it designed to do?

Previously

- Bode Plot
- 1st-order Filters

This week

- 2nd-order RLC (resonant) filters

Important Items:


- HW #5 due Thurs, 12/3
- Lab #5 due Friday, 12/4
- ESCI questionnaire
- HW # 6 posted, due 12/10

Quiz Time

Q1: True or False: An RC circuit with the output voltage measured across the capacitor is an example of a low-pass filter.

Q2: True or False: An RL circuit with the output voltage measured across the inductor is an example of a low-pass filter.

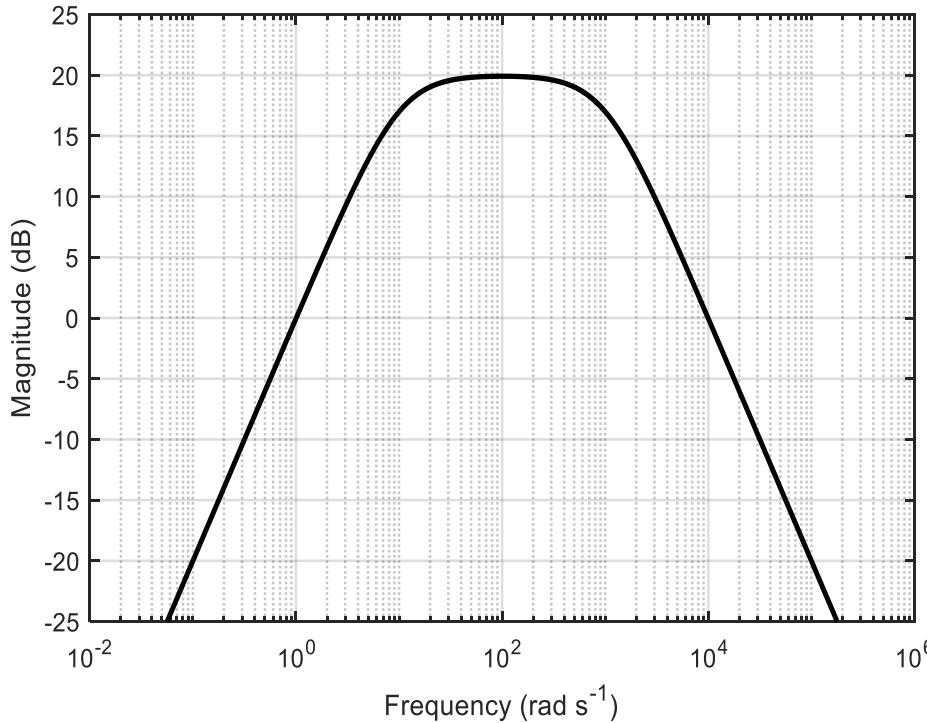Q3: Pick the correct transfer function for the gain showed in the plot below:




a) $\frac{(1+j\omega)}{(1+\frac{j\omega}{10})(1+\frac{j\omega}{100})}$

b) $\left(1 + \frac{j\omega}{10}\right) \left(1 + \frac{j\omega}{100}\right)$


c) $\frac{j\omega}{(1+\frac{j\omega}{10})(1+\frac{j\omega}{1000})}$

d) $\frac{j\omega}{(1+\frac{j\omega}{10})(1+\frac{j\omega}{100})}$


Filters

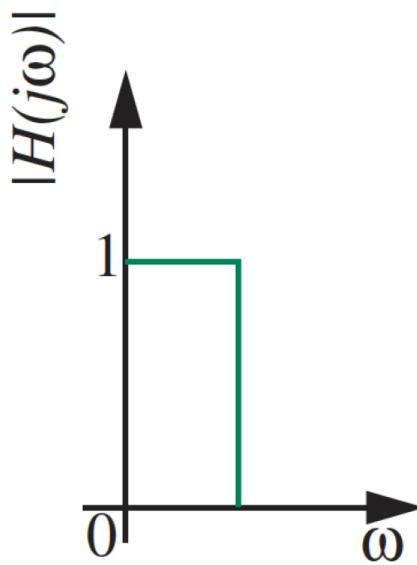


Low pass

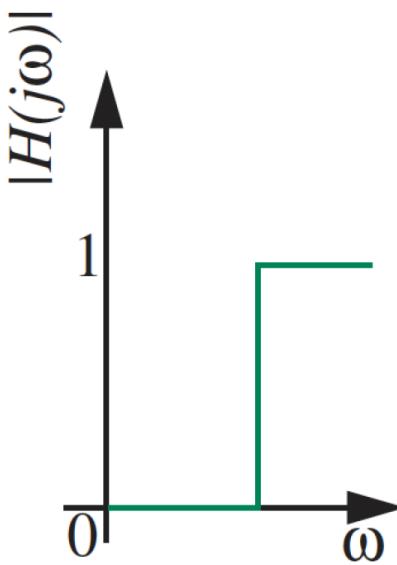

High pass

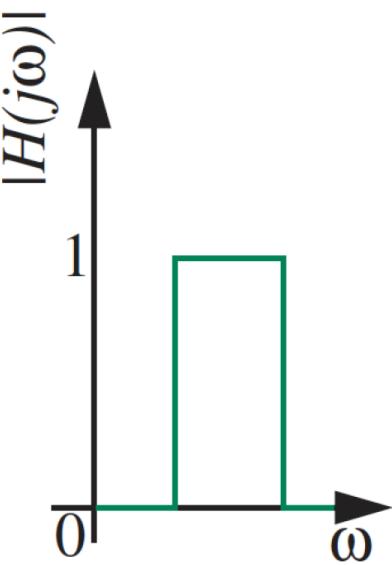

Band pass

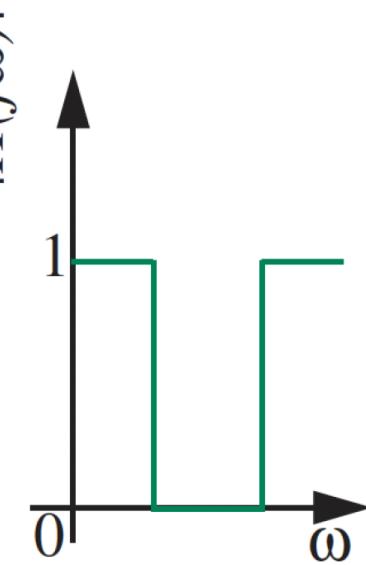

Band stop










RL and RC circuits

- ✓ First-order ODEs
- ✓ Exponential behavior
- ✗ Not oscillatory

RLC circuits

- ✓ Secord-order ODEs
- ✓ Oscillatory behavior
- ✓ Damped behavior

Frequency Response of General Functions

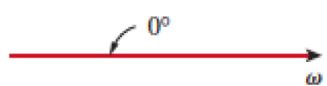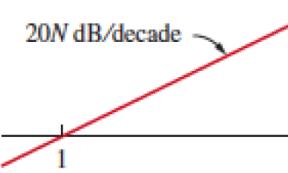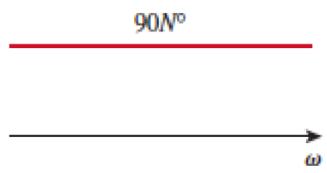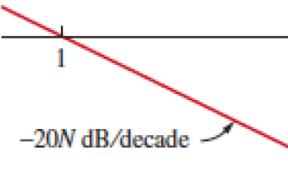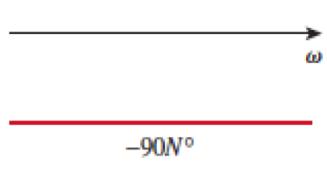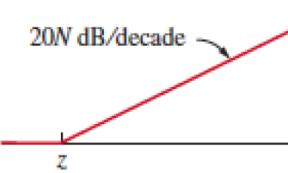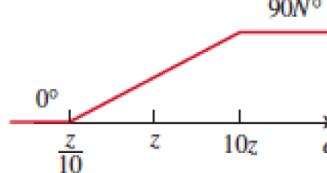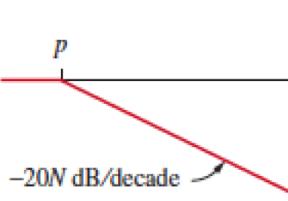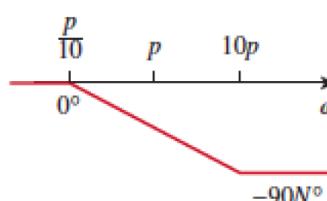Term	Magnitude	Phase shift
K	$20 \log_{10} K$ 	0° 
$(j\omega)^N$	$20N \text{ dB/decade}$  1 ω	$90N^\circ$ 
$\frac{1}{(j\omega)^N}$	$-20N \text{ dB/decade}$  1 ω	$-90N^\circ$ 
$\left(1 + \frac{j\omega}{z}\right)^N$	$20N \text{ dB/decade}$  z ω	0° at $\frac{z}{10}$, $90N^\circ$ at z , $90N^\circ$ at $10z$ 
$\frac{1}{(1 + j\omega/p)^N}$	$-20N \text{ dB/decade}$  p ω	0° at $\frac{p}{10}$, $-90N^\circ$ at p , $-90N^\circ$ at $10p$ 


Frequency Response of General Functions

Second-order terms (ω^2)


Term

$$\left[1 + \frac{2j\omega\zeta}{\omega_n} + \left(\frac{j\omega}{\omega_n} \right)^2 \right]^N$$



Magnitude

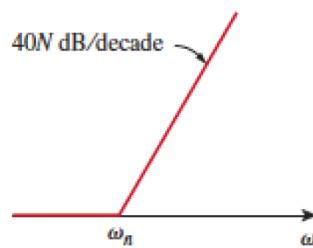

Phase shift


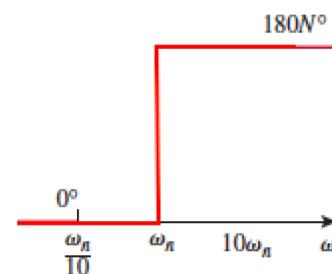

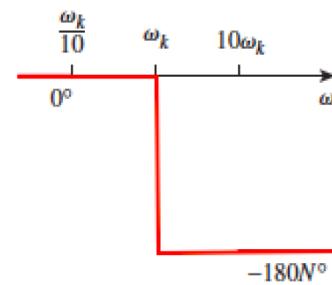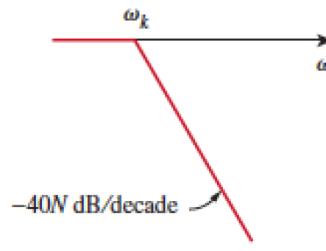
$$\frac{1}{[1 + 2j\omega\zeta/\omega_k + (j\omega/\omega_k)^2]^N}$$



Frequency Response with 2nd-Order Terms

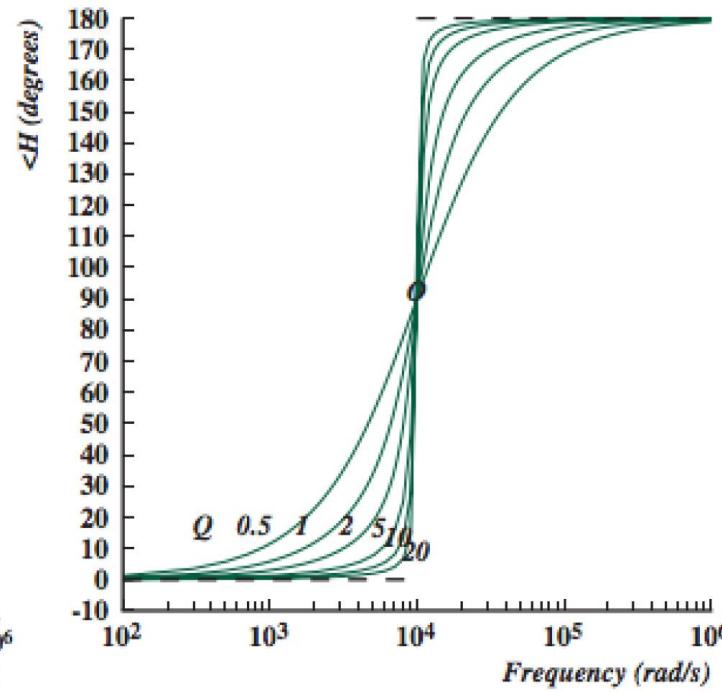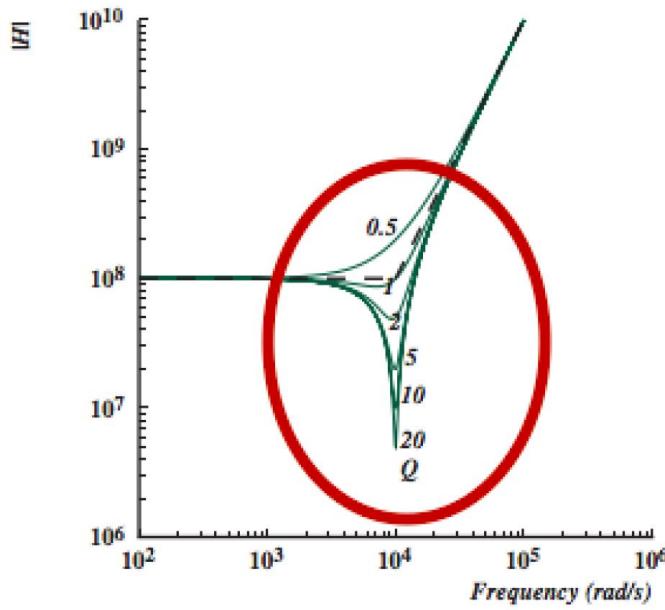
The actual frequency response of resonant circuits “peaks” at the resonance frequency



This peaking behavior is ideal for filter design, especially for bandpass and bandstop filters → **resonant** filters

Recall: Parallel RLC Circuit

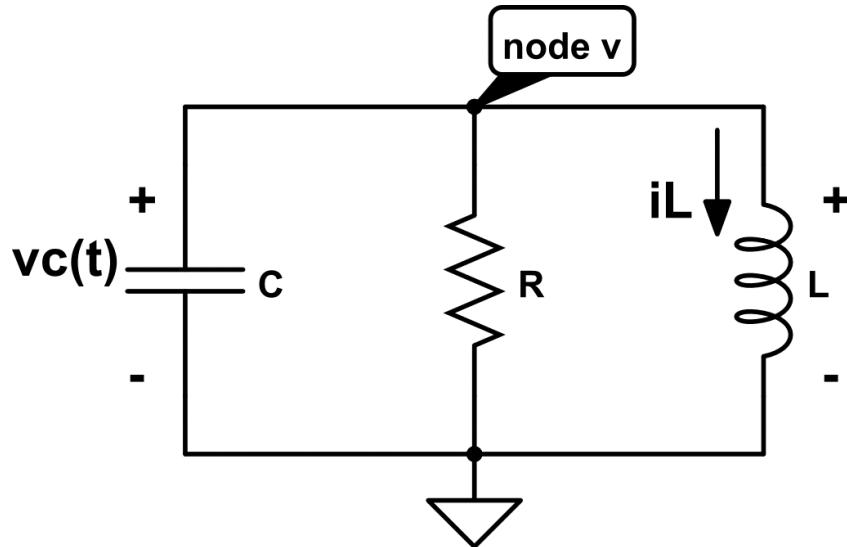Write the ODE, the general expression for $v_c(t)$, and the solutions to the characteristic equation for the undriven parallel RLC circuit below:



- Node KCL:

$$-C \frac{dv(t)}{dt} - \frac{v(t)}{R} - \frac{1}{L} \int_{-\infty}^t v(t') dt' = 0$$

- Take the derivative:

$$\frac{d^2v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = 0$$

- By substituting Ae^{st} , we get the characteristic equation:

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

Recall: Parallel RLC Circuit

- We can also write the characteristic equation as:

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

- Where we have defined:


$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

- The roots of the characteristic equation are:

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$
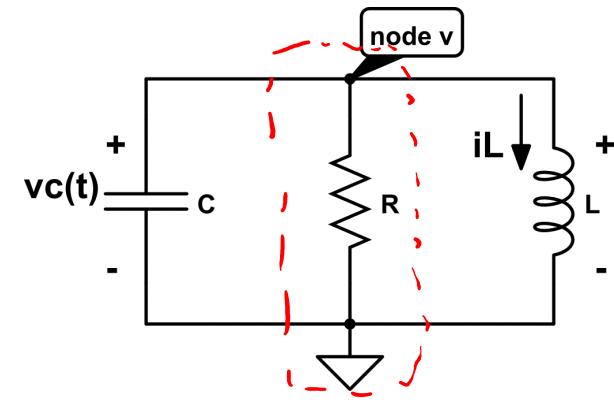
$$v_1(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$




Checking 2nd-Order Terms

Are all 2nd-order circuits resonant?

For a circuit to be resonant, we need to have terms in $H(s)$ such as:

$$s^2 + 2\alpha s + \omega_n^2$$

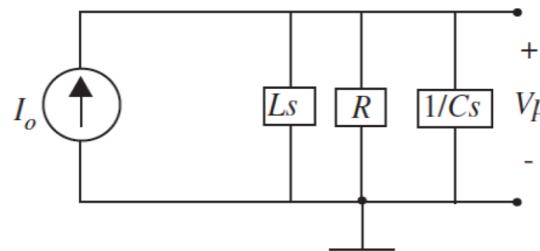If $Q = \frac{\omega_n}{2\alpha} > 0.5$, the roots of the equation above are complex, and we will have 2nd-order terms in $H(s)$, thus resonant behavior




Recall for Parallel RLC

$$\alpha = \frac{1}{2RC}$$

A parallel RLC is not resonant unless the resistance (R) is large enough to meet the following condition:

$$R > 0.5 \sqrt{\frac{L}{C}}$$

Resonant Parallel RLC Circuit

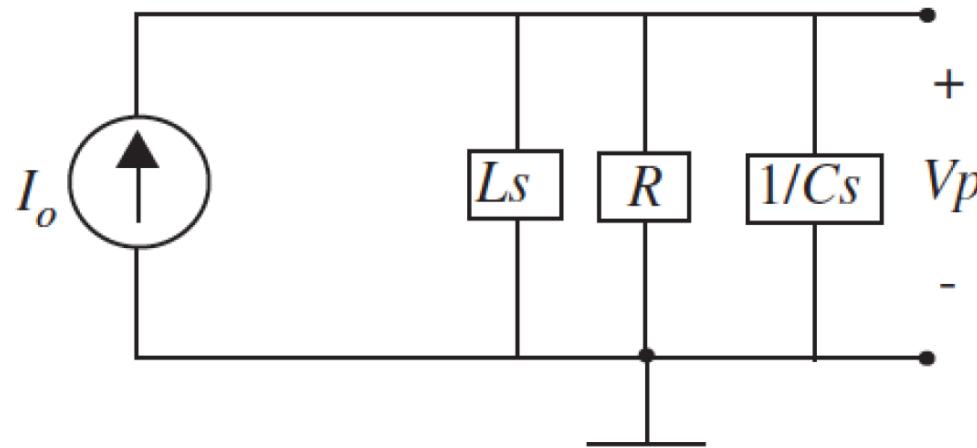

We always start with finding the transfer function:

$$H(j\omega) = \frac{V_p}{I} = \frac{1}{\frac{1}{j\omega L} + \frac{1}{R} + j\omega C} = \frac{1}{\frac{1}{R} + j(\omega C - \frac{1}{\omega L})}$$

Sketch Frequency Response: Asymptotic Method

$$H(j\omega) = \frac{V_p}{I} = \frac{1}{\frac{1}{j\omega L} + \frac{1}{R} + j\omega C} = \frac{1}{\frac{1}{R} + j(\omega C - \frac{1}{\omega L})}$$

High frequency asymptote?

$$H(j\omega) = \frac{1}{j\omega C} \rightarrow |H(j\omega)| = \frac{1}{\omega C}, \quad \angle H(j\omega) = -90^\circ$$

Low frequency asymptote?

$$H(j\omega) = j\omega L \rightarrow |H(j\omega)| = \omega L, \quad \angle H(j\omega) = 90^\circ$$

The high and low frequency asymptotes intersect at $\omega_o = \frac{1}{\sqrt{LC}}$



Sketch Frequency Response: Asymptotic Method

High frequency asymptote?

$$H(j\omega) = \frac{1}{j\omega C} \rightarrow |H(j\omega)| = \frac{1}{\omega C}, \quad \angle H(j\omega) = -90^\circ$$

Low frequency asymptote?

$$H(j\omega) = j\omega L \rightarrow |H(j\omega)| = \omega L, \quad \angle H(j\omega) = 90^\circ$$

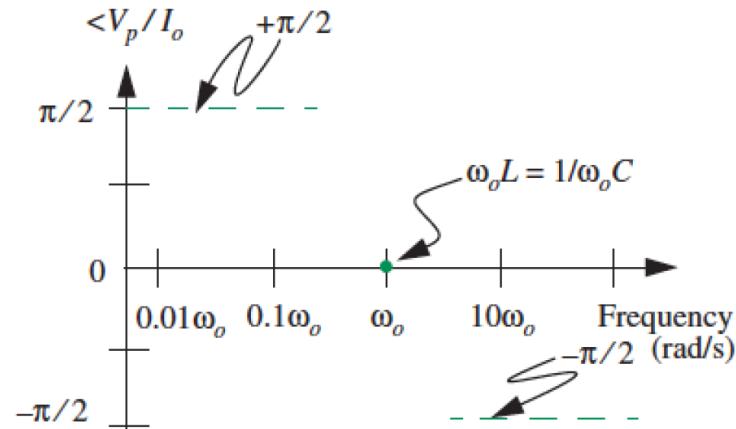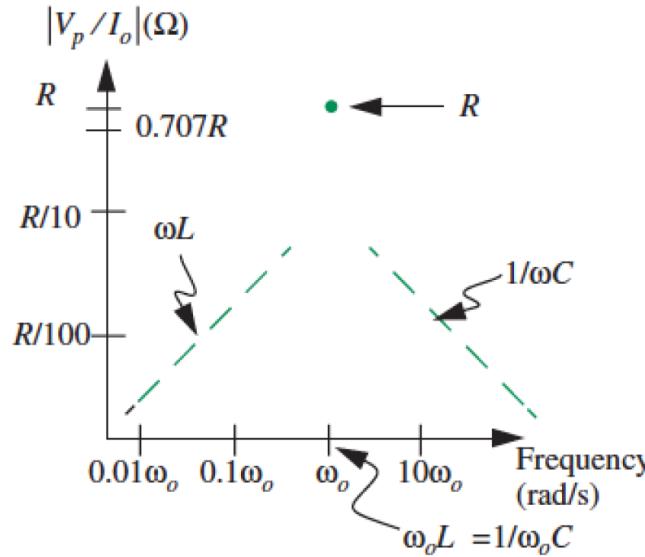


If we connect these asymptotes, we get an approximate sketch of the frequency response

Let's Double-Check Our Method



$$H(j\omega) = \frac{V_p}{I} = \frac{1}{\frac{1}{R} + j\omega C + \frac{1}{j\omega L}}$$
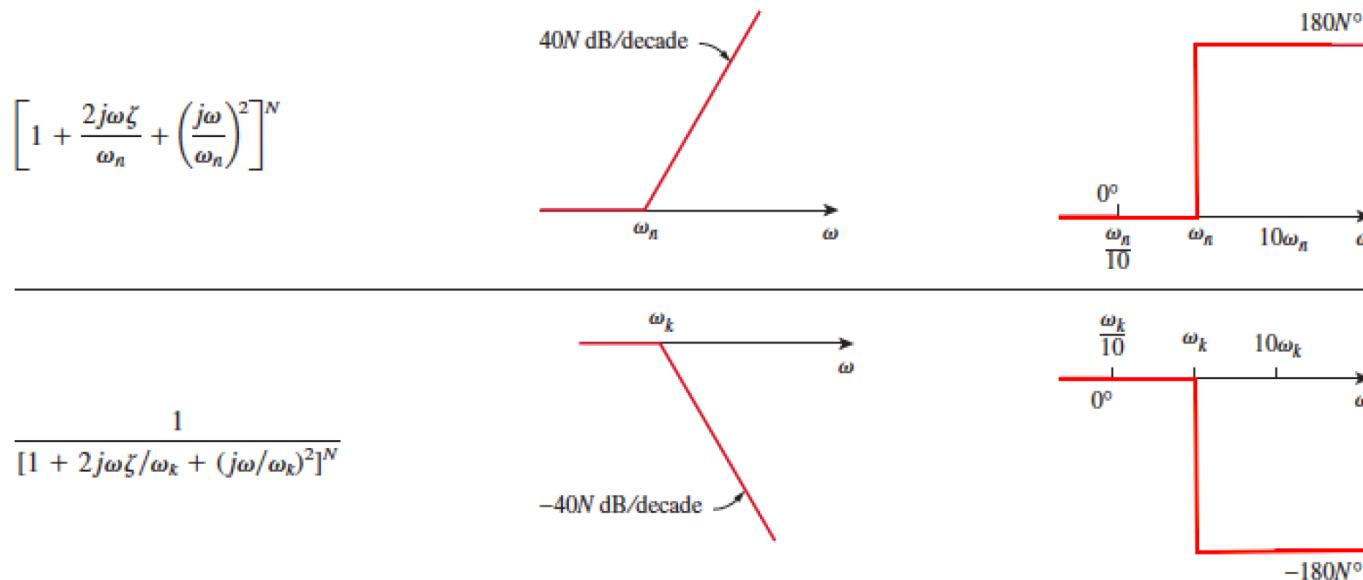
$$H(j\omega) = L \frac{j\omega}{1 + \frac{L}{R}j\omega + (j\omega)^2 LC}$$



Parallel RLC: Adding the Resonance Peak
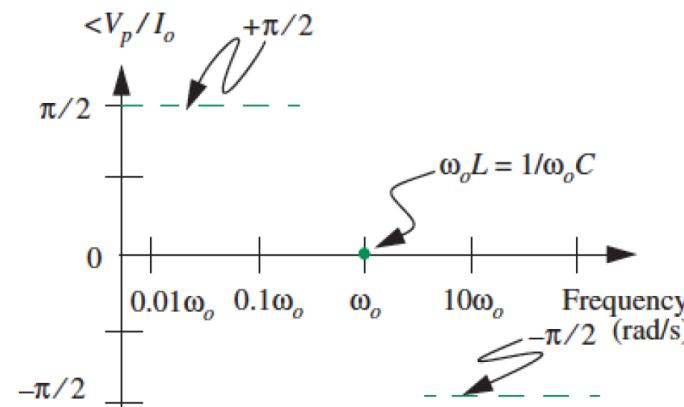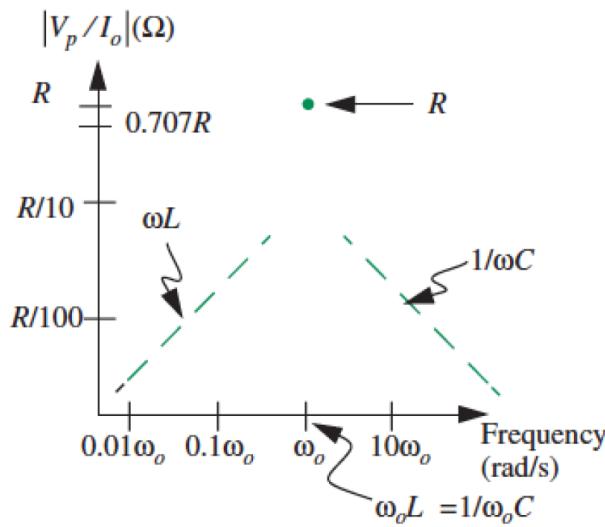
$$H(j\omega) = \frac{V_c}{I} = \frac{1}{\frac{1}{R} + j(\omega C - \frac{1}{\omega L})}$$





Value of $H(j\omega)$ at $\omega_o = \frac{1}{\sqrt{LC}}$?

$$\omega_o C - \frac{1}{\omega_o L} = 0 \rightarrow H(j\omega_o) = R$$

Parallel RLC: Adding the Resonance Peak
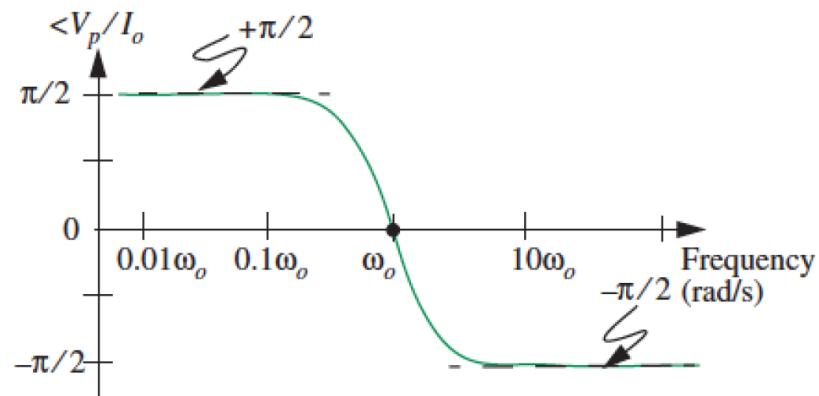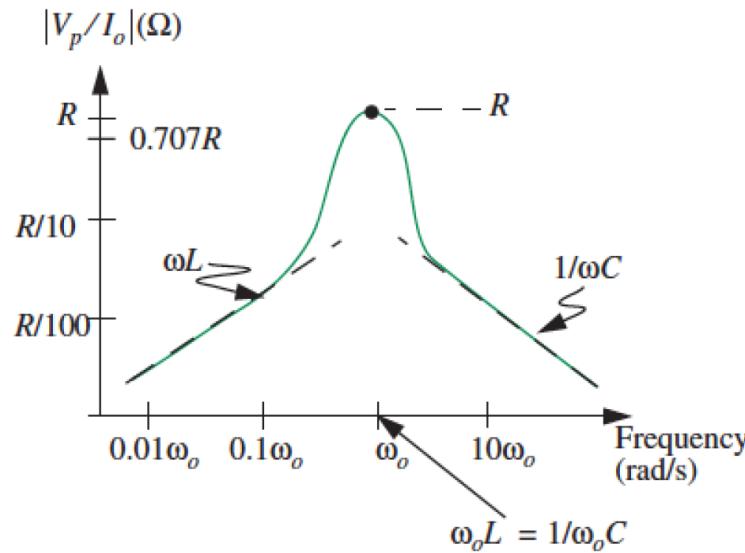
$$H(j\omega) = \frac{V_c}{I} = \frac{1}{\frac{1}{R} + j(\omega C - \frac{1}{\omega L})}$$




Value of $H(j\omega)$ at $\omega_o = \frac{1}{\sqrt{LC}}$?

$$\omega_o C - \frac{1}{\omega_o L} = 0 \rightarrow H(j\omega_o) = R$$

Resonant Filters

Note

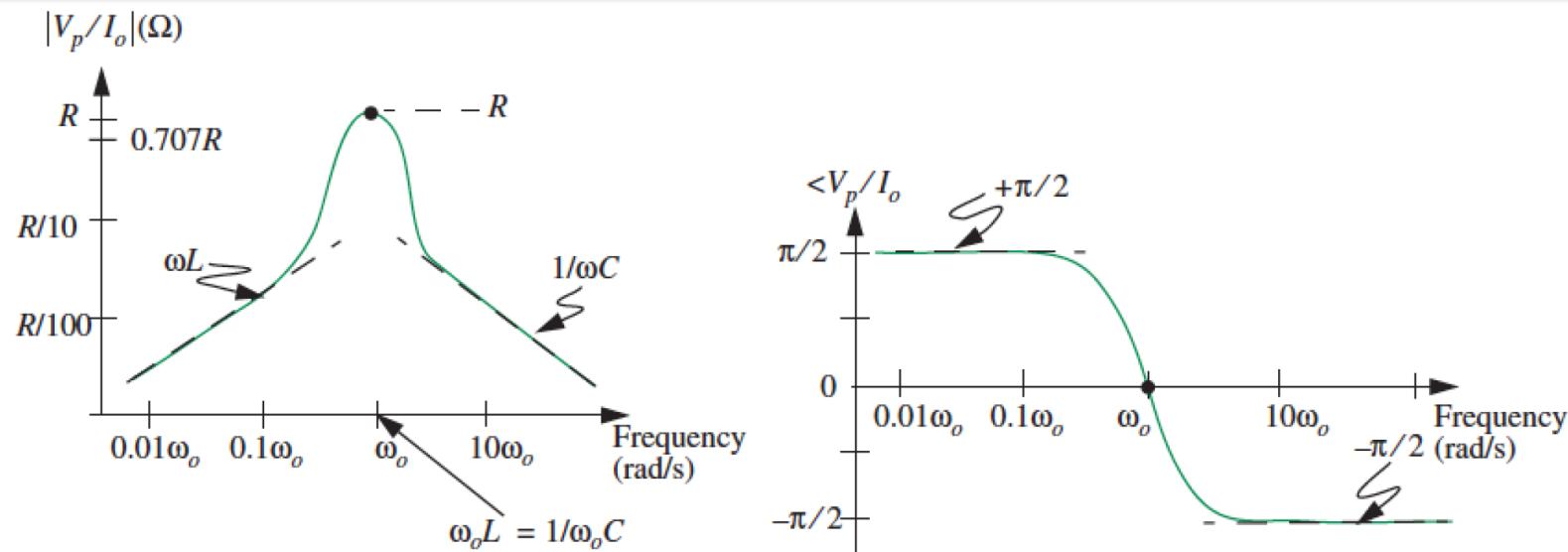You don't need a resonant term to design a bandpass or bandstop filter. You can do this through combinations of RL or RC first-order circuits. But these require a lot more components in more complex circuits to get similar effects.




Takeaway Lesson

Resonant Filters can help us design “highly selective” bandpass and bandstop filters. With RLC circuits, by expressing $H(s)$ in its standard form, we can identify the important parameters for the filters through inspection, and then plot using methods we've learned (log-log or Bode plots)

Resonance Frequency
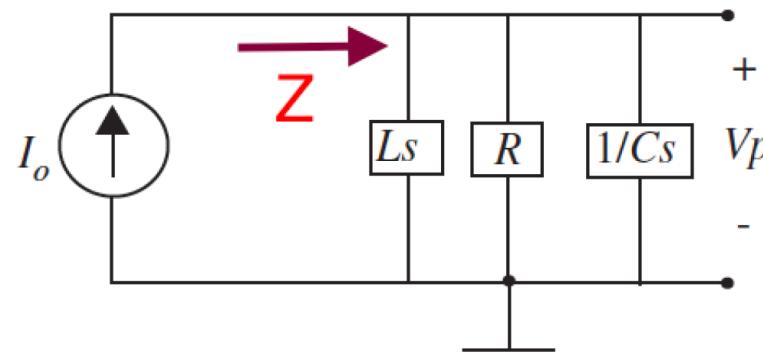
$$H(j\omega) = \frac{V_c}{I} = Z = \frac{1}{\frac{1}{R} + j \left(\omega_o C - \frac{1}{\omega_o L} \right)}$$



This is why the natural frequency ω_o is also called the **resonance frequency** in parallel RLC:

$$\omega_o C - \frac{1}{\omega_o L} = 0 \rightarrow \text{Input impedance} = R$$

System gain is at its peak


Resonance Frequency

At what frequency does resonance occur?

Multiple definitions of resonance frequency exist (usually very similar)

Definition: The resonance frequency is the frequency at which $|H(s)|$ is at a relative maximum or minimum. In a series or a parallel RLC circuit, the impedance seen from the input is purely real (i.e. resistive)
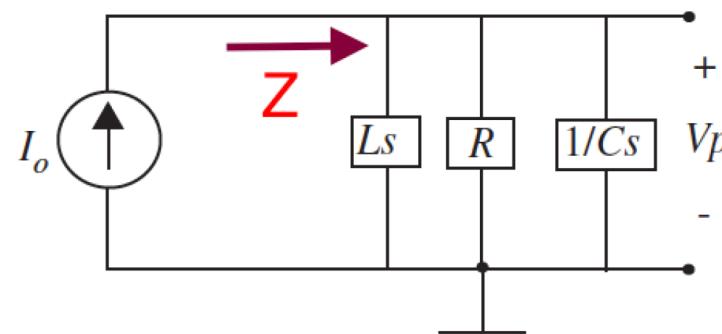
$$\text{Im}(Z) = 0 \text{ at resonance}$$



At resonant frequencies, small periodic driving forces have the potential to produce large amplitude oscillations

Peak Gain

How large is the gain peak at the resonance frequency?



Role of the Q-factor in 2nd-Order Resonant Systems

Remember: The Q factor or quality factor is a dimensionless parameter that describes how under-damped an oscillator is:

$$Q = \frac{\omega_0}{2\alpha} = \frac{\tau\omega_0}{2} \approx \# \text{ oscillations before energy dissipates}$$

As Q factor \uparrow , resonance with **larger relative gain + smaller bandwidth**

Effect of Q: Frequency Selectivity

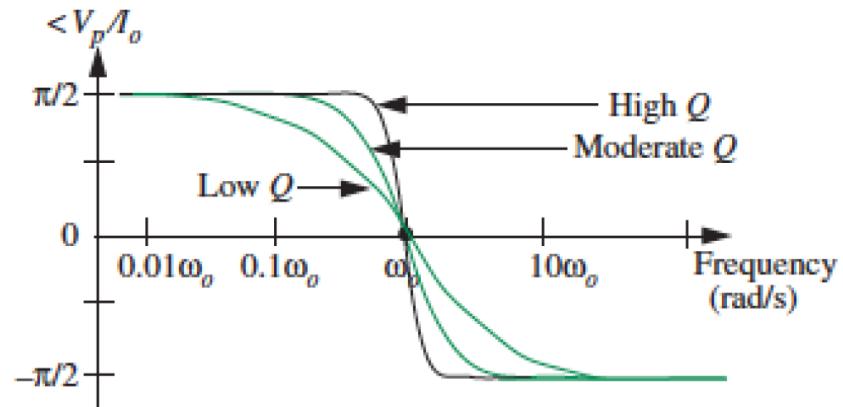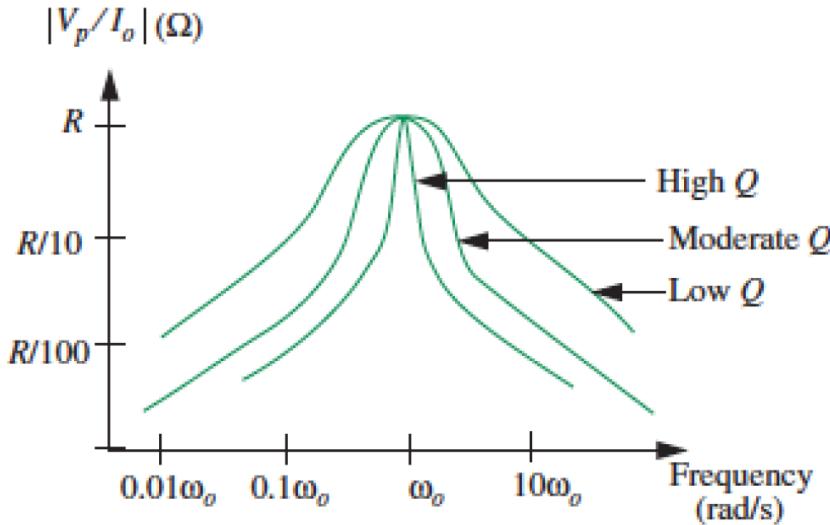


Selectivity is captured through the **bandwidth** of a filter

The bandwidth measures the width of a filter's “passband” (range of freqs that can pass through a filter) → **but how do we define passing?**

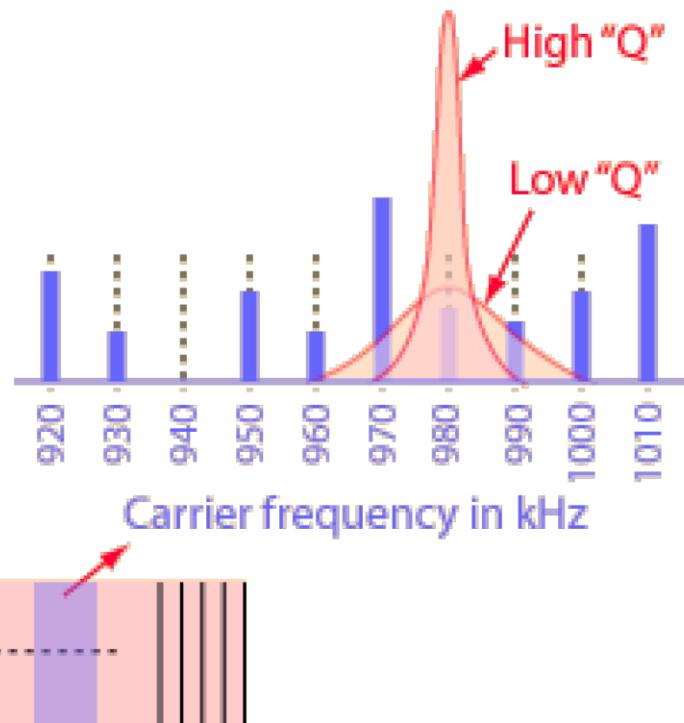Example: Importance of Right Choice of Q

Selection of AM radio stations by the radio receiver → The selectivity of the tuning must be high enough




10 kHz bandwidth from
540-1600 kHz for
106 possible bands

AM Radio

Bandwidth Definition


The bandwidth of a bandpass filter is usually defined as the difference between two lower and upper cut-off points where
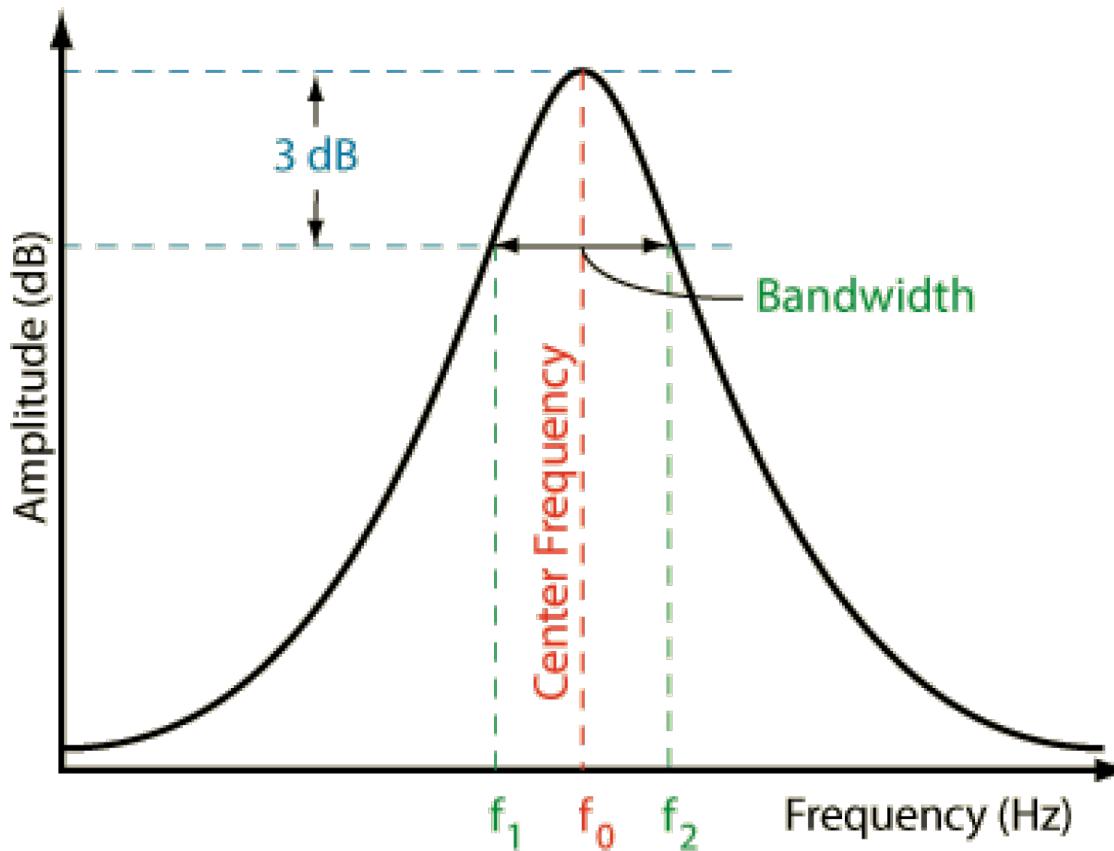
$$\text{Gain at cut-off} = \frac{1}{\sqrt{2}}(\text{max gain}) = 0.707(\text{max gain})$$



Bandwidth of a Low-Pass Filter

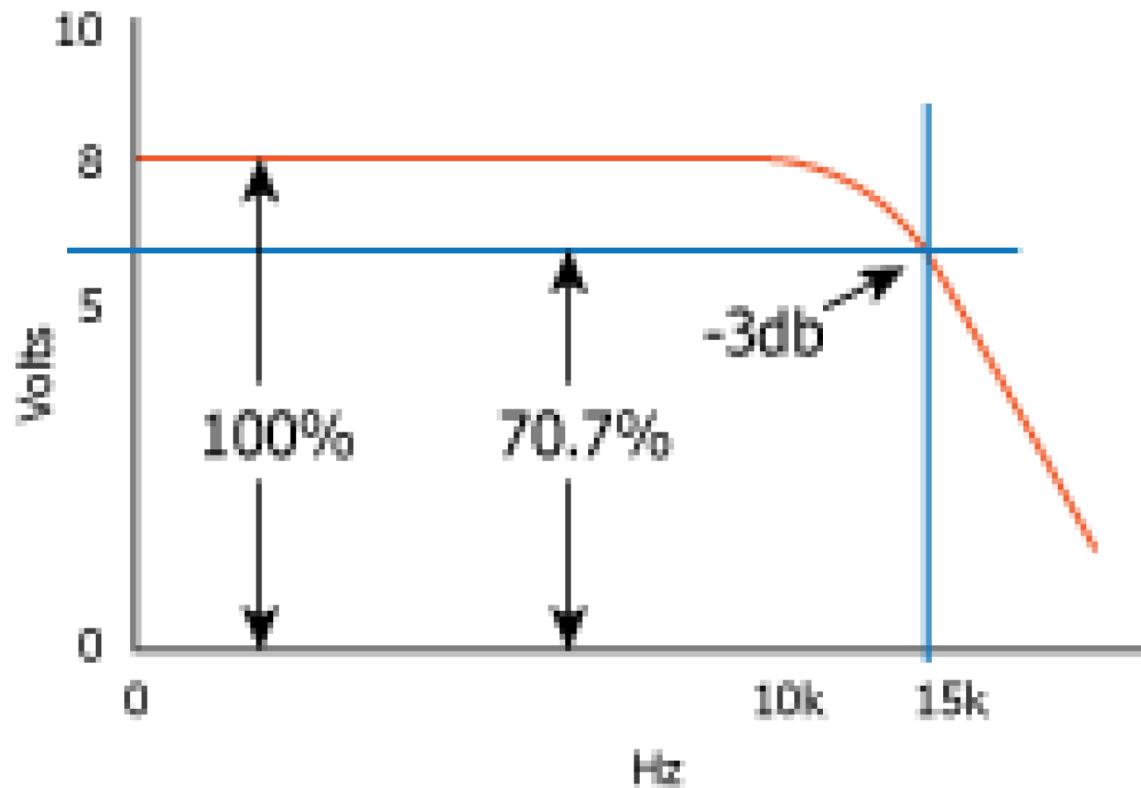The same idea applies to a lowpass filter (the highpass filter is solely characterized by its cut off frequency and does not have a bandwidth)




$$\text{Gain at cut off} = \frac{1}{\sqrt{2}} \text{ (DC gain)}$$

Bandwidth of a Parallel RLC Filter

$$H(j\omega) = \frac{V_c}{I} = \frac{1}{\frac{1}{j\omega L} + \frac{1}{R} + j\omega C} = \frac{1}{\frac{1}{R} + j(\omega C - \frac{1}{\omega L})}$$

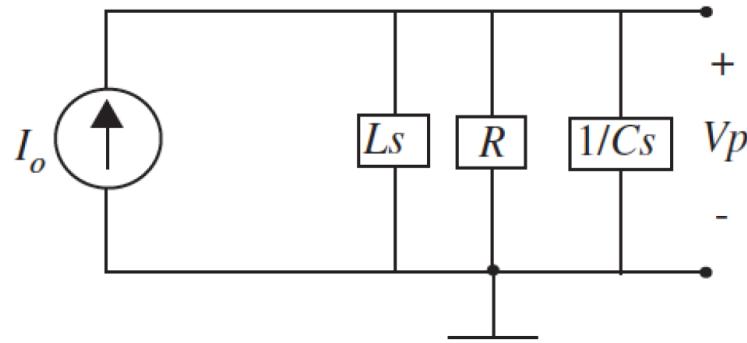We know the maximum gain point: $H(j\omega_0) = R$



$$|H(j\omega_{cut})| = \frac{R}{\sqrt{2}}$$

$$\left| \frac{1}{\frac{1}{R} + j(\omega_{cut}C - \frac{1}{\omega_{cut}L})} \right| = \frac{1}{\frac{1}{R}\sqrt{2}} \rightarrow \left| (1 + jR(\omega_{cut}C - \frac{1}{\omega_{cut}L})) \right| = \sqrt{2}$$

Bandwidth of a Parallel RLC Filter

$$R(\omega_{cut}C - \frac{1}{\omega_{cut}L}) = \pm 1$$

$$\frac{1}{R} = G \rightarrow \omega_{cut}^2 \pm \frac{G}{C}\omega_{cut} - \frac{1}{LC} = 0$$

Four roots $\rightarrow \omega_{cut} = \pm \frac{G}{2C} \pm \sqrt{(\frac{G}{2C})^2 + \frac{1}{LC}}$ \rightarrow Only two are positive



Cut-off frequencies and Bandwidth

$$\omega_{cut} = \pm \frac{G}{2C} + \sqrt{(\frac{G}{2C})^2 + \frac{1}{LC}} \rightarrow \text{Bandwidth} = \frac{G}{C} = \frac{1}{RC} = 2\alpha = \frac{\omega_0}{Q}$$

General definition of quality factor

$$Q = \frac{\omega_0}{\text{Bandwidth}}$$



Bandwidth of a Parallel RLC Filter

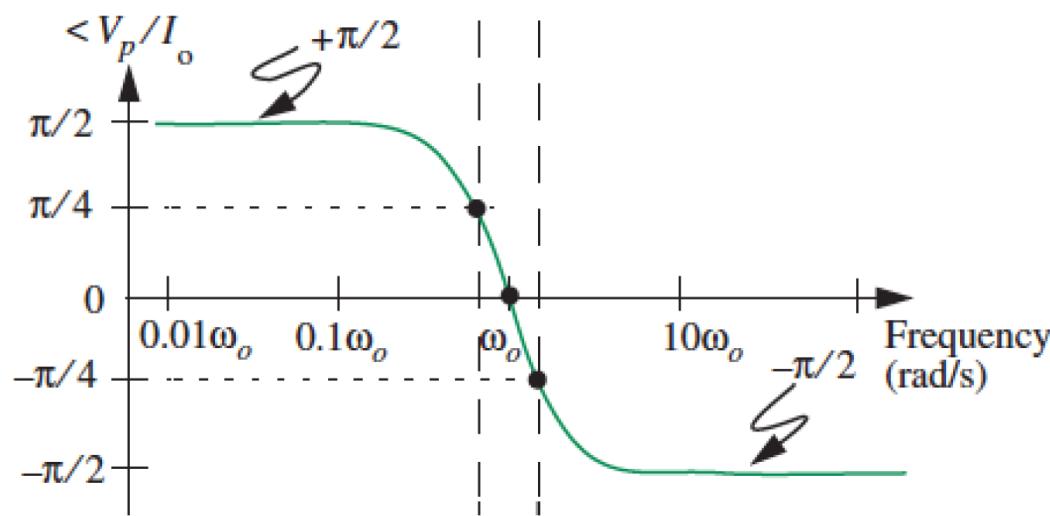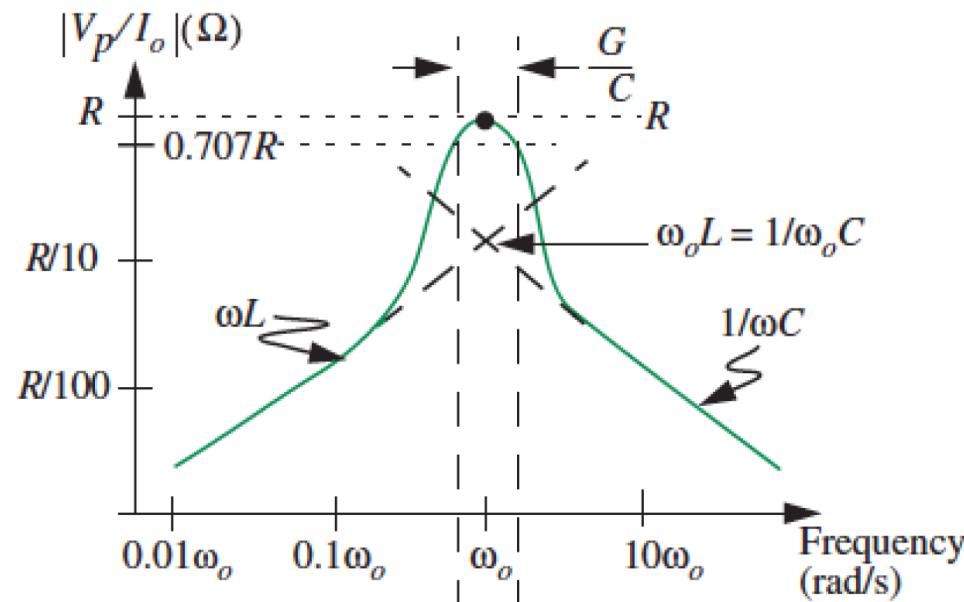

Cut-Off (Half Power) Frequencies

The cut-off frequencies
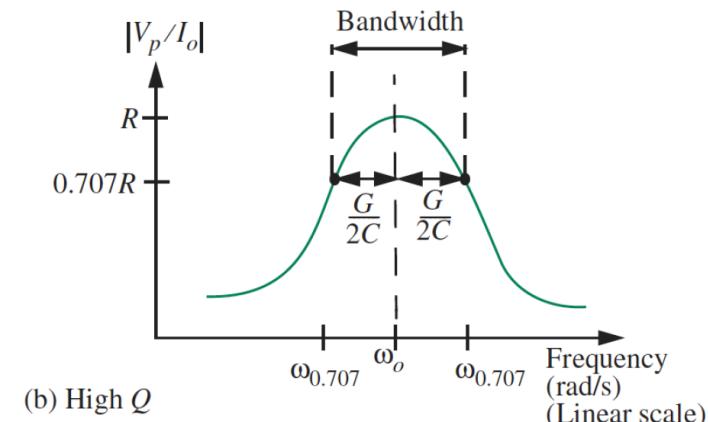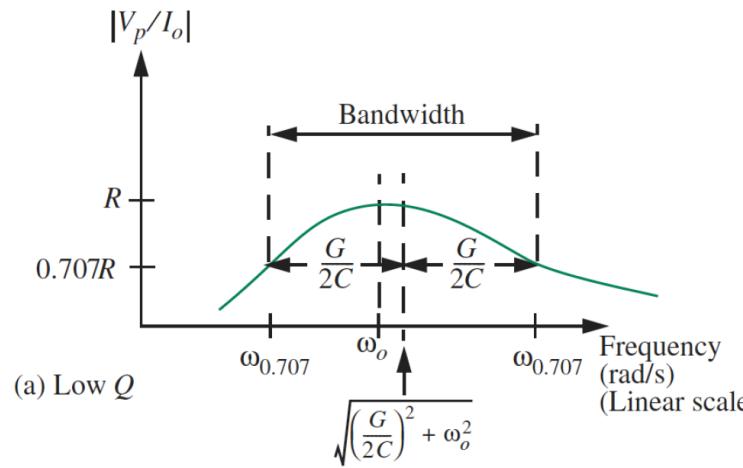
$$\omega_{cut} = \pm \frac{\omega_o}{2Q} + \omega_o \sqrt{1 + \left(\frac{1}{2Q}\right)^2}$$



The cut-off frequencies with high Q factor ($Q \geq 10$)

$$\omega_{cut} \approx \omega_o \pm \frac{\text{Bandwidth}}{2}$$

Designing a Bandpass Filter

We would like to choose R, L, C to get a certain peak gain, at a certain center frequency ω_o , with a given Q factor (or a given bandwidth $\frac{\omega_o}{Q}$).

- ① Peak gain = R
- ② Given the Q factor and ω_o , choose L and C such that:

$$\text{resonance frequency } \omega_o = \frac{1}{\sqrt{LC}} \rightarrow LC = \frac{1}{\omega_o^2}$$

$$Q = \omega_o RC = \frac{1}{\sqrt{LC}} RC \rightarrow \sqrt{\frac{C}{L}} = \frac{Q}{R} \rightarrow \frac{C}{L} = \left(\frac{Q}{R}\right)^2$$

$$\left(\frac{Q}{R}\right)^2 L^2 = \frac{1}{\omega_o^2} \rightarrow L = \frac{R}{Q\omega_o}$$

Example

Design constraints

Peak gain = 10, $\omega_o = 10^5$ rad/s, $Q = 1, 2, 0.5$

$$R = 10 \Omega \quad \text{for all } Q$$

For $Q = 1 \rightarrow L = \frac{R}{Q\omega_o} = 0.1\text{mH}, C = \frac{1}{\omega_o^2 L} = 1\mu\text{F}$



For $Q = 2 \rightarrow L = 0.05\text{mH}, C = 2\mu\text{F}$

For $Q = 0.5 \rightarrow L = 0.2\text{mH}, C = 0.5\mu\text{F}$

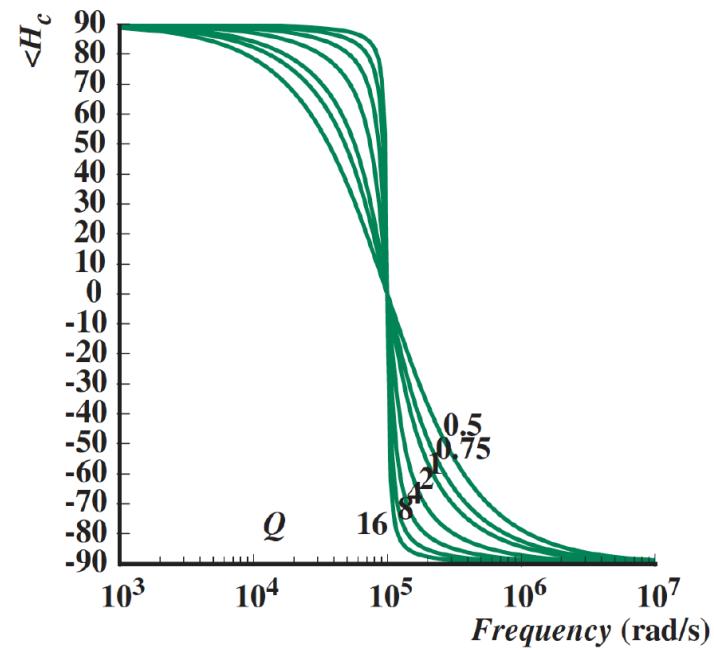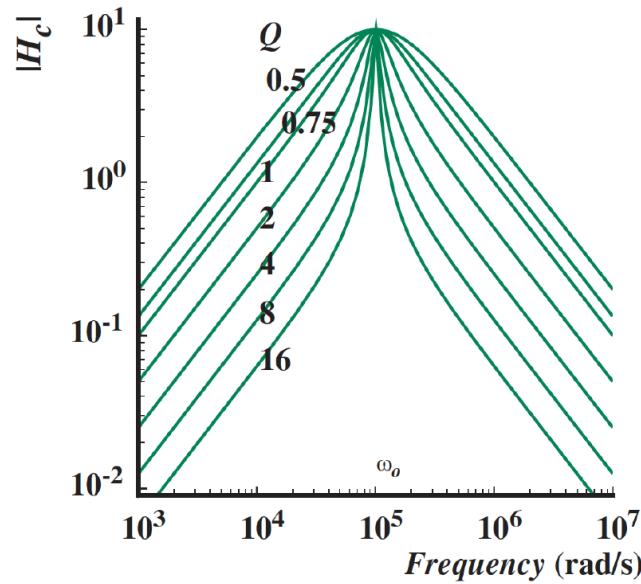Example

Design constraints

Peak gain = 10, $\omega_o = 10^5$ rad/s, $Q = 1, 2, 0.5$



Summary

Parallel RLC circuit transfer function: Can act as a resonant band-pass filter
(but not always, make sure to check that circuit's underdamped!)

Thursday: Series RLC resonant circuit. Measuring output across R, L, or C gives different filter response (bandpass and bandstop).

HW #5 Due Thursday, 12/3

HW#6 Posted, Due Thursday 12/10

(remember: I drop your lowest HW score)