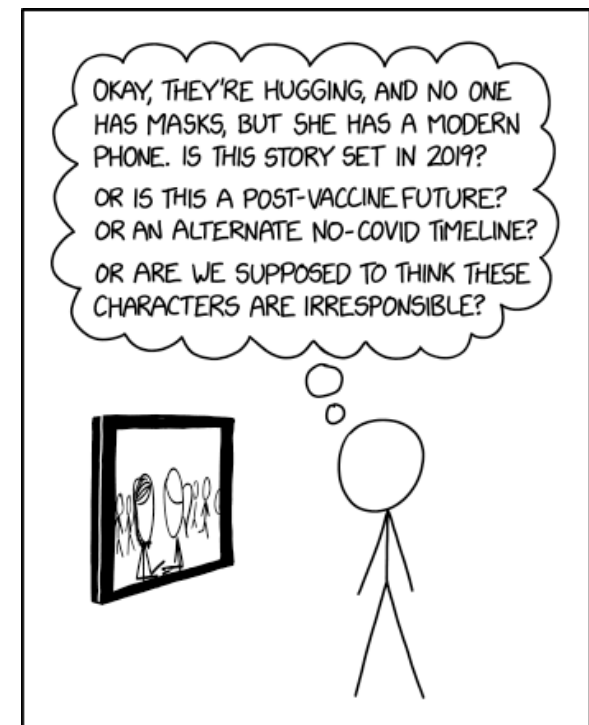


ECE 10C
Fall 2020
Slide Set 8
Instructor: Galan Moody
TA: Kamyar Parto



MOVIES AND SHOWS THAT ARE VAGUELY SET IN "THE PRESENT" WILL BE AWKWARD FOR A WHILE.

Tuesday

- Exam Review
- Op Amps

Today

- Transfer Function
- Logs and dB scale

Important Items:

- HW #4 due Thurs, 11/19
- Lab #4 due 11/20
- **Check your kits to make sure you have all components!**

Quiz Time!

Q1: Let's think about orders of magnitude: The number of electrons/second passing through any point of a wire carrying a 1 A current is approximately equal to (within an order of magnitude or so) [multiple choices]:

- a) The estimated age of the universe, in seconds
- b) The ratio of 1 second to an attosecond (the shortest laser pulse to date)
- c) The ratio of UCSB Turkey Trot 5K distance to the size of an atomic nucleus
- d) All of the above
- e) None of the above


Q2: The decibel (dB) scale is a relative unit of measurement and a convenient way to express the ratio of one value of power to another value. A power ratio of $\frac{1}{2}$ (output/input) approximately corresponds to:

- a) $\frac{1}{2}$ dB
- b) 2 dB
- c) 50 dB
- d) 3 dB
- e) -3 dB

HW 3: Average 89%, Nice Job!

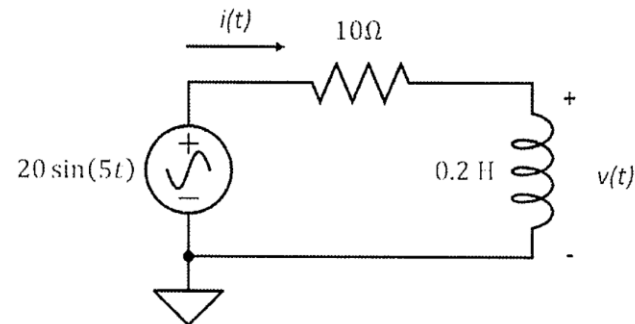Problem 2

Using the impedance method, find $v(t)$ and $i(t)$. Give a very brief explanation of each step to reach the solution



1. $V(t) = 20 \sin(5t) = 20 \cos(5t - \pi/2)$. $\rightarrow V_s = 20 \angle -\pi/2$ ✓

2. $Z = R + j\omega L$ ($\omega = 5 \text{ rad/s}$) $\rightarrow Z = 10 + j \Omega$.

3. $I = \frac{V_s}{Z} = \frac{20 e^{-j\pi/2}}{10 + j} = \frac{-20j}{10 + j} \cdot \frac{10 - j}{10 - j} = \frac{-20 - 200j}{101} = -0.198 - 1.98j \text{ A.}$
 $\cong 2 \angle -1.47 \text{ rad.}$

$i(t) = 2 \cos(5t - 1.47) \text{ A.}$ ✓


4. $V = I \cdot Z_L = (-0.198 - 1.98j) \cdot j = 1.98 - 0.198j$.
 $\cong 2 \angle -0.1 \text{ rad.}$

$V(t) = 2 \cos(5t - 0.1) \text{ V.}$ ✓

HW 3: Average 89%, Nice Job!

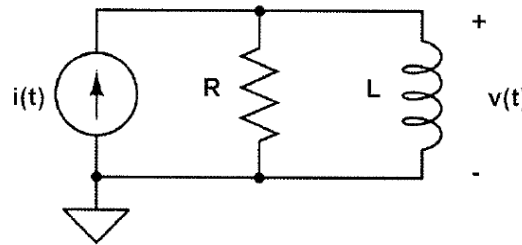Problem 3

Given that $i(t) = I_0 \cos(\omega t)$, where $I_0 = 3 \text{ mA}$ and $\omega = 10^6 \text{ rad/sec}$, determine $v(t)$. Assume $R = 1 \text{ k}\Omega$ and $L = 1 \text{ mH}$.



$$1. \quad i(t) \rightarrow I_0 \angle \phi. \quad Z_R = 1 \text{ k}\Omega \quad Z_L = j \text{ k}\Omega.$$

$$Z_T = \frac{Z_R \cdot Z_L}{Z_R + Z_L} = \frac{1\text{E}3 \cdot 1\text{E}3j}{1\text{E}3 + 1\text{E}3j}$$



$$V = I \cdot Z_T = \frac{I_0 \cdot Z_R Z_L}{Z_R + Z_L} = \frac{3 \cdot j}{1 + j} = \frac{3j}{1+j} \cdot \frac{1-j}{1-j} = \frac{3+3j}{2} = \frac{3}{\sqrt{2}} e^{j\pi/4}$$

$$\text{Thus: } v(t) = \frac{3}{\sqrt{2}} \cos(10^6 \cdot t + \pi/4) \text{ V. } \checkmark$$

HW 3: Average 89%, Nice Job!

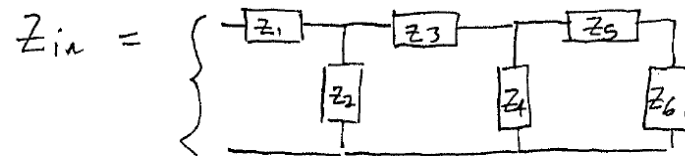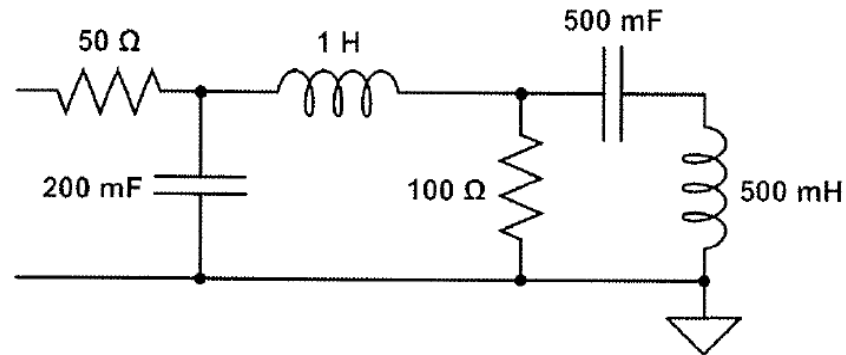Problem 4

Determine the input impedance of the circuit at frequency $\omega = 2 \text{ rad/s}$.




$$Z_{in} = Z_1 + \left[(Z_5 + Z_6) // Z_4 + Z_3 \right] // Z_2$$

$$= Z_1 + \left\{ \left[\frac{(Z_5 + Z_6) \cdot Z_4}{Z_5 + Z_6 + Z_4} + Z_3 \right] \cdot Z_2 \right\} / \left\{ \left[\frac{(Z_5 + Z_6) \cdot Z_4}{Z_5 + Z_6 + Z_4} + Z_3 \right] + Z_2 \right\}$$

HW 3: Average 89%, Nice Job!

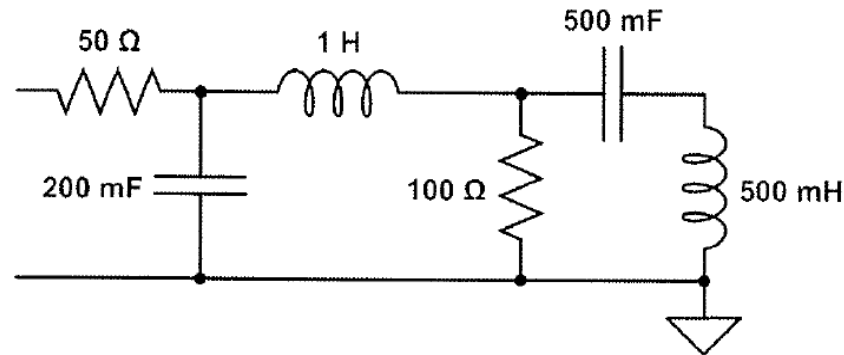Problem 4

Determine the input impedance of the circuit at frequency $\omega = 2 \text{ rad/s}$.



$$Z_1 = 50 \Omega$$

$$Z_2 = \cancel{0.4} - 2.5j \Omega$$

$$Z_3 = 2j \Omega$$

$$Z_4 = 100 \Omega$$

$$Z_5 = -j \Omega$$

$$Z_6 = j \Omega$$

$$Z_5 + Z_6 = 0 \Omega. \text{ Thus:}$$

$$Z_m = Z_1 + [Z_3 \cdot Z_2 / (Z_3 + Z_2)].$$

$$Z_3 + Z_2 = -0.5j \Omega.$$



$$Z_3 \cdot Z_2 = 5 \Omega.$$

↓

$$Z_m = 50 + \frac{5}{-0.5j} = 50 + 10j. \checkmark$$

The Impedance Method

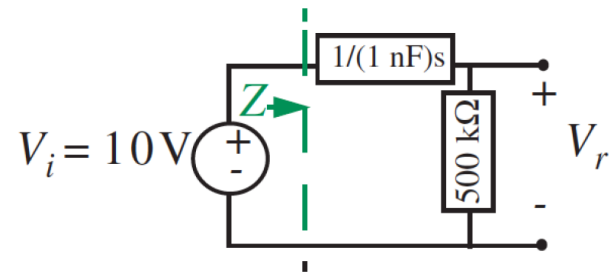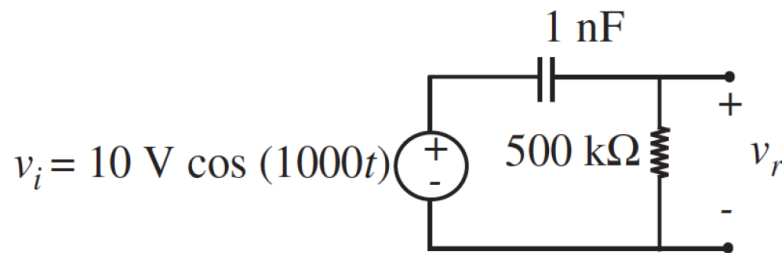Impedance: A generalization of resistance for sinusoidal steady state inputs. Associated with each element is a characteristic impedance that affects the flow of current/voltage drop across the element, analogous to a resistor.



$$v_0(t) = |V_0| \cos(\omega t + \angle V_0) = \text{Re}\{|V_0| e^{j\angle V_0} e^{j\omega t}\}$$

Generalization of Ohm's Law for Sinusoidal Steady State

$$\text{Resistor: } V = IR \rightarrow Z_R = R$$

$$\text{Capacitor: } V = I \frac{1}{sC} \rightarrow Z_C = \frac{1}{sC} = \frac{1}{j\omega C}$$

$$\text{Inductor: } V = sLI \rightarrow Z_L = sL = j\omega L$$

Impedance Method

$$v_0(t) = |V_0| \cos(\omega t + \angle V_0) = \text{Re}\{V_0(j\omega)e^{j\omega t}\}$$

1. First, **replace** the (sinusoidal) sources by the complex amplitudes
2. Then, replace the circuit elements by their impedances. The resulting diagram is called **the impedance model of the network**.
3. Now, **determine the complex amplitudes** of the voltages and currents in the circuits (e.g. $V_c(j\omega)$). You can use any standard linear circuit analysis technique you like—Node method, KVL, KCL, Thevenin, intuitive method based on series/parallel simplifications, etc.
4. Finally, we can obtain the time variables from the complex amplitudes and **plug into the general expression for the dynamics**. This isn't usually necessary though. As an example, the time domain response corresponding to the node variable V_c is given by:

Outline for 2nd half of this course

- **Definition of transfer function [today]**
 - Impedance method simplifies circuit analysis
- **Frequency domain analysis [today/next week]**
 - Log-log plots, Bode plots
 - Intuitive method for plotting frequency response
- **Filter designs [next week, week 9]**
 - Arrange R, L, C circuits to achieve high, low, or bandpass filters
- **Review + Thanksgiving**
- **Resonant filter designs [week 9]**
- **Review / final topics TBD [week 10]**

Frequency Domain Analysis


We've seen that a **circuit's behavior** in steady state **depends on the source frequency**. Frequency domain analysis formally studies this dependence

$$v_o(t) = |V_o| \cos(\omega_1 t + \angle V_o)$$


$$V_o = \frac{Z_R}{Z_R + Z_L} V_i$$

$$V_o = \frac{R}{R + j\omega_1 L} V_i$$

$$\begin{aligned} v_o(t) &= \Re\{V_o e^{j\omega_1 t}\} \\ &= |V_o| \cos(\omega_1 t + \angle V_o) \end{aligned}$$

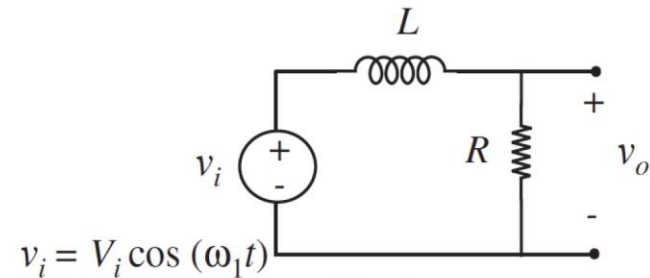

(a) Circuit

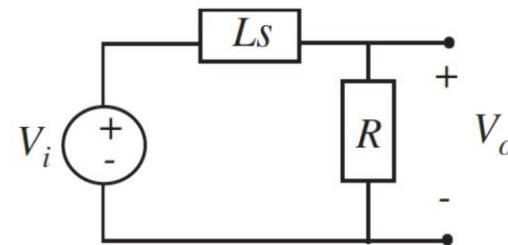

(b) Impedance model


$$v_o(t) = |V_o| \cos(\omega_1 t + \angle V_o) = \frac{R}{\sqrt{R^2 + \omega_1^2 L^2}} V_i \cos\left(\omega_1 t + \tan^{-1} \frac{-\omega_1 L}{R}\right)$$

RL Circuit – Frequency Dependence of Output

- Let's use some numbers

$$L = 1 \text{ mH}$$

$$R = 1 \text{ k}\Omega$$

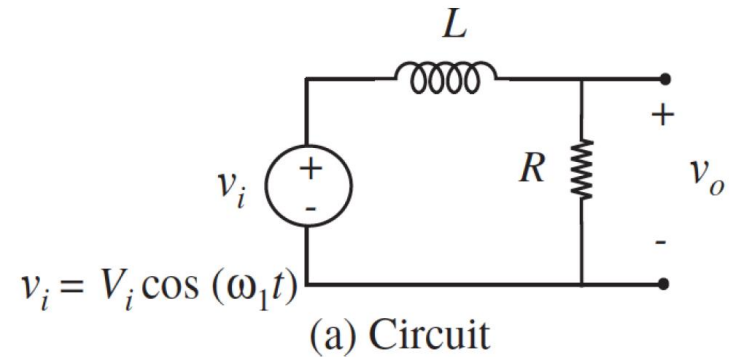

- Using impedances and the voltage divider relation:

$$V_o = \frac{Z_R}{Z_R + Z_L} V_i = \frac{1000}{1000 + j0.001\omega} V_i = H(j\omega) V_i$$

$H(j\omega) = \frac{V_o}{V_i}$ is called the **transfer function**

Transfer Function

Definition

The **transfer function** is the ratio of the complex amplitude of the circuit **output** to the complex amplitude of the **input**

$$H(j\omega) = \frac{V_o}{V_i} = \frac{1000}{1000 + j0.001\omega} \quad \text{(only info about the circuit using its complex impedances)}$$

Given the transfer function of a system, we know:

$$H(j\omega) = |H(j\omega)|e^{\angle H(j\omega)}$$


$$V_o = H(j\omega)V_i$$

The output response of the system to a sinusoidal input $v_i = V_i \cos(\omega t)$ is:

$$v_o(t) = |H(j\omega)|V_i \cos(\omega t + \angle H(j\omega))$$

Transfer Function

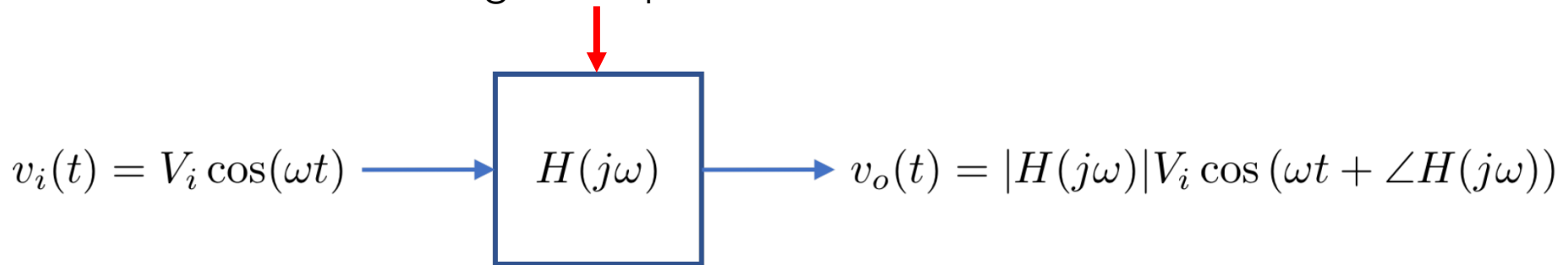determined by analyzing the circuit, independent of the source, using the impedance method



Some naming conventions:

Transfer Type	Output/Input	Units
Transfer Function	V_o/V_i	none
Transconductance (DC) Transadmittance (AC)	I/V	$1/\Omega$
Transresistance/ Transimpedance	V/I	Ω

Frequency Response of a Circuit

$$v_o(t) = |H(j\omega)|V_i\cos(\omega t + \angle H(j\omega))$$

Frequency Response

A plot of the magnitude and phase of the circuit's transfer function as a function of frequency: $|H(j\omega)|$ and $\angle H(j\omega)$




- The magnitude is the ratio of the **amplitudes** of the output and input, and shows the **gain of the circuit** as a function of frequency

$$H(j\omega) = \frac{V_o}{V_i} \quad |H(j\omega)| = \frac{|V_o|}{|V_i|}$$

- The phase is the angular difference between the output and the input sinusoids (**phase shift**)

RL Circuit – Frequency Response
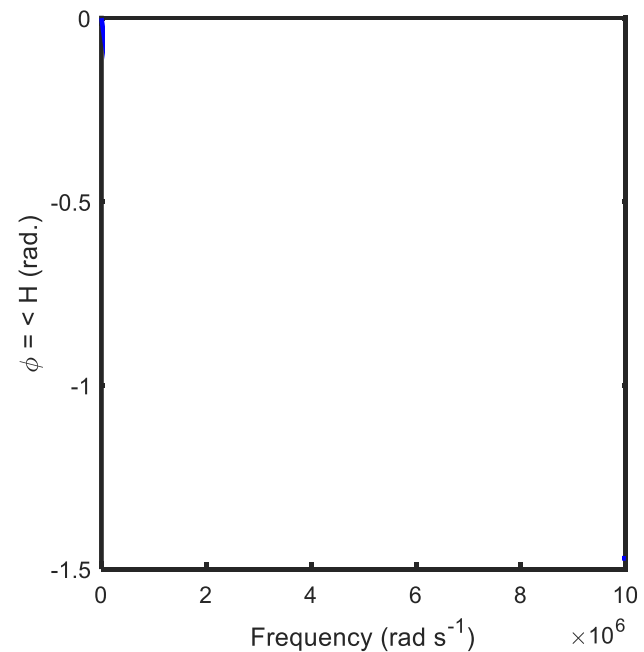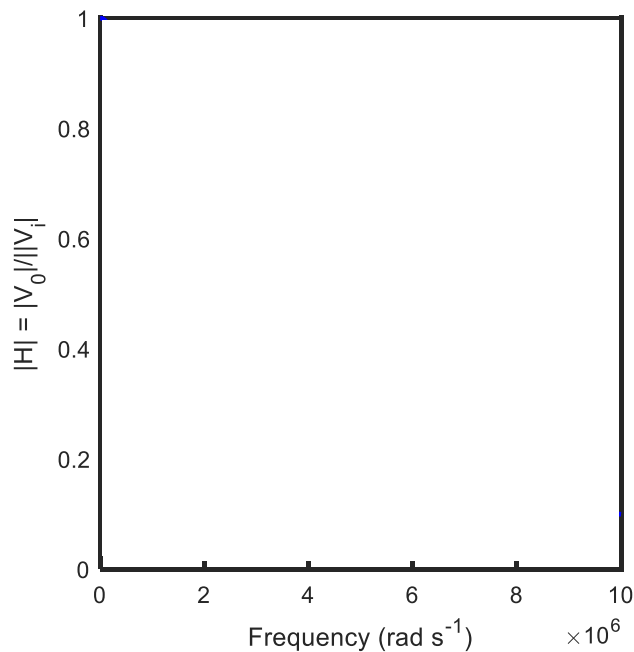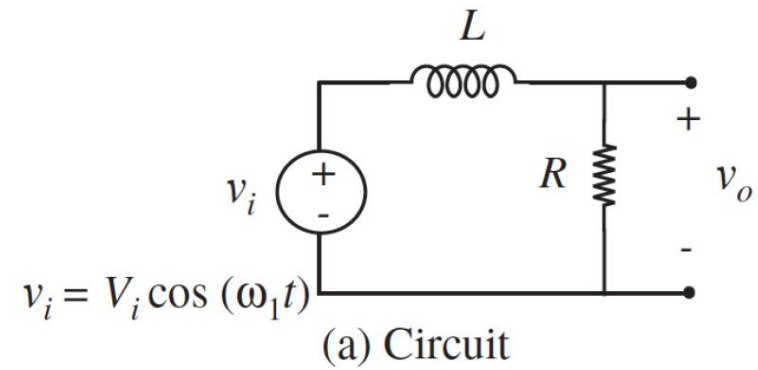
$$H(f) = \frac{V_o}{V_i} = \frac{1000}{1000 + j0.001\omega}$$






RL Circuit – Frequency Response

$$H(f) = \frac{V_o}{V_i} = \frac{1000}{1000 + j0.001\omega}$$

$$\omega \rightarrow 0, H \rightarrow 1 = r[\cos(\varphi) + j\sin(\varphi)]$$
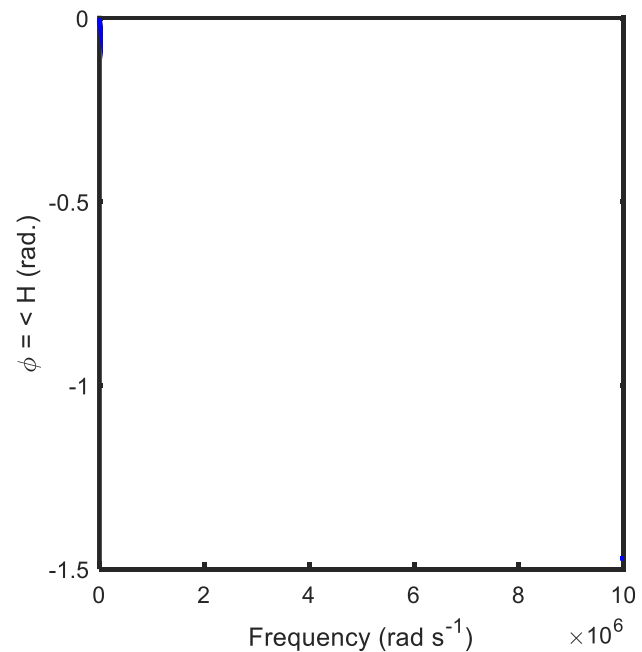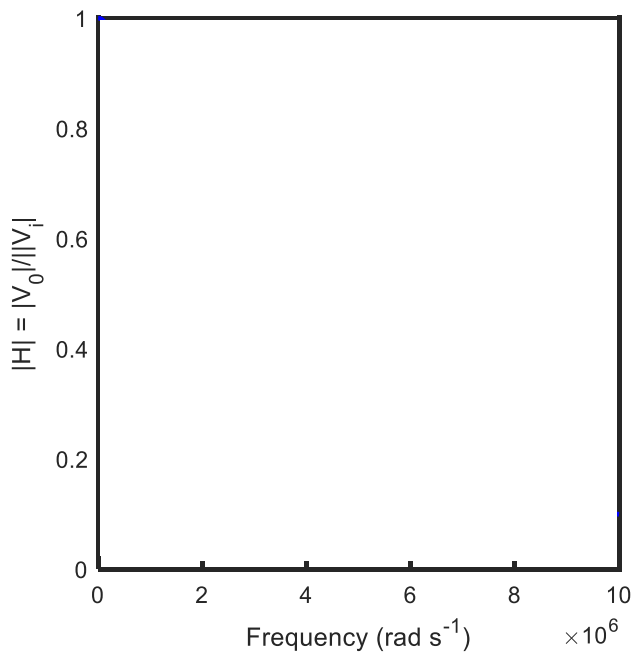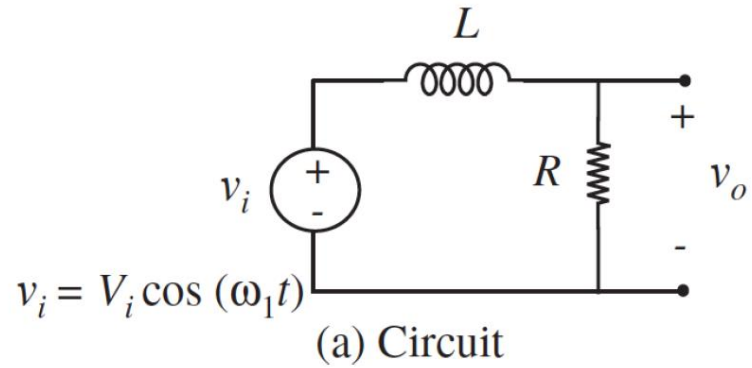
$$\omega \rightarrow \infty, H \rightarrow -j/\omega = r[\cos(\varphi) + j\sin(\varphi)]$$






RL Circuit – Frequency Response

$$H(f) = \frac{V_o}{V_i} = \frac{1000}{1000 + j0.001\omega}$$

$$\omega \rightarrow 0, H \rightarrow 1 = r[\cos(\varphi) + j\sin(\varphi)]$$
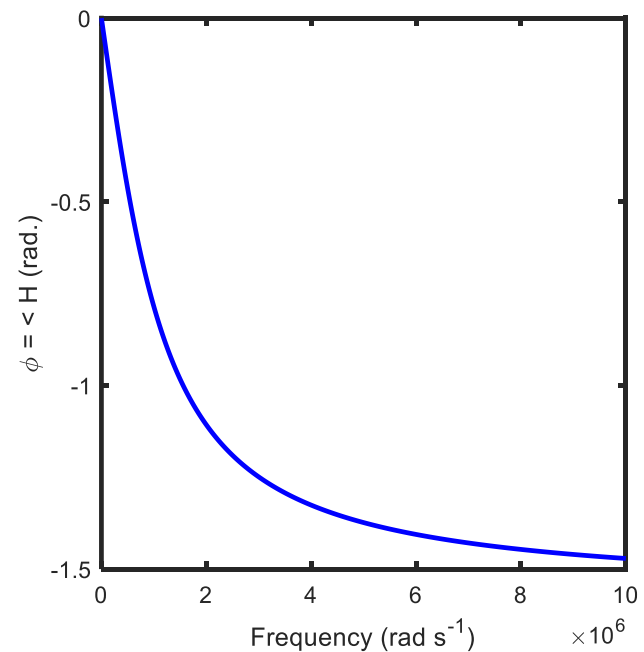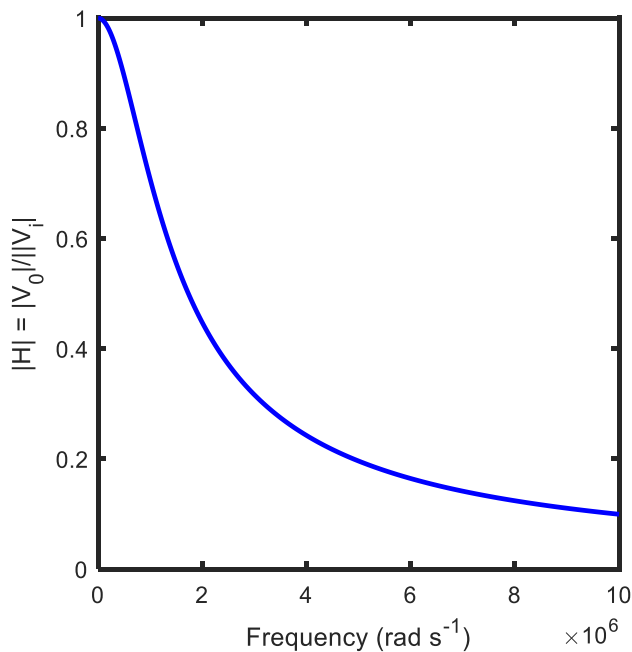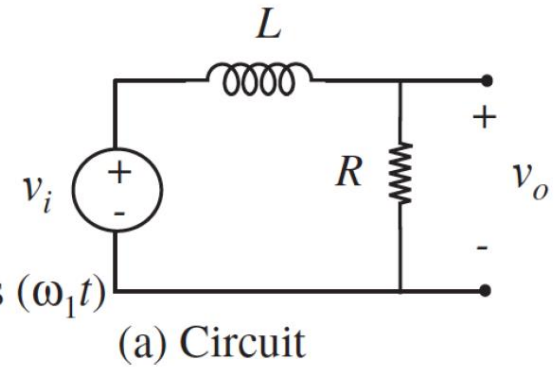
$$\omega \rightarrow \infty, H \rightarrow -j/\omega = r[\cos(\varphi) + j\sin(\varphi)]$$




RL Circuit – Frequency Response

$$H(f) = \frac{V_o}{V_i} = \frac{1000}{1000 + j0.001\omega}$$



$$\omega \rightarrow 0, H \rightarrow 1 = r[\cos(\varphi) + j\sin(\varphi)]$$
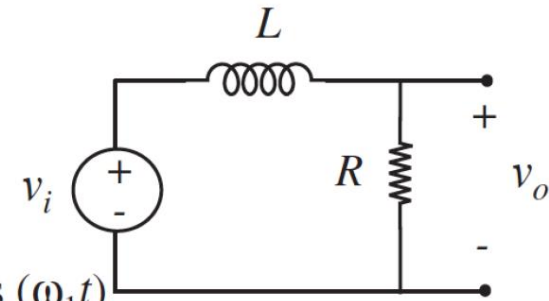
$$\omega \rightarrow \infty, H \rightarrow -j/\omega = r[\cos(\varphi) + j\sin(\varphi)]$$



(a) Circuit

Low-pass filter

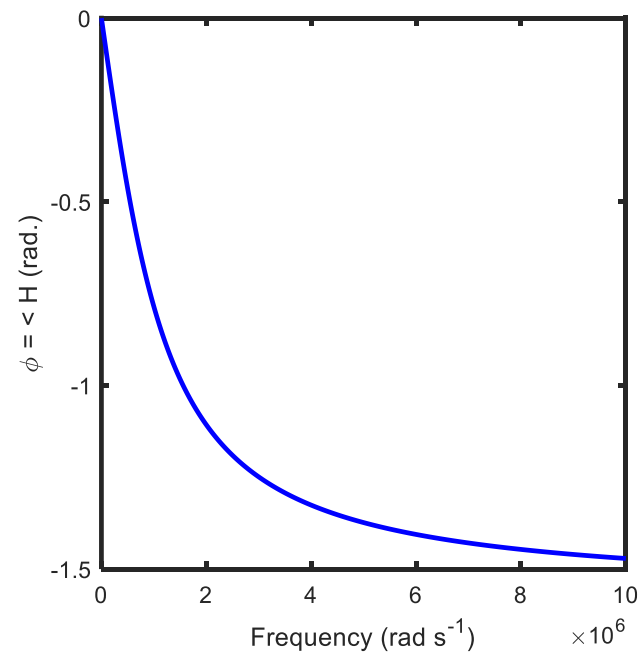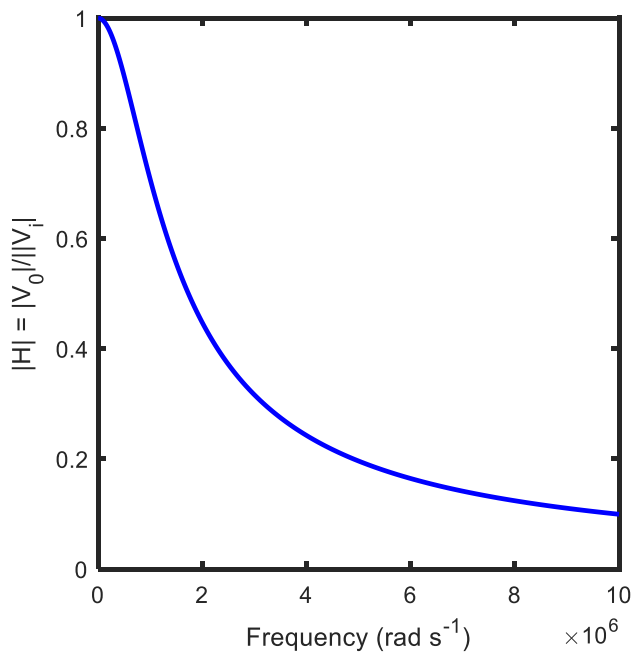

Finding Magnitude and Phase of Transfer Function

$$H(j\omega) = \frac{V_o}{V_i} = \frac{j\omega}{(j\omega + \frac{3}{2})(j\omega + \frac{5}{2})} =$$

Finding Magnitude and Phase of Transfer Function

$$H(j\omega) = \frac{V_o}{V_i} = \frac{j\omega}{(j\omega + \frac{3}{2})(j\omega + \frac{5}{2})} = \frac{A_1}{A_2 A_3} = \frac{|A_1| e^{j\angle A_1}}{|A_2| e^{j\angle A_2} |A_3| e^{j\angle A_3}}$$

Finding Magnitude and Phase of Transfer Function

$$H(j\omega) = \frac{V_o}{V_i} = \frac{j\omega}{(j\omega + \frac{3}{2})(j\omega + \frac{5}{2})} = \frac{A_1}{A_2 A_3} = \frac{|A_1| e^{j\angle A_1}}{|A_2| e^{j\angle A_2} |A_3| e^{j\angle A_3}}$$


$$|H(j\omega)| = \frac{|A_1|}{|A_2| |A_3|} = \frac{\omega}{\sqrt{\omega^2 + \frac{9}{4}} \sqrt{\omega^2 + \frac{25}{4}}}$$

$$\angle H(j\omega) = \angle A_1 - \angle A_2 - \angle A_3 = \frac{\pi}{2} - \tan^{-1} \left(\frac{\omega}{\frac{3}{2}} \right) - \tan^{-1} \left(\frac{\omega}{\frac{5}{2}} \right)$$

Plotting the Frequency Response

typically V_o or I_o
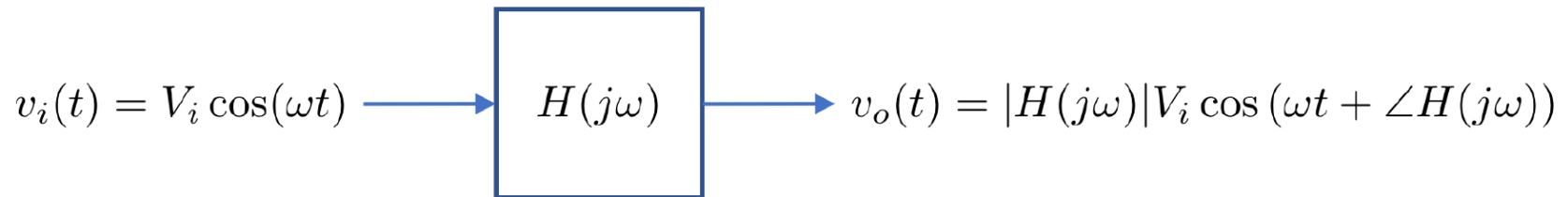
$$\text{transfer function} = H(j\omega) = \frac{\text{complex amplitude of the output}}{\text{complex amplitude of the input}}$$




When asked to plot the frequency response of a system, you need to draw the approximate sketches of the magnitude and phase as follows:

Plotting the Frequency Response

- Plot $|H(j\omega)|$: the log magnitude plotted against log frequency
- Plot $\angle H(j\omega)$: the angle in linear scale plotted against log frequency

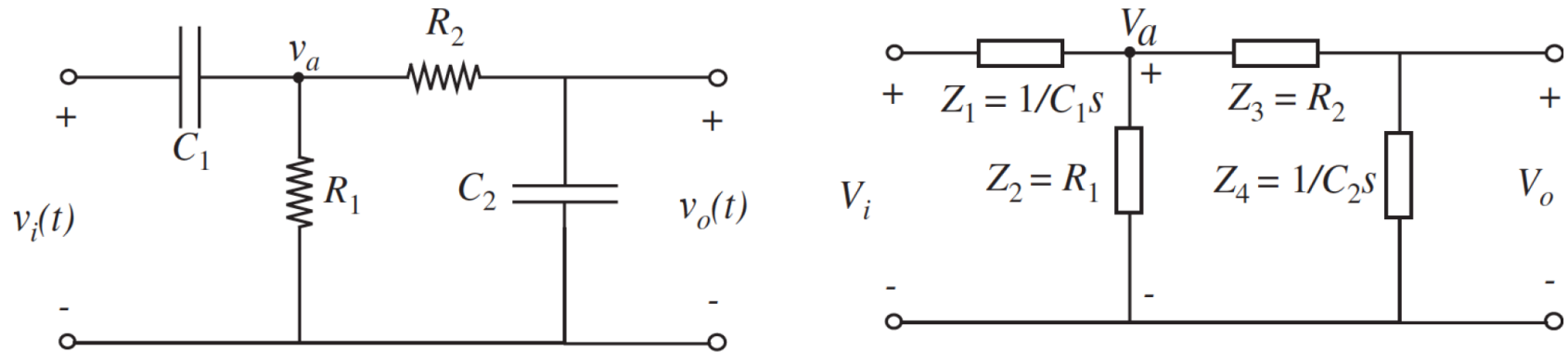Example 1

We find the complex amplitude V_o of the output as a function of V_i :



- You would need to apply the voltage divider relation two times:

$$V_a = \frac{\left(R_2 + \frac{1}{C_2 s}\right) \parallel R_1}{\left(R_2 + \frac{1}{C_2 s}\right) \parallel R_1 + \frac{1}{C_1 s}} V_i$$

$$V_o = \frac{\frac{1}{C_2 s}}{\frac{1}{C_2 s} + R_2} V_a = \left(\frac{\frac{1}{C_2 s}}{\frac{1}{C_2 s} + R_2}\right) \left(\frac{\left(R_2 + \frac{1}{C_2 s}\right) \parallel R_1}{\left(R_2 + \frac{1}{C_2 s}\right) \parallel R_1 + \frac{1}{C_1 s}}\right) V_i$$

Example 1

$$V_o = \frac{\frac{1}{C_2 s}}{\frac{1}{C_2 s} + R_2} V_a = \left(\frac{\frac{1}{C_2 s}}{\frac{1}{C_2 s} + R_2} \right) \left(\frac{\left(R_2 + \frac{1}{C_2 s} \right) \parallel R_1}{\left(R_2 + \frac{1}{C_2 s} \right) \parallel R_1 + \frac{1}{C_1 s}} \right) V_i$$



- Assume $R_1 = 1 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$, $C_1 = 1 \text{ mF}$, $C_2 = 1 \text{ mF}$

$$\begin{aligned} V_o &= \frac{R_1 C_1 s}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2) s + 1} V_i \\ &= \frac{s}{s^2 + 3s + 1} \\ &\stackrel{s=j\omega}{=} \frac{j\omega}{\left(j\omega - \frac{-3-\sqrt{5}}{2} \right) \left(j\omega - \frac{-3+\sqrt{5}}{2} \right)} V_i \\ &= \frac{|A_1|}{|A_2||A_3|} e^{j(\phi_1 - \phi_2 - \phi_3)} V_i \end{aligned}$$

Example 1

$$H(j\omega) = \frac{V_o}{V_i} = \frac{j\omega}{\left(j\omega - \frac{-3-\sqrt{5}}{2}\right) \left(j\omega - \frac{-3+\sqrt{5}}{2}\right)}$$



Let us plot $|H(j\omega)|$ and $\angle H(j\omega)$:

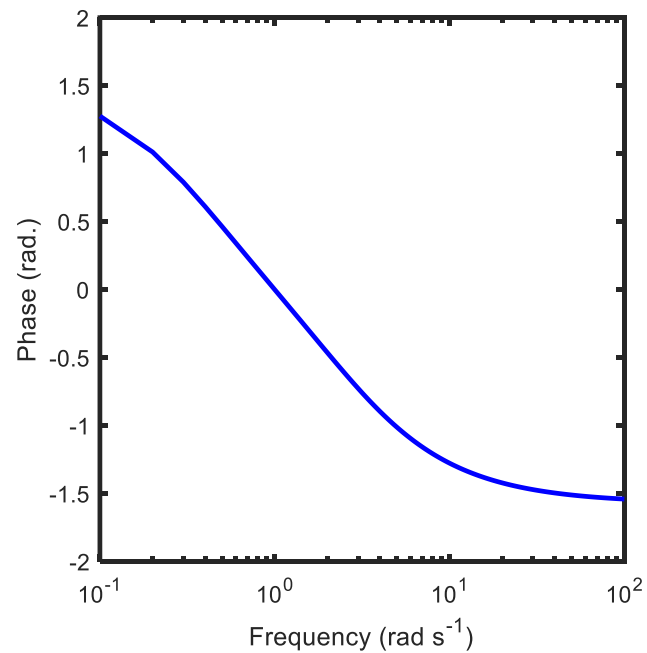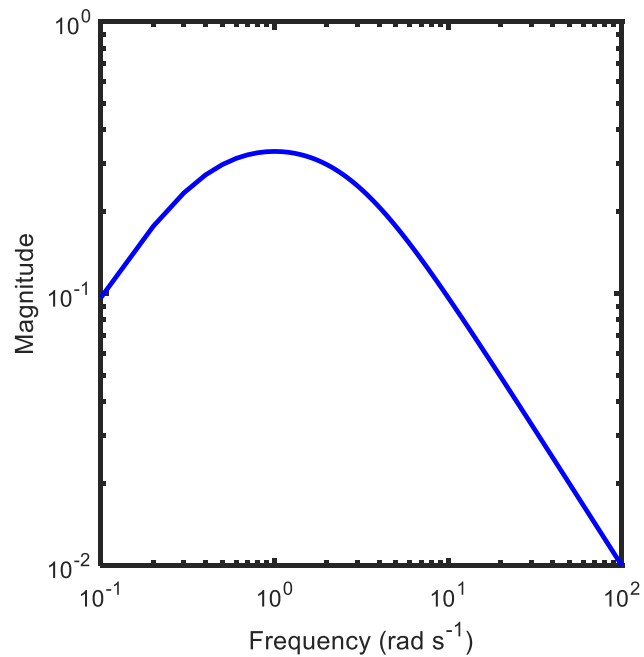

Example 1

$$H(j\omega) = \frac{V_o}{V_i} = \frac{j\omega}{\left(j\omega - \frac{-3-\sqrt{5}}{2}\right) \left(j\omega - \frac{-3+\sqrt{5}}{2}\right)}$$

Let us plot $|H(j\omega)|$ and $\angle H(j\omega)$:

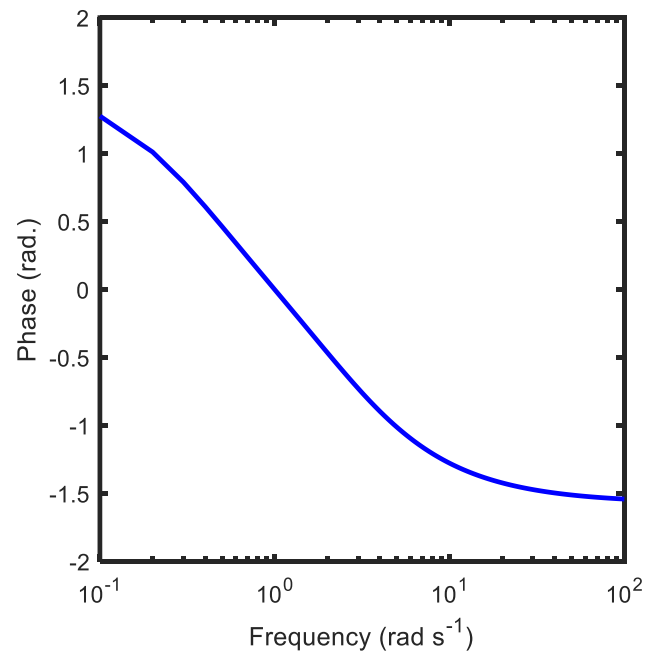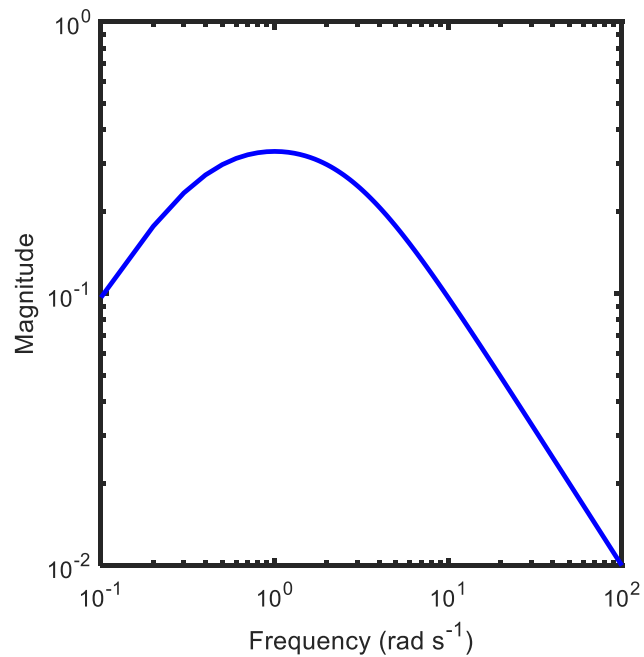

attenuates both low and high frequencies

Plotting the Frequency Response

- Let's review log-log plots
- Plot transfer functions for R, L, and C on their own
- Intuitive sketching of RL and RC plots
- Examples

dB	power ratio	amplitude ratio
100	10 000 000 000	100 000
90	1 000 000 000	31 620
80	100 000 000	10 000
70	10 000 000	3 162
60	1 000 000	1 000
50	100 000	316.2
40	10 000	100
30	1 000	31.62
20	100	10
10	10	3.162
3	1.995	1.413
1	1.259	1.122
0	1	1
-10	0.1	0.316 2
-20	0.01	0.1
-30	0.001	0.031 62
-40	0.000 1	0.01
-50	0.000 01	0.003 162
-60	0.000 001	0.001
-70	0.000 000 1	0.000 316 2
-80	0.000 000 01	0.000 1
-90	0.000 000 001	0.000 031 62
-100	0.000 000 000 1	0.000 01

Decibels:

$$P_2 = 10^{L/10 \text{ dB}} P_1$$


$$L = 10 \log(P_2/P_1) \text{ dB}$$

$$P = \frac{V^2}{R} = i^2 * R$$

$$L = 20 \log(V_2/V_1) \text{ dB}$$

Review of Log Plots

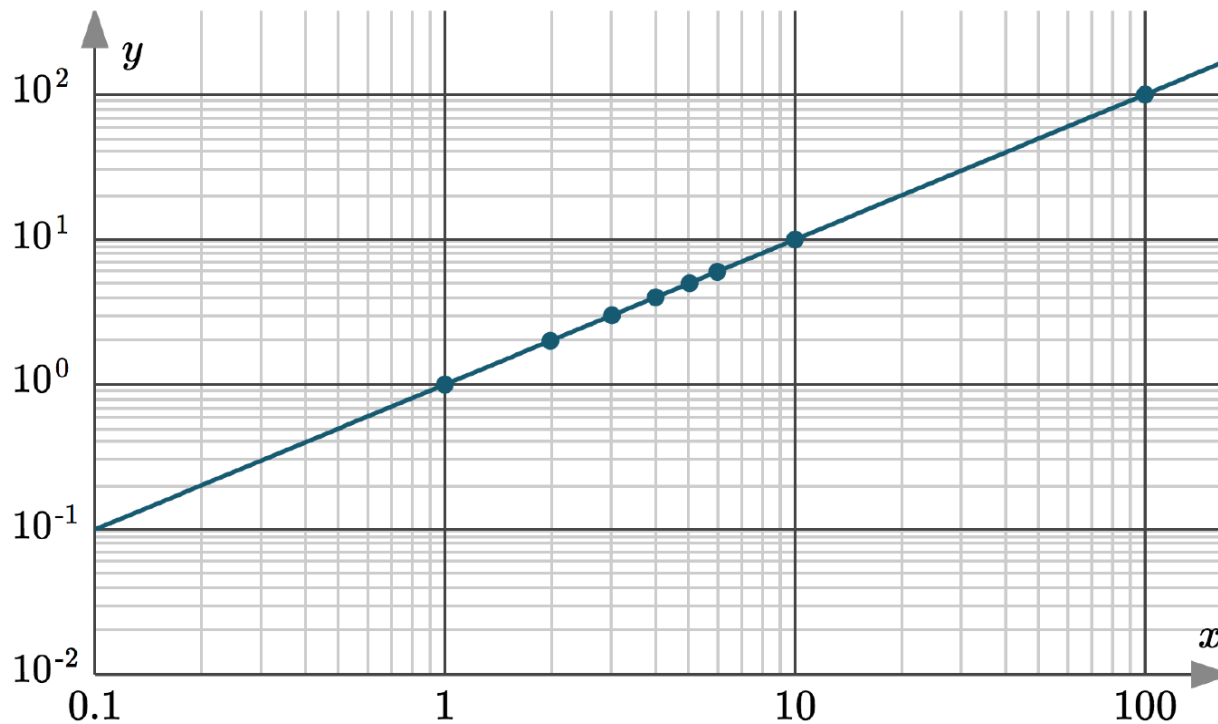- In log-log plots, both axes are on logarithmic (base 10) scale



- Easier to see details for small values of y as well as large values of y

Review of Log Plots

Power relations of the form

$$y = kx^p, \quad p \begin{matrix} \leq \\ > \end{matrix} 0$$

may be rendered straight by plotting on log-log paper

Take the logarithm of both sides

$$\log y = \log K + p \log x$$

Now if y is plotted against x on log-log paper we get a line of slope:

$$\frac{\log y_2 - \log y_1}{\log x_2 - \log x_1} = p$$

To draw a line, you need the slope + a point the line passes through


On the log-log paper, neither intercept has any useful meaning
($\log x$ never has a zero value)


Pick another point to draw the line

Examples: R, L, and C


- First, we'll see what the frequency response of resistors, capacitors, and inductors looks like to build some intuition
- Then we'll study a general method of approximately sketching the frequency response of complex circuits

$$Z = j\omega L$$

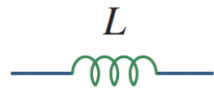


Short circuit at dc


The diagram shows a blue wire with a red wire connected in parallel across it, representing a short circuit.

Open circuit at high frequencies


The diagram shows a blue wire with two open circles, representing an open circuit.

$$Z = 1/j\omega C$$

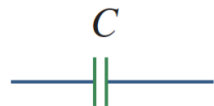

Open circuit at dc

The diagram shows a blue wire with two open circles, representing an open circuit.

Short circuit at high frequencies

The diagram shows a blue wire with a red wire connected in parallel across it, representing a short circuit.

Examples: R, L, and C

We know the element laws for resistors, inductors, and capacitors in terms of complex amplitudes of V and I :

$$\text{Resistor: } V_o = RI_o$$

$$\text{Inductor: } V_o = sLI_o = j\omega LI_o$$

$$\text{Capacitor: } V_o = \frac{1}{sC}I_o = \frac{1}{j\omega C}I_o$$

So the elements' frequency response is:

$$\text{Resistor: } H(j\omega) = \frac{V_o}{I_o} = R$$

$$\text{Inductor: } H(j\omega) = \frac{V_o}{I_o} = j\omega L$$

$$\text{Capacitor: } H(j\omega) = \frac{V_o}{I_o} = \frac{1}{j\omega C}$$

Examples: R, L, and C

So here is the frequency response. How do we plot them?

$$\text{Resistor: } H(j\omega) = \frac{V_o}{I_o} = R$$

$$\text{Inductor: } H(j\omega) = \frac{V_o}{I_o} = j\omega L$$

$$\text{Capacitor: } H(j\omega) = \frac{V_o}{I_o} = \frac{1}{j\omega C}$$

Let's calculate the magnitude and phase of the frequency response:



$$\text{Resistor: } \left| \frac{V_o}{I_o} \right| = R, \quad \angle \frac{V_o}{I_o} = 0$$

$$\text{Inductor: } \left| \frac{V_o}{I_o} \right| = \omega L, \quad \angle \frac{V_o}{I_o} = \frac{\pi}{2}$$

$$\text{Capacitor: } \left| \frac{V_o}{I_o} \right| = \frac{1}{\omega C}, \quad \angle \frac{V_o}{I_o} = -\frac{\pi}{2}$$

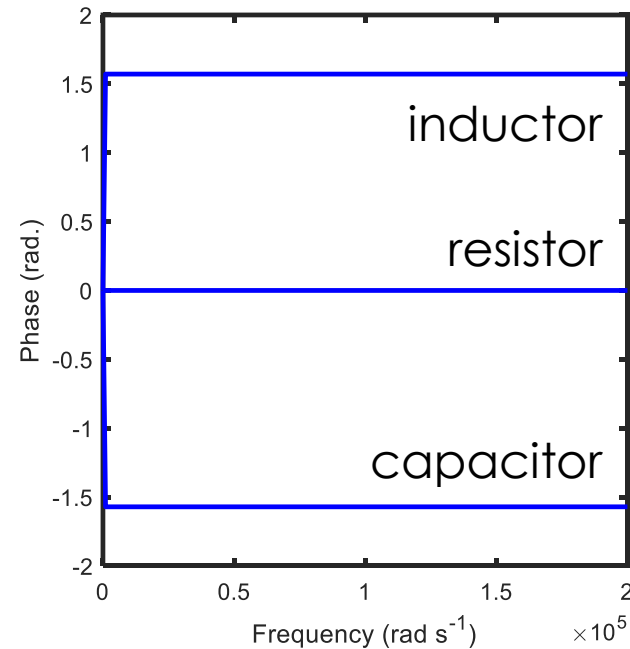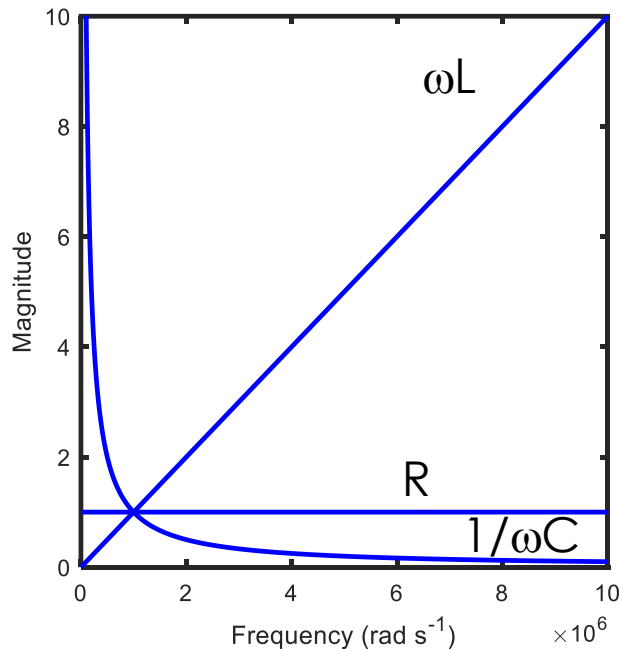Examples: R, L, and C on Linear Scale

Plot the frequency response for $R = 1\Omega$, $L = 1\mu\text{H}$, and $C = 1\mu\text{F}$





Resistor: $\left| \frac{V_o}{I_o} \right| = R, \quad \angle \frac{V_o}{I_o} = 0$

Inductor: $\left| \frac{V_o}{I_o} \right| = \omega L, \quad \angle \frac{V_o}{I_o} = \frac{\pi}{2}$

Capacitor: $\left| \frac{V_o}{I_o} \right| = \frac{1}{\omega C}, \quad \angle \frac{V_o}{I_o} = -\frac{\pi}{2}$

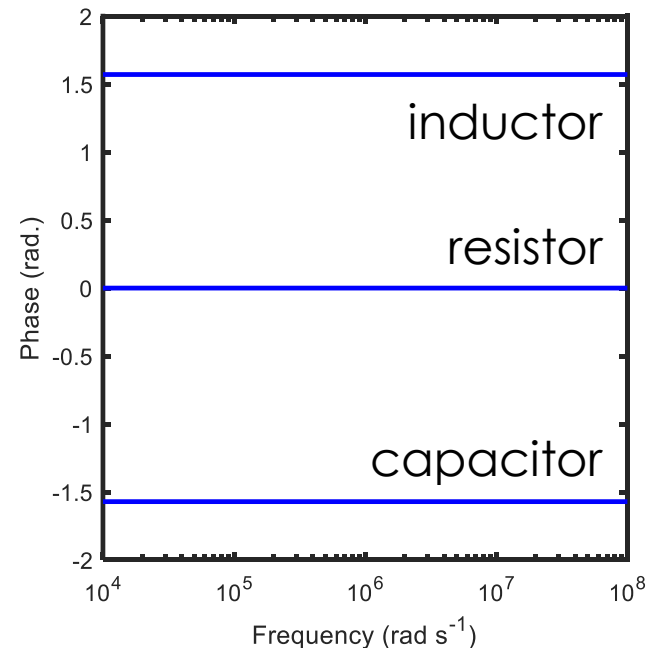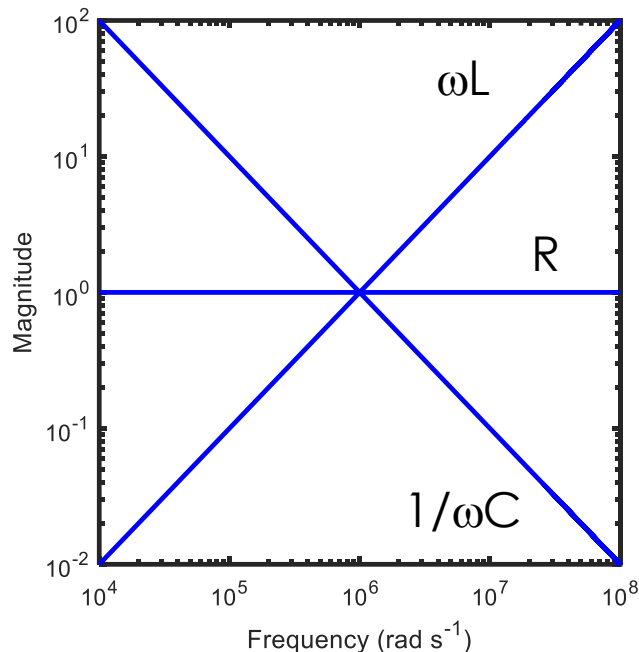Examples: R, L, and C on Log Scale

Plot the frequency response for $R = 1\Omega$, $L = 1\mu\text{H}$, and $C = 1\mu\text{F}$



$$\text{Resistor: } \log \left| \frac{V_o}{I_o} \right| = \log R$$

If we use log scales: Inductor: $\log \left| \frac{V_o}{I_o} \right| = \log L\omega = \log L + \log \omega$

$$\text{Capacitor: } \log \left| \frac{V_o}{I_o} \right| = \log \frac{1}{\omega C} = -\log C - \log \omega$$

Summary of Log Plots

- Imagine if you wanted to plot:

$$|H(j\omega)| = \left| \frac{j\omega + 1}{2j\omega + 1} \right|$$

- Summing terms is easy to do graphically; products are harder
- On a log scale, products (and divisions) turn into a sum:


$$\log \left| \frac{j\omega + 1}{2j\omega + 1} \right| = \log |j\omega + 1| - \log |2j\omega + 1|$$

- You'll see shortly how we plot terms that appear in RL and RC circuits

Intuitive Sketching for RL and RC Circuits

- Let's first consider the series RL circuit:
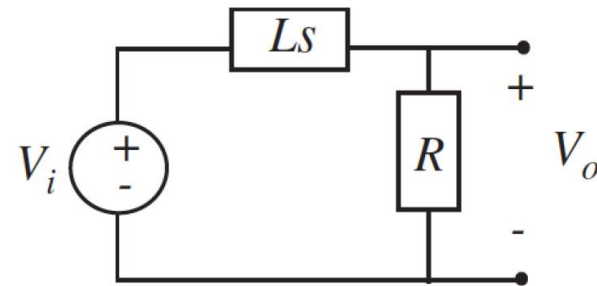
$$\begin{aligned} H(j\omega) &= \frac{V_o}{V_i} = \frac{R}{R + j\omega L} \\ &= \frac{\frac{R}{L}}{\frac{R}{L} + j\omega} \end{aligned}$$



(b) Impedance model

- So we get:

$$\begin{aligned} |H(j\omega)| &= \left| \frac{\frac{R}{L}}{\frac{R}{L} + j\omega} \right| \\ \angle H(j\omega) &= \tan^{-1} \frac{-\omega L}{R} \end{aligned}$$

Intuitive Sketching, Magnitude $|H(j, \omega)|$

- First, find the asymptotes of the magnitude plot:

$$|H(j\omega)| = \left| \frac{\frac{R}{L}}{\frac{R}{L} + j\omega} \right|$$

- At low frequencies ($\omega \rightarrow 0$):

$$|H(j\omega)| \approx 1$$

- Hence the magnitude appears as a horizontal line at low frequencies
- At high frequencies $\omega \rightarrow \infty$, ω dominates in the denominator


$$|H(j\omega)| \approx \frac{R/L}{\omega} \rightarrow \log |H(j\omega)| \approx \log R/L - \log \omega$$

- On a log scale, a line with slope = -1 passing through (R/L, 1)**

Intuitive Sketching, Magnitude $|H(j, \omega)|$

- At low frequencies ($\omega \rightarrow 0$): $|H(j\omega)| = 1$
- At high frequencies $\omega \rightarrow \infty$, ω dominates in the denominator


$$|H(j\omega)| \approx \frac{R/L}{\omega} \rightarrow \log |H(j\omega)| \approx \log R/L - \log \omega$$

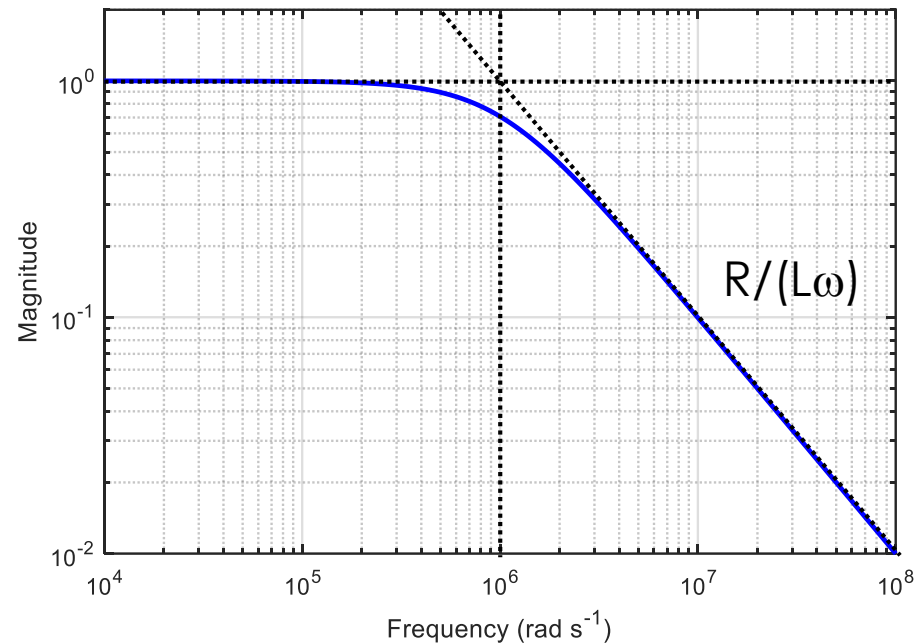

Intuitive Sketching, Magnitude $|H(j, \omega)|$

- The two asymptotes intersect at: $\omega = \frac{R}{L}$
- This frequency is called the “corner” or “cutoff” frequency


At the cutoff frequency, the real and imaginary components of $H(j, \omega)$ are equal, and $|H(j, \omega)| = \frac{1}{\sqrt{2}} = 0.707$

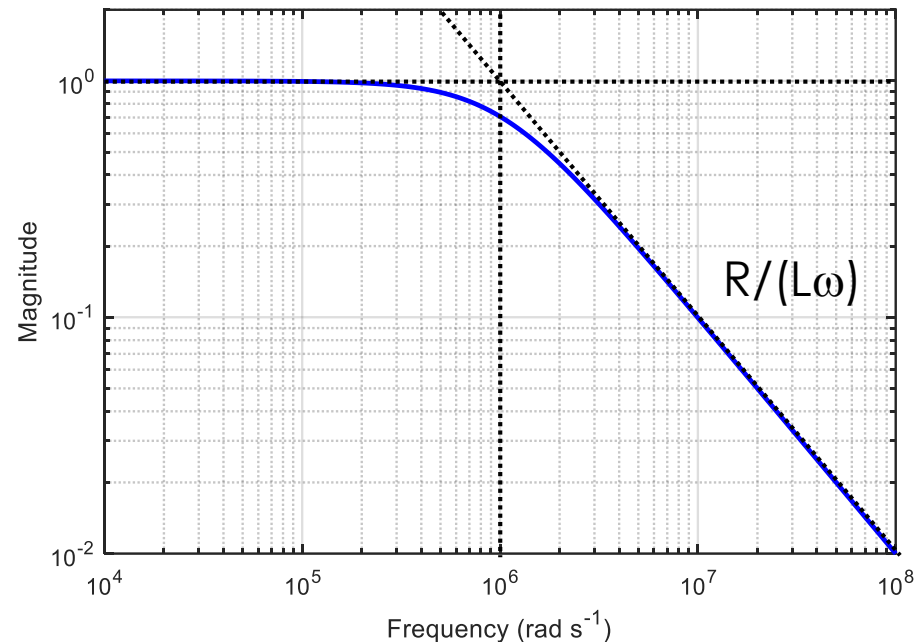

$$|H(j\omega)| \approx \frac{R/L}{\omega} \rightarrow \log |H(j\omega)| \approx \log R/L - \log \omega$$

Intuitive Sketching, Magnitude $|H(j, \omega)|$

At the cutoff frequency, the real and imaginary components of $H(j, \omega)$ are equal, and $|H(j, \omega)| = \frac{1}{\sqrt{2}} = 0.707$

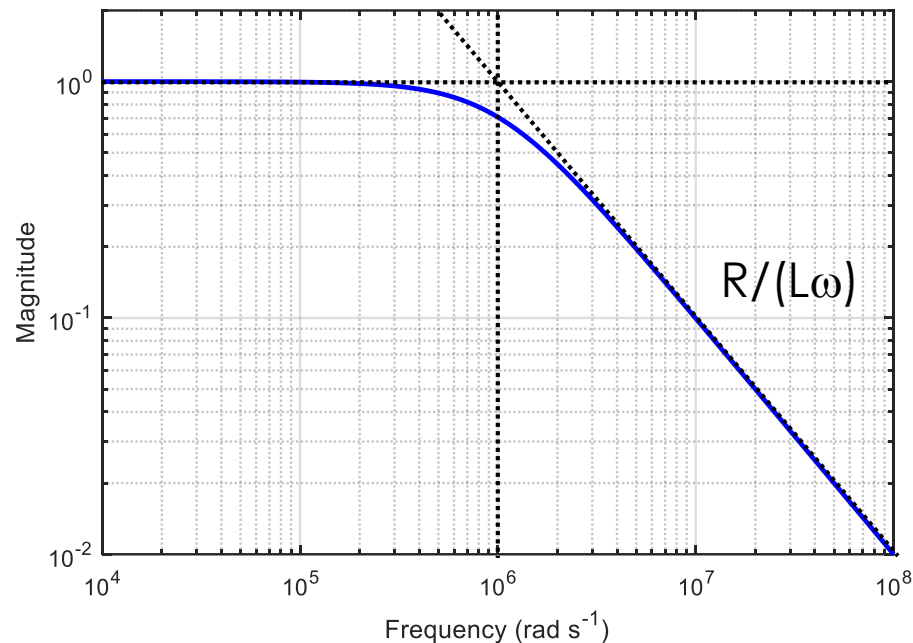

1

Decibels:

$$P_2 = 10^{L/10 \text{ dB}} P_1$$

$$L = 10 \log(P_2/P_1) \text{ dB}$$

$$10 \log\left(\frac{1}{2}\right) \sim -3 \text{ dB}$$



Recall that power dissipated through impedance Z is $\frac{V_0^2}{Z}$, and $V_0^2 \propto |H(j, \omega)|^2$. At the cutoff frequency, $|H(j, \omega)|^2 = 1/2$. **Thus the cutoff frequency also tells you the “3 dB” point**, i.e. the frequency at which the output power is halved.

Intuitive Sketching, Phase $\angle H(j, \omega)$

$$H(j\omega) = \frac{\frac{R}{L}}{\frac{R}{L} + j\omega}$$

- At low frequencies ($\omega \rightarrow 0$): $\angle H(j\omega) \approx \angle 1 = 0$
- At high frequencies $\omega \gg R/L$, ω dominates in the denominator

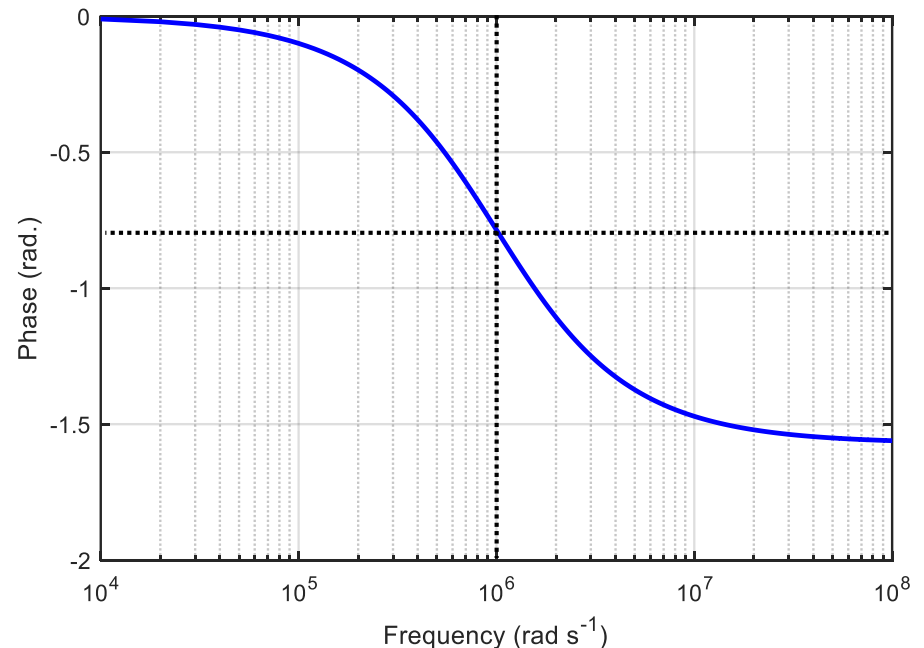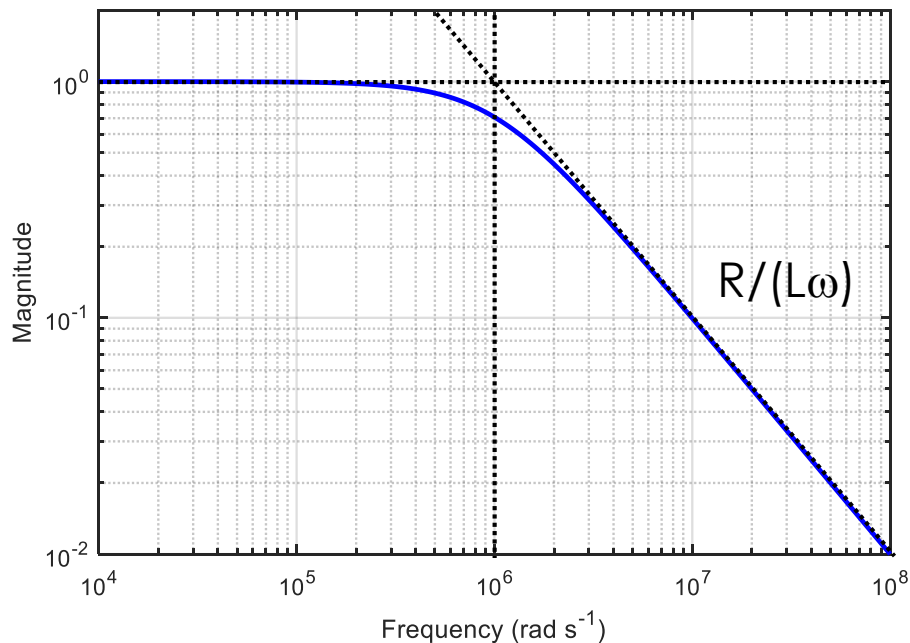
$$\angle H(j\omega) \approx \angle \frac{1}{j\omega} = -\frac{\pi}{2}$$



Summary

typically V_o or I_o
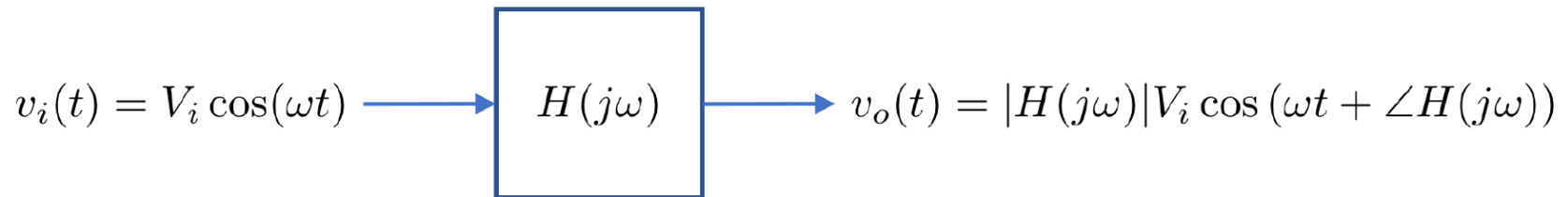
$$\text{transfer function} = H(j\omega) = \frac{\text{complex amplitude of the output}}{\text{complex amplitude of the input}}$$



When asked to plot the frequency response of a system, you need to draw the approximate sketches of the magnitude and phase as follows:

Plotting the Frequency Response

- Plot $|H(j\omega)|$: the log magnitude plotted against log frequency
- Plot $\angle H(j\omega)$: the angle in linear scale plotted against log frequency

Next Week

- Finish up Transfer Function, Log and Bode Plots
- Begin Filter Design
- Don't forget HW 4 due next Thursday
- Don't forget Lab 4 due next Friday